



CALCULATOR LEARNS TO KEEP TIME

INTRODUCTION

A number of interesting stopwatch and elapsed time functions can be implemented using the MM5736 calculator chip and a few packages of CMOS gates. This note describes six different circuits that are intended to stimulate thinking along these lines. The circuits to be described are listed below.

1. Stopwatch with 1/10 second resolution
2. Stopwatch with 1/100 second resolution
3. Stopwatch/calculator (1/10 second resolution)
4. Stopwatch/calculator (1/100 second resolution)
5. Stopwatch with 1/10 secs, secs, mins display
6. Interval timer with keyboard and alarm

With the exception of circuits 5 and 6 all of these circuits work in decimal fractions of seconds. They do not display in seconds and minutes. Circuit 6 displays minutes and tenths of minutes but not seconds. Circuit 5 displays tenths of seconds, seconds and minutes. It is anticipated that a number of applications can be satisfied by counting in only one unit, either seconds or minutes.

In all these circuits, the MM5736 calculator chip is used in the autosumming mode as a counting and display element. Application note AN-112 illustrates how to accomplish this counting. A thorough understanding of the calculator's operation as a counter can be gained from AN-112 and the MM5736 data sheet. Consequently, the emphasis in this note is on controlling the counter in such a way that useful timing functions are performed.

Two types of timebases are also described. The first, a CMOS RC oscillator, is depicted in all the circuits described but may not be stable enough for some applications. Consequently, a simple crystal controlled timebase is also described.

STOPWATCH WITH 0.1 SECOND RESOLUTION

The circuit in *Figure 1* provides the classic stopwatch functions of:

- A) START
- B) STOP
- C) RESET

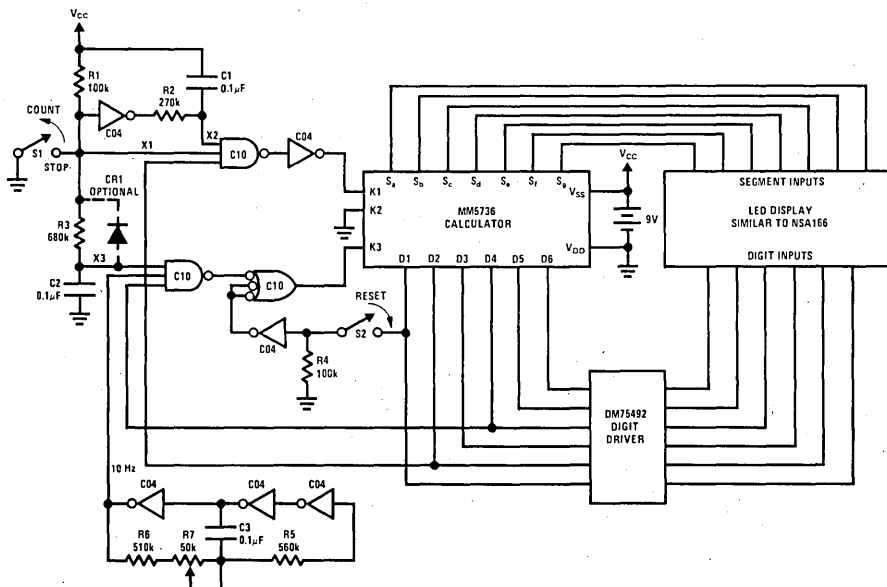


FIGURE 1. 1/10 Second Stopwatch

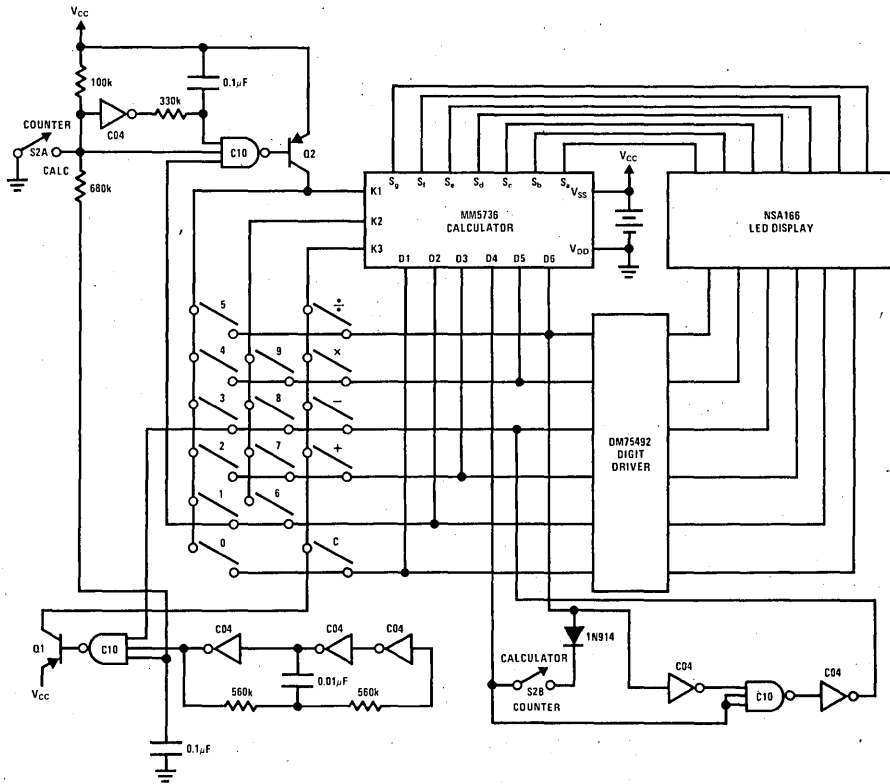


FIGURE 4. 1/100 Second Stopwatch/Calculator

Since the counter is clocked by D3, only a 6 in the 3rd digit will cause the counter to be present. This corresponds to a time of 60.0 seconds and signals the beginning of a base 60 conversion. The counter is preset to the state 1001 0000. Since the MSB is a 1, the counter's count enable term is enabled and its load term is disabled. It will now count word times on every D3.

Reference to AN-112 will reveal that with the calculator "speeded up" it is necessary to allow a digit output to be connected to the inputs for a minimum of 4 word times and then there must be at least 4 word times during which nothing is applied to the calculator inputs before the next entry is allowed. This timing is accomplished by Q_D of the low order counter. It toggles with a half period of 8 word times. This Q_D is connected to the D input of the decoder which is used as an enable input. When this signal is high, all outputs of the decoder are high and all the MOS transistors are off. When this signal is low the proper decoder output is low. So the first 4 bits of the counter provide timing and the next 3 bits provide the necessary sequence of entries. The last bit turns the sequence on or off. The sequence of entries is as described earlier and is implemented by transistors Q2-Q7.

Initialization

When S1 is first switched to the stopwatch mode, a burst of D2 pulses is gated into the K1 input by the one shot comprised of R2, C1 and the gate that drives Q8. This enters a "1" to get the calculator ready to count. A little later, Q9 will be turned on by the timebase oscillator at a 10 Hz rate and counting will begin.

Segment Drivers

Two DM8895 segment drivers are used in *Figure 5*. This is not absolutely necessary. The calculator can drive some displays directly. However, it is necessary to buffer both segment e and segment b to preserve proper logic levels for the CMOS decoding gates. This could be done by non-inverting CMOS buffers like the MM80C96 or 2 inverters in series. But if only S_a and S_b are buffered, there is no guarantee of segment intensity uniformity. Therefore, it is more desirable to buffer all segments. The DM8895 is a segment driver with internal current limiting resistors that are mask programmable. The DM75491 could also be used if external resistors are not objectionable.

"Speed Up" Circuit

Transistors Q11 and Q10 implement the "speed up" function in the same way as that described in Figure 2 except that naked MOS transistors are used in place of the MM5616 CMOS switch.

AN INTERVAL TIMER WITH A KEYBOARD

An interval timer that can be programmed to time out long intervals can also be made using the calculator chip. The desired time interval is entered from a keyboard. When the interval is complete, a tone is emitted by a small speaker until the operator activates a RESET switch. The timer (as described) will handle intervals as long as 99999.9 minutes, which is about 69 1/2 days. This is probably too long an interval for an RC oscillator to be acceptable as a timebase. Figure 6 shows an RC oscillator but it could be replaced by the crystal oscillator described later in this note. Counting speeds other than 0.1 minutes could be used as long as the counting speed of the calculator is not exceeded.

Circuit Description


As was the case for the stopwatch described in Figure 5, a small controller made from a counter and a decoder is used to switch Digit outputs to the proper K input to create the sequence of entries required. The counter is clocked by a 30 Hz oscillator whose output is also gated with all the Digit lines to create the proper "key down" and "key up" times.

There are two sequences of entries required: one for RESET and one for START, the beginning of the timing interval.

Reset Sequence

When the RESET switch is activated, it is debounced by a latch and differentiated by C1 to generate a positive going pulse that clears the MM74C193 controller counter and the sequence proceeds as follows:

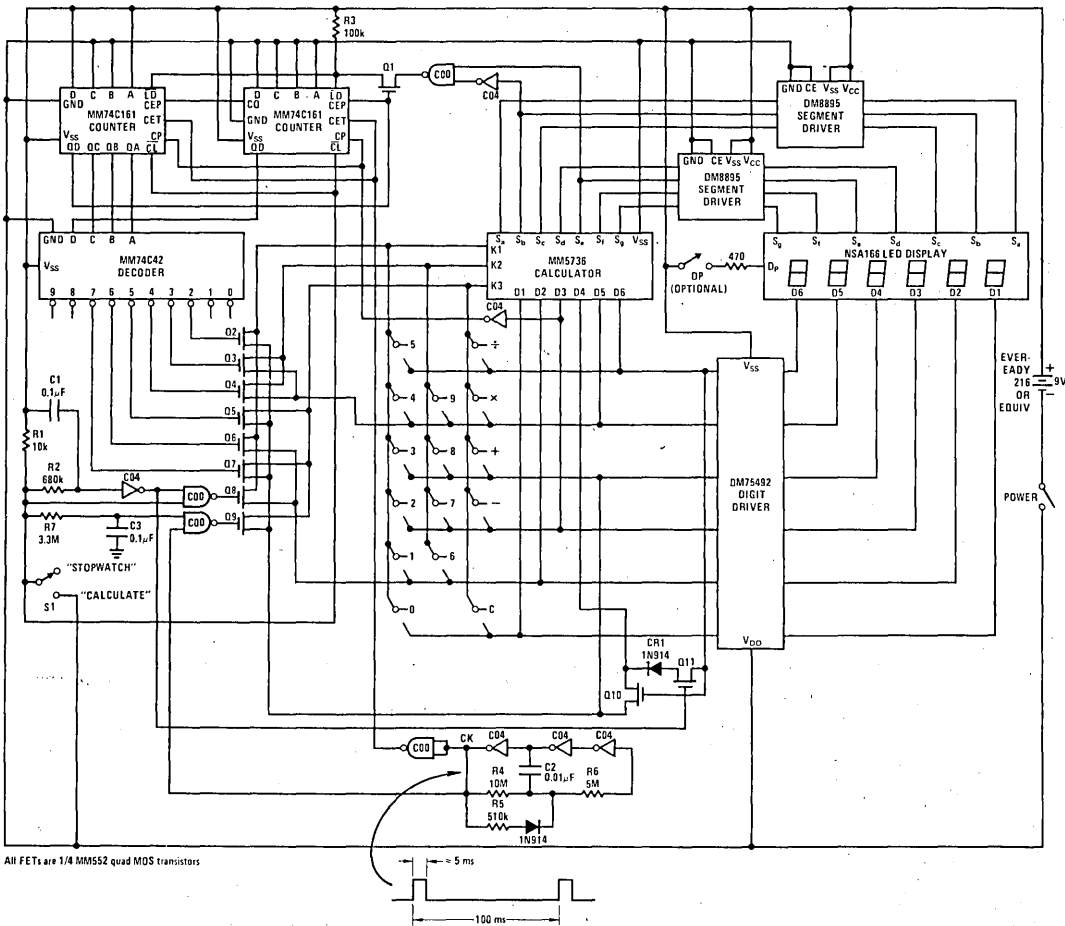1. Reset Latches: The "0" output of the decoder resets the zero decode latch and the buzzer latch.



All FETs are 1/4 MM552 quad MOS transistors

FIGURE 5. 1/10 Second, Seconds, Minutes Stopwatch/Calculator



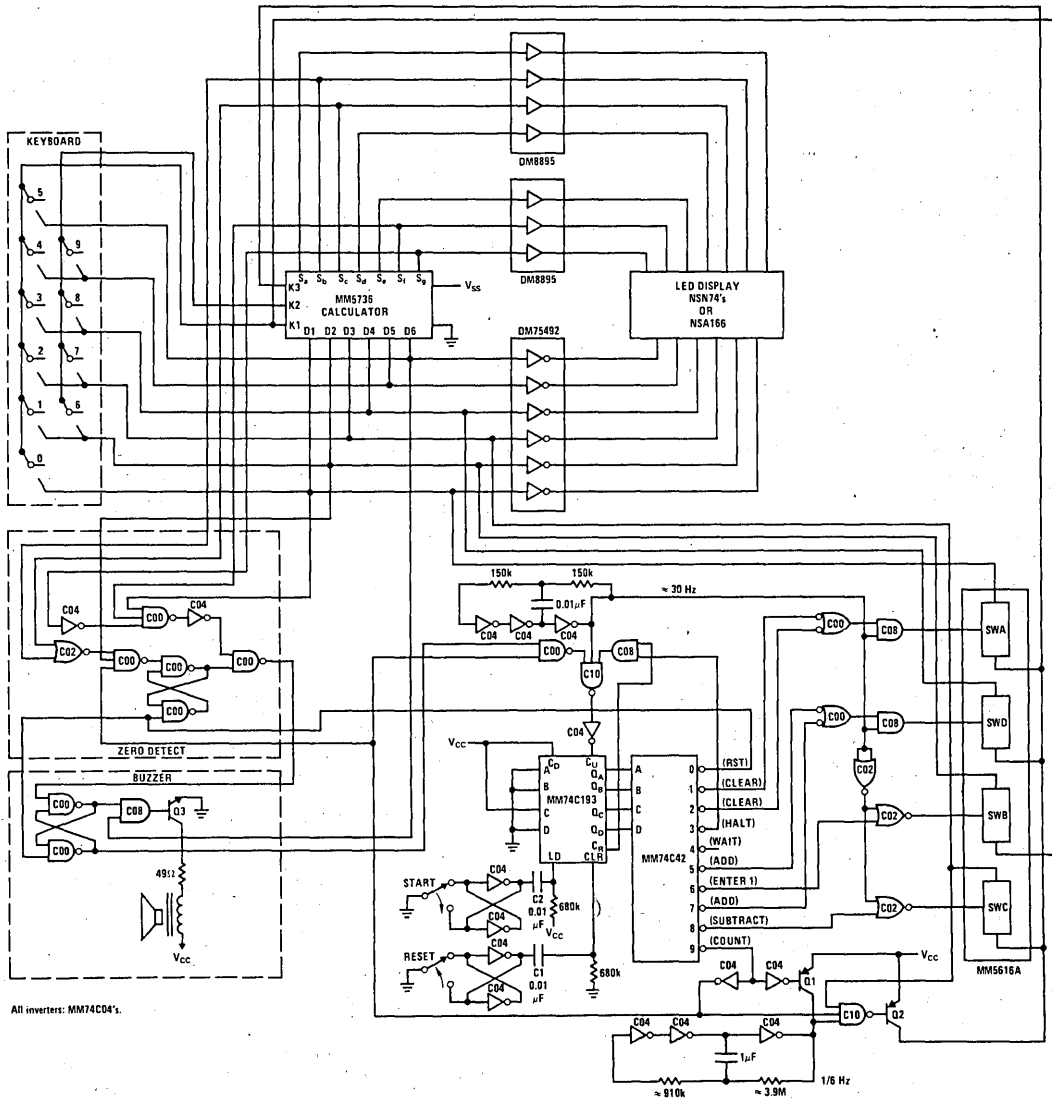


FIGURE 6. Interval Timer

2. Clear Calculator
3. Clear Calculator: Both outputs 1 and 2 of the decoder are "or'ed" and then gated to switch D1 into the K3 input of the Calculator to cause a clear. Two clears are necessary to insure that all registers are reset to zero.
4. Halt: Decoder output 3 forces count enable low and hangs up the counter.

Start Sequence

When the START switch is activated, C2 differentiates the latch output and generates a negative going pulse that loads the counter to state 4. Since this can happen at

any time with respect to the 30 Hz clock, it is necessary to wait until the counter goes to the next count before trying to enter anything into the calculator. This is done to insure that a full cycle of the 30 Hz clock elapses during the time an entry is being made. The sequence then proceeds:

1. Synchronize: Decoder output 4 does nothing but insure that the first application of signals to the calculator will last for a complete interval.
2. Add: Decoder output 5 causes D4 to be gated into input K3 causing an add. This will enter (in normal Polish notation) the number already entered from the keyboard.

3. **Enter 1:** Decoder output 6 gates D2 into K1 to enter a 1. This is the number that will be repeatedly subtracted to make the total count down.
4. **Add:** This simply causes the 1 just entered to be added to the number that was entered from the keyboard. The total will now be one count higher than desired. Since this would shake up most users, the next step corrects this.
5. **Subtract:** Decoder output 8 causes a subtraction which decrements the display by 1 and brings it back to the correct reading.
6. **Count:** Decoder output 9 makes the controller halt and also turns transistor Q1 off. Q1 was initializing the timebase oscillator so the timer won't begin to count down prematurely. D3 is also gated into the base of Q2 which causes repeated subtractions at the timebase rate.

At this point the timer simply chugs away decrementing until it reaches zero. Time remaining to zero is continuously displayed. When zero has been detected, the controller's count enable term will go high and it will advance to state 15 at which time the "carry out" term will go high and inhibit any further counting. It will stay this way until the RESET button is activated.

Zero Decode Logic

A zero is detected by recognizing that a blank exists in digit 2 and a 0 exists in digit 1. A blank is decoded with the expression $S_b + S_c$ since one of these two segments is always on when any number is being displayed. When $BLANK \cdot D2$ exists, a latch is set. Then when a zero is detected in digit 1 according to the expression $S_f \cdot \bar{S}_g$ the buzz latch is set. This gates D6 into the base of Q3 which turns the speaker on at about a 1 kHz rate with a 1/6 duty cycle and generates a buzz. The buzz latch will be reset during the RESET sequence.

OSCILLATORS

Two CMOS oscillators have been mentioned: one RC and one crystal controlled. These oscillators are analyzed elsewhere in National's applications literature (AN-118) so only a summary is given here.

RC Oscillator

An odd number of inverting gates (NAND, NOR, INVERTERS) will always oscillate if tied around on themselves as in *Figure 7*. Most beginning logic designers have discovered this fact of life by accident at one time or another.

 


FIGURE 7. Odd Number of Gates Always Oscillates

Odd Number of Gates Always Oscillates

The oscillator will generate a square wave whose frequency will be determined by the propagation delay through the gates. All that remains to make this a useful

oscillator is to control the frequency of oscillation. *Figure 8* depicts a simple and foolproof way to do this.

 


FIGURE 8. RC-CMOS Oscillator

The frequency of oscillation will be about $f = 0.55/R2 C$ if $R1 = R2$. $R2$ has the most effect on frequency and in most applications it would be a pot. Stability of the oscillator as a function of time is dominated by the passive elements, especially at frequencies as low as 100 Hz or less. Variations in output drive capability of the CMOS will be swamped if $R2$ is 100k or more. Stability with respect to supply voltage in the range of voltages that can be used with the calculator chip (6.5-9.5V) is a function of frequency but the following is representative:

FREQUENCY	VARIATION (6.5-9.5V)
100 Hz	≈ 3%
10 Hz	≈ 0.5%

Empirically determined temperature drift of this oscillator due only to the CMOS is:

FREQUENCY	DRIFT
100 Hz	0.03%/°C (-15 → +50°C)
10 Hz	0.01%/°C

Crystal Oscillator

Figure 9 illustrates how to build a crystal oscillator using CMOS. This oscillator is also described in AN-118.

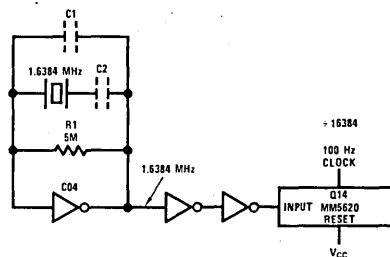


FIGURE 9. CMOS Crystal Oscillator and Divider for 100 Hz

The CMOS inverter is biased into its linear region by resistor R1. This dc path around the inverter ensures that the oscillator will start. C1 can be used to pull the crystal down and C2 to pull it up. The output of the oscillator is cleaned up by the next two inverters. This signal then is divided by 2¹⁴ or 16384 to yield the 100 Hz clock needed for the 0.01 second resolution timers.

The 0.1 second resolution timers could be obtained by using the dividing logic as suggested in *Figures 10 and 11*. The interval timer could use the 0.1 minute time base shown in *Figure 12*.

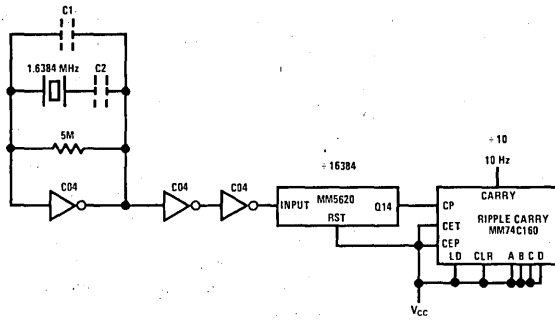


FIGURE 10. Divider for 10 Hz

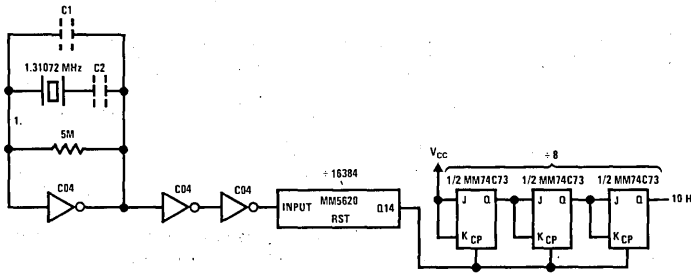


FIGURE 11. Alternate Divider for 10 Hz

 


FIGURE 12. Divider for 1/6 Hz

SUMMARY

A rich variety of timing functions can be done digitally and many of these can be implemented with the MM5736 calculator chip. The MM5736 offers six decades of counting and display in one package and will yield low

parts count solutions to many of these problems. It can be used in a variety of ways, it interfaces ideally with the 74C line of CMOS and consumes little power.