# Modeling and Design of Current Mode Control Boost Converters

### Introduction

This application note presents a detail modeling and design of current mode control boost converters operating in the continuous conduction mode (CCM). Based on the derived small signal models, the design of a lag compensator for current mode control boost converters will be detailed. The LM3478 boost controller will be used in the example. Simulation and hardware measurement of frequency responses will be shown.

# Basic Operation of a Boost Converter



FIGURE 1. An Open Loop Boost Converter

Figure 1 shows an open loop boost converter with an inductor L<sub>1</sub>, a diode D<sub>1</sub>, an output capacitor C<sub>OUT</sub> with an equivalent series resistance R<sub>COUT</sub>. It is assumed that the load is a resistor R<sub>OUT</sub>, and the switch Q<sub>1</sub> is ideal. Let v<sub>IN</sub>, v<sub>OUT</sub>, and v<sub>COUT</sub> be the input voltage, output voltage, and the voltage across C<sub>OUT</sub>, i<sub>L1</sub> be the current through L<sub>1</sub>, and V<sub>D1</sub> be the forward voltage drop of D<sub>1</sub> when D<sub>1</sub> is turned on. Under the CCM, when Q<sub>1</sub> is turned on, the state equations are

$$v_{\rm IN} = L_1 \frac{d}{dt} i_{\rm L1}, \tag{1}$$

$$\frac{v_{OUT}}{R_{OUT}} = -C_{OUT} \frac{d}{dt} v_{COUT}$$
(2)

Also, the output equation is

$$v_{OUT} = v_{COUT} + C_{OUT} \frac{d}{dt} v_{COUT} R_{COUT}$$
 (3)

Similarly, when  $Q_1$  is turned off, the output equation of (3) still holds, while the state equations become

$$v_{\rm IN} = L_1 \frac{d}{dt} i_{\rm L1} + V_{\rm D1} + v_{\rm OUT},$$
 (4)

$$\frac{v_{OUT}}{R_{OUT}} = i_{L1} - C_{OUT} \frac{d}{dt} v_{COUT}$$

National Semiconductor Application Note 1994 L.K.Wong and T.K.Man March 3, 2010



## Modeling of an Open Loop Boost Converter

To obtain a small signal model of boost converters, it is required to apply the averaging technique, perturbation, and the linearization technique. First, by applying the averaging technique, the averaged state equations and output equation are

$$\overline{v}_{IN} = L_1 \frac{d}{dt} \overline{i}_{L1} + (1 - \overline{d}) V_{D1} + (1 - \overline{d}) \overline{v}_{OUT},$$
 (6)

$$\frac{\overline{v}_{OUT}}{R_{OUT}} = (1 - \overline{d})\overline{i}_{L1} - C_{OUT}\frac{d}{dt}\overline{v}_{COUT},$$
(7)

$$\overline{v}_{OUT} = \overline{v}_{COUT} + R_{COUT}C_{OUT} \frac{d}{dt}\overline{v}_{COUT}$$
 (8)

where  $\overline{d}$  is the duty cycle,  $\overline{x}$  is the averaged variable for the variable x (which can represent  $v_{IN}$ ,  $v_{OUT}$ ,  $v_{COUT}$ , and  $i_{L1}$ ). Second, by applying small signal perturbations to (6) to (8), i.e. let

$$\overline{\mathbf{x}} = \overline{\mathbf{X}} + \widetilde{\mathbf{x}},$$

where  $\overline{X}$  and  $\widetilde{X}$  are nominal (DC) and perturbed (AC) variables,

$$\overline{V}_{|N} + \widetilde{v}_{|N} = L_1 \frac{d}{dt} (\overline{I}_{L1} + \widetilde{I}_{L1}) + (1 - \overline{D} - \widetilde{d})V_{D1} + (1 - \overline{D} - \widetilde{d})(\overline{V}_{OUT} + \widetilde{v}_{OUT}),$$
(9)

$$\frac{(\overline{V}_{OUT} + \widetilde{v}_{OUT})}{R_{OUT}} = (1 - \overline{D} - \widetilde{d})(\overline{I}_{L1} + \widetilde{i}_{L1}) - C_{OUT} \frac{d}{dt} (\overline{V}_{COUT} + \widetilde{v}_{COUT}),$$
(10)

$$\overline{V}_{OUT} + \widetilde{v}_{OUT} = \overline{V}_{COUT} + \widetilde{v}_{COUT} + R_{COUT}C_{OUT} \frac{d}{dt}(\overline{V}_{COUT} + \widetilde{v}_{COUT})$$
(11)

Third, by applying the linearization technique (assume that the high order non-linear terms are small and negligible), a set of DC and AC equations can be obtained as follows: DC equations:

From (9)

$$\overline{V}_{IN} = (1 - \overline{D})V_{D1} + (1 - \overline{D})\overline{V}_{OUT}$$
$$\overline{D} = \frac{\overline{V}_{OUT} - \overline{V}_{IN} + V_{D1}}{\overline{V}_{OUT} + V_{D1}}.$$
(12)

Also

$$\overline{V}_{OUT} = \frac{\overline{V}_{IN} - (1 - \overline{D})V_{D1}}{(1 - \overline{D})}$$

For simplicity, consider that  $(1 - \overline{D})V_{D1}$  is small compared with  $\overline{V}_{IN}$ ,

$$\overline{V}_{OUT} = \frac{\overline{V}_{IN}}{(1 - \overline{D})}.$$
(13)

From (10),

(5)

$$\bar{I}_{L1} = \frac{\bar{V}_{OUT}}{(1 - \bar{D})R_{OUT}}.$$
(14)

AC equations: From (9),

$$\begin{split} \widetilde{v}_{\text{IN}} &= \mathrm{sL}_{1} \widetilde{i}_{\text{L}1} + (1 - \overline{D}) \widetilde{v}_{\text{OUT}} - \widetilde{d} \overline{V}_{\text{OUT}} \\ \mathrm{sL}_{1} \widetilde{i}_{\text{L}1} &= \widetilde{v}_{\text{IN}} - (1 - \overline{D}) \widetilde{v}_{\text{OUT}} + \widetilde{d} \overline{V}_{\text{OUT}} \end{split}$$

From (10),

$$\frac{\widetilde{\nu}_{OUT}}{R_{OUT}} = (1 - \overline{D})\widetilde{i}_{L1} - \widetilde{d}\widetilde{i}_{L1} - sC_{OUT}\widetilde{\nu}_{COUT},$$
(16)

From (11),

 $\tilde{v}_{OUT} = \tilde{v}_{COUT} + sR_{COUT}C_{OUT}\tilde{v}_{COUT}$ ,

$$\widetilde{v}_{\text{COUT}} = \frac{\widetilde{v}_{\text{OUT}}}{1 + \text{sR}_{\text{COUT}}C_{\text{OUT}}},$$
(17)

Substitute (13), (14), (15), and (17) into (16),

$$\widetilde{v}_{OUT} = \frac{\frac{(1 + sR_{COUT}C_{OUT})\widetilde{v}_{IN}}{(1 - \overline{D})} + \frac{(1 + sR_{COUT}C_{OUT})\overline{v}_{IN}}{(1 - \overline{D})^2} \left[1 - \frac{sL_1}{R_{OUT}(1 - \overline{D})^2}\right]\widetilde{d}}{1 + s\left[\frac{L_1}{R_{OUT}(1 - \overline{D})^2} + R_{COUT}C_{OUT}\right] + s^2\frac{L_1C_{OUT}(R_{OUT} + R_{COUT})}{R_{OUT}(1 - \overline{D})^2}}\right]}$$
(18)

# Modeling of a Current Mode Control Boost Converter

Under current mode control,  $i_{L1}$  is fed back when  $Q_1$  is turned on to determine the on-time of  $Q_1$  by comparing it to a current control signal  $i_C$ . A compensation ramp of slope  $-m_C$  is normally added to avoid sub-harmonic oscillation. Figure 2 shows the current waveform of an on period. The averaged state equation is as follows:





$$\bar{i}_{L1} = i_{C} - m_{C}\bar{d}T_{SW} - \frac{m_{1}}{2}\bar{d}T_{SW},$$
 (19)

where

(15)

$$m_1 = \frac{v_{IN}}{L_1}$$
(20)

is the slope of  ${\rm i}_{\rm L1}$  during the on period. By adding small signal perturbations to the above equation,

$$\overline{I}_{L1} + \widetilde{I}_{L1} = \overline{I}_{C} + \widetilde{I}_{C} - m_{C}(\overline{D} + \widetilde{d})T_{SW} - \frac{T_{SW}}{2}(\overline{M}_{1} + \widetilde{m}_{1})(\overline{D} + \widetilde{d}).$$
(21)

By applying the linearization technique (assume that the high order non-linear terms are small and negligible), a set of DC and AC equations can be obtained as follows: DC equation:

$$\overline{I}_{L1} = \overline{I}_{C} - m_{C}\overline{D}T_{SW} - \frac{T_{SW}}{2}\overline{M}_{1}\overline{D}$$
(22)

where

 $\overline{M}_1 = \frac{\overline{V}_{IN}}{L_1}$ 

AC eqaution:

$$\widetilde{i}_{L1} = \widetilde{i}_{C} - m_{C}T_{SW}\widetilde{d} - \frac{T_{SW}}{2}\overline{M}_{1}\widetilde{d} - \frac{T_{SW}}{2}\overline{D}\widetilde{m}_{1}$$
(23)

Define

$$T_2 = \frac{T_{SW}}{2},$$
(24)

$$T_{\rm M} = \frac{T_{\rm SW}}{2} (2m_{\rm C} + \overline{\rm M}_1) \tag{25}$$

From (20), (23), (24), (25),

$$\widetilde{i}_{L1} = \widetilde{i}_{C} - T_{M} \widetilde{d} - \widetilde{D} T_{2} \frac{\widetilde{v}_{IN}}{L_{1}}$$
(26)

Substitute (13) into (15),

$$sL_{1}\widetilde{i}_{L1} = \widetilde{v}_{IN} - (1 - \overline{D})\widetilde{v}_{OUT} + \widetilde{d}\frac{\overline{V}_{IN}}{(1 - \overline{D})}.$$
 (27)

Substitute (27) into (26),

$$\widetilde{d} = \frac{sL_{1}\widetilde{i}_{C} + (1 - \overline{D})\widetilde{v}_{OUT} - \left(1 + \frac{sL_{1}DT_{2}}{L_{1}}\right)\widetilde{v}_{IN}}{\left[\frac{\overline{V}_{IN}}{(1 - \overline{D})} + sL_{1}T_{M}\right]}.$$
(28)

By substituting (28) into (18), the small signal model of the current mode control boost converter can be formulated as follows:

$$\widetilde{v}_{OUT} = \frac{G_{NC}(s)\widetilde{v}_{IN} + G_{IC}(s)\widetilde{i}_{C}}{\Delta(s)},$$
(29)

where

$$\begin{split} G_{\text{NC}}(s) &= R_{\text{OUT}}(1-\bar{D})(1+sR_{\text{COUT}}C_{\text{OUT}}) \\ &\left\{ \frac{(1-\bar{D})T_{\text{M}}}{\bar{V}_{\text{IN}}} + \frac{1}{R_{\text{OUT}}(1-\bar{D})^2} - \frac{\bar{D}T_2}{L_1} + \frac{s\bar{D}T_2}{R_{\text{OUT}}(1-\bar{D})^2} \right\} \\ G_{\text{IC}}(s) &= R_{\text{OUT}}(1-\bar{D})(1+sR_{\text{COUT}}C_{\text{OUT}}) \left[ 1 - s\frac{L_1}{R_{\text{OUT}}(1-\bar{D})^2} \right] \\ \Delta(s) &= 2 + R_{\text{OUT}}(1-\bar{D})^2 T_{\text{M}} \frac{(1-\bar{D})}{\bar{V}_{\text{IN}}} \\ &+ s \left\{ \left[ L_1 + R_{\text{COUT}}R_{\text{OUT}}C_{\text{OUT}}(1-D)^2 \right] T_{\text{M}} \frac{(1-\bar{D})}{\bar{V}_{\text{IN}}} + (R_{\text{OUT}} + 2R_{\text{COUT}})C_{\text{OUT}} \right\} \right. \end{split}$$

If the current  $i_{L1}$  is sensed by a resistor  $R_{SN}$  connecting between  $Q_1$  and the ground, the current control signal  $i_C$  can be converted to a voltage control signal  $v_C$ . The relationship between the output voltage and the voltage control signal can be formulated as follows:

$$\widetilde{v}_{OUT} = \frac{G_{IC}(s)}{\Delta(s)R_{SN}} \, \widetilde{v}_{C}, \tag{30}$$

### Principle Of a Lag Compensator



FIGURE 3. Frequency Response of a Lag Compensator

A lag compensator consists of a pair of pole and zero at the frequency  $f_{PC}$  and  $f_{ZC}$ , with  $f_{PC} < f_{ZC}$ . It also provides a dc gain A<sub>C</sub>. As shown in Figure 3, the lag compensator provides an attenuation in magnitude at the high frequency. The degree of attenuation is determined by the distance between  $f_{PC}$  and  $f_{ZC}$ . It is because the magnitude is decreased at a slope of 20dB/decade between  $f_{PC}$  and  $f_{ZC}$ . The lag compensator also provides a phase lag. However,  $f_{PC}$  and  $f_{ZC}$  can be placed at a low frequency (much lower than the frequency of interest, e.g. the cross over frequency  $f_C$ ) such that the lag compensator nearly does not affect the phase at the high frequency.

The aim of designing a lag compensator is to provide a desired phase margin for the compensated system. Starting from a bode plot of an un-compensated system, and a requirement of phase margin of  $\Phi_m$ , a new  $f_C$  can be selected at the frequency corresponding to  $180^\circ - \Phi_m$  of the un-compensated system. Then the magnitude of the un-compensated system at  $f_C$  is found. The magnitude at  $f_C$  can be attenuated to 0dB by the lag compensator through proper design of  $f_{PC}$  and  $f_{ZC}$ . As a result, the compensated system will have a phase margin of  $\Phi_m$ , and the cross over frequency will be  $f_C$ . An illustrative example will be presented to show the design steps.



#### FIGURE 4. A Lag Compensator Implemented by a Transconductance Amplifier Circuit

A lag compensator can be implemented by a transconductance amplifier, with an open loop gain of gm and an output impedance of R<sub>0</sub>, connecting to a resistor R<sub>C1</sub> and a capacitor C<sub>C1</sub> in series to the ground, as shown in Figure 4. Let the negative input of the amplifier is connected to a reference voltage V<sub>REF</sub>, and the positive input is connected to the output voltage v<sub>OUT</sub> through a resistor divider network implemented by R<sub>F1</sub> and R<sub>F2</sub>, the transfer function relating v<sub>C</sub> and v<sub>OUT</sub> is

$$v_{C} = \left(\frac{R_{F2}}{R_{F1} + R_{F2}} v_{OUT} - V_{REF}\right) g_{m} \left[R_{0} / \left(R_{C1} + \frac{1}{SC_{C1}}\right)\right]_{(31)}$$

By adding small signal perturbations, the AC equation can be obtained as follows:

$$\widetilde{v}_{C} = \frac{R_{F2}}{R_{F1} + R_{F2}} g_{m} R_{0} \frac{1 + sR_{C1}C_{C1}}{1 + s(R_{C1} + R_{0})C_{C1}} \widetilde{v}_{OUT}.$$
(32)

Hence,

$$\begin{split} A_{C} &= \frac{R_{F2}}{R_{F1} + R_{F2}} \, g_{m} R_{0}, \\ f_{PC} &= \frac{1}{2\pi (R_{C1} + R_{0}) C_{C1}}, \\ f_{ZC} &= \frac{1}{2\pi R_{C1} C_{C1}}. \end{split}$$

## **Illustrative Example**

The design of a current mode control Boost converter with a nominal input voltage of 5V and an output voltage of 12V and an output current of 0.5A will be shown. The major components are listed in table 1. A current mode controller LM3478 will be used. The parameters of the LM3478, which can be derived from the datasheet, are also listed in table 2.

#### TABLE 1. Major Parameters of the Example Boost Converter

Parameter	Value	
$\overline{V}_{IN}$	5V	
 ∇ <sub>OUT</sub>	12V	
R <sub>OUT</sub>	24Ω	
L <sub>1</sub>	10 µH	
C <sub>OUT</sub>	150 µF	
R <sub>COUT</sub>	0.05Ω	
f <sub>sw</sub>	400 kHz	
R <sub>SN</sub>	0.05Ω	
R <sub>SL</sub>	604Ω	

#### TABLE 2. Parameters of the LM3478

Parameter	Value	
V <sub>REF</sub>	1.26V	
9 <sub>m</sub>	800 μΩ <sup>-1</sup>	
R <sub>0</sub>	$A_V/g_m = 38/800 \ \mu\Omega^{-1}$	
	= 47.5 kΩ	
V <sub>SL</sub>	92 mV	

Other parameters of (30) are calculated below. From (13),

From (24),

$$\mathsf{T}_2 = \frac{\mathsf{T}_{\mathrm{SW}}}{2} = \frac{1}{2\mathsf{f}_{\mathrm{SW}}}$$

T<sub>2</sub> = 1.25 μs

The parameter  $m_C$  is determined by an internal compensation ramp  $V_{SL}$  and an external compensation ramp determined by an internal current of 40  $\mu A$  passing through an external resistor  $R_{SL}$ . It can be calculated by the following equation:

 $m_{C} = (V_{SL} + 40 \ \mu A \ x \ R_{SL}) f_{SW} / R_{SN} = 929280 A s^{-1} \label{eq:mc}$  From (25),

$$T_{\rm M} = \frac{T_{\rm SW}}{2} \left( 2m_{\rm C} + \frac{\overline{V}_{\rm IN}}{L_1} \right)$$
$$= 2.9482A$$

Hence, all parameters of (30) are obtained. A bode plot of (30) with the above parameters is shown in Figure 5. The DC gain, zeros, and poles are

DC gain: 36.39dB Zeros: 53 kHz, 66 kHz (right half plane zero) Poles: 133 Hz, 65 kHz



#### FIGURE 5. Frequency Response of the Un-Compensated System

The design of the lag compensator can be achieved by following (32). Since  $\overline{V}_{OUT}$  and  $V_{REF}$  are 12V and 1.26V respectively, we can design that

 $R_{F1} = 84.5 \text{ k}\Omega$ 

 $R_{F2} = 10 \text{ k}\Omega$ 

From (32),

 $A_{C} = \frac{R_{F2}}{R_{F1} + R_{F2}} g_{m} R_{0}$ = 4.02 = 12.09 dB

In this example, a compensated system with a phase margin of around 90° is desired. From Figure 5,  $f_C$  can be selected as 3.5kHz (the frequency at which the phase is around 180° - 90° = 90°). The attenuation required is 7dB +  $A_C$  = 19.09dB, which implies that the distance between  $f_{PC}$  and  $f_{ZC}$  should be 0.96 decade. Select  $f_{ZC}$  to be 350 Hz, i.e. one decade lower than  $f_C$ , then  $f_{PC}$  should be 38.3 Hz.

$$I/R_{C1}C_{C1} = 2\pi x 350 Hz$$





Finally, select  $R_{C1} = 5.9 \text{ k}\Omega$  and  $C_{C1} = 100 \text{ nF}$ . The frequency response of the compensated system is shown in Figure 6. It can be found that the 0dB point is at around 4 kHz, and the phase margin is around 95°.

## Conclusion

This application note details the modeling of an open loop and a current mode control boost converter under the continuous conduction mode. The principle and design of a lag compensator have also been addressed. An example has been presented to illustrate the design. A lag compensator has been designed for a compensated system with around 90° phase margin.

The selection of a desired phase margin affects the transient response of the output voltage. Moreover, some practical systems are suffered from noise, and transient responses are not a major concern. A lower cross over frequency may be required. In this case, the application of the dominant pole compensation method may be more appropriate. The lag compensator can be easily changed to a compensator with a dominant pole by setting  $R_{C1}$  to zero, i.e. to eliminate the zero. Application engineers are suggested to design properly based on practical situations.

# Notes

For more National Semiconductor product information and proven design tools, visit the following Web sites at: www.national.com

Products		Design Support	
Amplifiers	www.national.com/amplifiers	WEBENCH® Tools	www.national.com/webench
Audio	www.national.com/audio	App Notes	www.national.com/appnotes
Clock and Timing	www.national.com/timing	Reference Designs	www.national.com/refdesigns
Data Converters	www.national.com/adc	Samples	www.national.com/samples
Interface	www.national.com/interface	Eval Boards	www.national.com/evalboards
LVDS	www.national.com/lvds	Packaging	www.national.com/packaging
Power Management	www.national.com/power	Green Compliance	www.national.com/quality/green
Switching Regulators	www.national.com/switchers	Distributors	www.national.com/contacts
LDOs	www.national.com/ldo	Quality and Reliability	www.national.com/quality
LED Lighting	www.national.com/led	Feedback/Support	www.national.com/feedback
Voltage References	www.national.com/vref	Design Made Easy	www.national.com/easy
PowerWise® Solutions	www.national.com/powerwise	Applications & Markets	www.national.com/solutions
Serial Digital Interface (SDI)	www.national.com/sdi	Mil/Aero	www.national.com/milaero
Temperature Sensors	www.national.com/tempsensors	SolarMagic™	www.national.com/solarmagic
PLL/VCO	www.national.com/wireless	PowerWise® Design University	www.national.com/training

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

#### LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

#### Copyright© 2010 National Semiconductor Corporation

For the most current product information visit us at www.national.com



National Semiconductor Americas Technical Support Center Email: support@nsc.com Tel: 1-800-272-9959

National Semiconductor Europe Technical Support Center Email: europe.support@nsc.com National Semiconductor Asia Pacific Technical Support Center Email: ap.support@nsc.com National Semiconductor Japan Technical Support Center Email: jpn.feedback@nsc.com