# Noise, TDMA Noise, and Suppression Techniques

#### Noise and TDMA Noise

The term "noise" is often and loosely used to describe unwanted electrical signals that distort the purity of the desired signal. Some forms of noise are unavoidable (e.g., real fluctuations in the quantity being measured), and they can be overcome only with the techniques of signal averaging and bandwidth narrowing. Other forms of noise (e.g., radio frequency interference and "ground loops") can be reduced or eliminated by a variety of techniques, including filtering and careful attention to wiring configuration and parts location. Finally, there is noise that arises in signal amplification and it can be reduced through the techniques of low-noise amplifier design. Although noise reduction techniques can be effective, it always pays to begin with a system that is free of preventable interference and that possesses the lowest amplifier noise possible<sup>1</sup>. What follows is a brief summary of different kinds of noise afflicting electronic circuits.

Thermal Noise (or Johnson Noise or White Noise) is directly related to temperature manifested by the thermal agitation of electrons in resistors. In the case of loudspeakers and microphones, the source of noise is the thermal motion of the air molecules<sup>2</sup>.

Shot Noise is generated due to random fluctuation in the number of charged carriers when emitted from a surface or diffused from a junction. This noise is always associated with a direct current flow, independent of temperature, and is present in bipolar transistors<sup>2</sup>.

Flicker Noise (or 1/f Noise or Pink Noise) is caused mainly by traps associated with contamination and crystal defects.

National Semiconductor Application Note 1496 Allan Soriano April 28, 2008



These traps capture and release carriers in a random fashion and the time constants associated with the process give rise to a noise signal with energy concentrated at low frequencies<sup>3</sup>.

Burst Noise (Popcorn Noise) is generated by the presence of heavy metal ion contamination and is found in some integrated circuits and discrete transistors. With some bipolar integrated circuits, the popcorn noise was a result of too much doping of the emitter. Reducing the doping level made it possible to eliminate the popcorn noise test completely. This is another type of low-frequency noise<sup>3</sup>.

Avalanche Noise is a form of noise produced by Zener or avalanche breakdown in a pn junction. In avalanche breakdown, holes and electrons in the depletion region of a reversebiased pn junction acquire sufficient energy to create holeelectron pairs by colliding with silicon atoms<sup>3</sup>.

TDMA Noise ("buzz") in GSM mobile phones is generated from a 217Hz waveform which produces an audible noise when coupled into the audio path and conducts to the speaker, earpiece, or microphone<sup>4</sup>. Further details of this type of noise will follow.

This application note will specifically address the problem of TDMA Noise customers have encountered while driving mono speakers in their GSM phone designs. Before delving into solutions that minimize this problem, some background describing the operations of a bridge-tied load (BTL) mono amplifier will be reviewed. In the following applicable figures, all resistors are of equal value, R (Figure 1).



FIGURE 1. Bridge-Tied Load Mono Amplifier

AN-1496

AN-1496

In this configuration (Figure 1), an input signal  $V_{\rm IN}$  is applied to the inverting input terminal of amplifier A1and passes through with a gain of 0dB. The output of A1 is connected to one side of the loudspeaker and the inverting terminal of amplifier A2, which is also at a gain of 0dB. The output of A2 is connected to the other side of the loudspeaker. Since the output of A2 is 180° out of phase with the output of A1, the

resulting difference between A1 and A2, VOUT, has twice the magnitude of the individual amplifier outputs. When compared to a single-ended amplifier and a given sinusoidal input signal, this BTL configuration effectively doubles the output voltage and quadruples the output power with the same load (Figure 2).



FIGURE 2. Bridge-Tied Load Output Voltage

As GSM phone manufacturers have discovered, the BTL mono configuration can be susceptible to radio frequency interference (RFI). Such unwanted signals are directly coupled into the audio path, distort the desired waveform, and may be audible as a "buzz", known as TDMA Noise. GSM cell phones use a TDMA (time-division multiple-access) time-slot sharing technique that results in high-power RF in the 800MHz to 900MHz or 1800MHz to 1900MHz bands. The transmitter current, which can exceed 1A, pulses during a phone call at a repetition rate of 217Hz and pulse width of about 0.5ms. If current pulses couple to the audio circuitry, the harmonic-rich 217Hz signal results in the audible buzz<sup>4</sup>.

What is causing the audible buzz? Energy in the audio frequency range, including the 217Hz TDMA pulse-repetition rate and its harmonics, exists in the phone in two forms: as variations in the DC supply current and as the RF signal's modulation envelope. The DC supply current pulse waveform comes from the large current that the RF power amplifier draws during transmission time slots and the smaller current that the RF circuitry draws during the receive interval (Figure 3).



FIGURE 3. Periodic Transmitting and Receiving Current Pulse Waveform

The two primary mechanisms for coupling the current waveform into the audio circuits are supply and ground ripple, both at the 217Hz. Additionally, a portion of the transmitted RF energy can couple in the audio circuits<sup>4</sup>.

AN-1496



FIGURE 4. RF Energy Coupling into the Audio Circuitry

The potential for RF energy coupling into the audio circuit is most likely when there are long traces connecting the amplifier outputs to the loudspeaker, thereby acting as antennas. Good layout must also prevent RF energy from coupling into the audio and power traces that serve the baseband section or audio circuits within the phone. The design of these subsystems must block or bypass RF to ground so that it is not conducted to the semiconductor junctions of active audio components. RF energy can get from the RF circuitry to the audio circuitry through a variety of paths<sup>4</sup>:

• Radiation from the antenna to the audio or voltage supply components or to traces or components connected to them

Conduction from RF components through traces to the audio components

· Conduction through ground to the audio subsystem

• Trace-to-trace coupling between lines or from a line to ground on the same or adjacent layers

 Coupling from line to component or component to component

Prevention methods include shielding, ground design, and careful overall layout practice. Some preventive measures are as follows:

 Shield the audio section and its associated power-management ment and baseband sections to isolate them from stray RF. Shield the RF section to minimize the stray energy.

• Terminate the shield on a solid ground that is free of high dynamic currents.

• Isolate solid, largely unbroken audio ground on the layer below the audio sections from pulsing current.

• Do not allow traces onto same layer to bisect ground.

• Connect components to the ground layer through multiple vias.

• Do not route traces carrying power or audio signals parallel to those containing RF or large dynamic supply currents.

Maximize the spacing between sensitive traces and potential sources of interference.

• For traces that must maintain perpendicular or (90°) design to minimize any noise coupling.

• Isolate audio traces on inner layers from non-audio traces by a ground trace with enough via holes to act as a Faraday shield.

• Do not place traces containing RF or dynamic DC currents directly under audio components.

Place audio-feedback and signal-path components as close as possible to audio amplifiers, and isolate components from RF energy sources<sup>4</sup>.

Some RF energy will couple onto audio traces regardless of the effort to prevent this phenomenon from occurring. Utilizing bypass capacitors to ground to create single-pole low-pass filters will attenuate this energy from conducting into the audio amplifiers' semiconductor junctions. Small value capacitors must be used to bypass RF energy and not affect audio signals. Since GSM phone bands approximately inhabit the 900MHz and 1800MHz range, the best capacitors are those that are self-resonant at the aforementioned frequencies; typical capacitors of 10pF to 39pF have negligible effect on audio signals. Use each capacitor to shunt RF energy operating at each audio amplifier input, output, or power pin that is sensitive to RF energy. For further isolation, add an inductor (or ferrite bead; the ferrite bead is a combined inductor and resistor) to form a two-pole low-pass filter, placing the components as close to the amplifier outputs as physically possible<sup>4</sup>. Figure 5 shows an actual application at the mono output of the LM4845. Experiencing an audio buzz at the mono loudspeaker, a customer implemented a two-pole lowpass filter with a -3dB cutoff frequency of 1MHz, well above the audio range and well below the GSM frequency bands. The audio buzz was attenuated by 30dB, an acceptable audible level to the customer.



FIGURE 5. External Two-pole Low-pass Filter Isolating the Amplifier Outputs

Although one GSM cell phone manufacturer experienced TD-MA noise while using the LM4845, other customers did not. After troubleshooting the customer's circuit, it was determined that poor part placement and poor layout was responsible for the audio buzz. To minimize noise susceptibility and aid system designers, the LM4845 was redesigned with differential mono inputs and a proprietary RF suppression circuit at the outputs of the amplifiers. This improved part is the LM4946.. Figure 6 shows a comparison of the LM4845 and LM4946 under identical conditions. Without the RF suppression circuitry, RF energy is propagated in the LM4845 and coupled into the audio path, with the 217Hz TDMA-pulse repetition carried on the RF modulation envelope. Although the same 217Hz TDMA-pulse repetition is still present in the LM4946, the RF suppression circuitry attenuates the RF energy 20dB to 30dB. Figure 6 also shows the modulation envelope in the LM4946 substantially attenuated.



**FIGURE 6. Measured TDMA Noise** 

To date, only the LM4884 and LM4946 contain the proprietary RF suppression circuits but further products are under development with this technology.

### Conclusion

As the old adage goes, "an ounce of prevention is worth a pound of cure"; the same philosophy can be applied to GSM phone design. Trying to suppress TDMA noise after the design is costly, time consuming, and frustrating. Good prevention techniques must occur prior to the actual board layout: component placement, power supply trace locations, ground trace locations, shielding, and many more prevention techniques previously listed. The LM4946, LM4884, and future products with RF suppression can substantially minimize TD-MA noise problems, but no single solution can prevent TDMA noise from occurring.

Note: In this application note the terms "TDMA noise", "RF energy", "audio buzz", and "buzz" are used interchangeably.

#### References

1. P. Horowitz, W. Winfield. The Art of Electronics, Cambridge University Press, New York, 1999, Chapter 7

2. M. Rashid. SPICE For Circuits And Electronics Using PSpice, Prentice Hall, New Jersey, 1990, Appendix B

3. P. Gray, P. Hurst, S. Lewis, and R. Meyer. Analysis and Design of Analog Integrated Circuits, John Wiley & Sons, New York, 2001, Chapter 11

4. B. Poole. "Reducing Audio 'Buzz' in GSM Cell Phones", EDN, pp. 67 – 70, February 2005

AN-1496

## **Revision Table**

Rev	Date	Description	
1.0	05/24/06	Initial release.	
1.1	10/01/07	Corrected a misspelled word.	
1.2	04/28/08	Edited graphics 20197019, 20, and 21.	

Pr	oducts	Design Support	
Amplifiers	www.national.com/amplifiers	WEBENCH	www.national.com/webench
Audio	www.national.com/audio	Analog University	www.national.com/AU
Clock Conditioners	www.national.com/timing	App Notes	www.national.com/appnotes
Data Converters	www.national.com/adc	Distributors	www.national.com/contacts
Displays	www.national.com/displays	Green Compliance	www.national.com/quality/green
Ethernet	www.national.com/ethernet	Packaging	www.national.com/packaging
Interface	www.national.com/interface	Quality and Reliability	www.national.com/quality
LVDS	www.national.com/lvds	Reference Designs	www.national.com/refdesigns
Power Management	www.national.com/power	Feedback	www.national.com/feedback
Switching Regulators	www.national.com/switchers		
LDOs	www.national.com/ldo		
LED Lighting	www.national.com/led		
PowerWise	www.national.com/powerwise		
Serial Digital Interface (SDI)	www.national.com/sdi		
Temperature Sensors	www.national.com/tempsensors		
Wireless (PLL/VCO)	www.national.com/wireless		

For more National Semiconductor product information and proven design tools, visit the following Web sites at:

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

#### LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

Copyright© 2008 National Semiconductor Corporation

For the most current product information visit us at www.national.com



AN-1496

Americas Technical Support Center Email: new.feedback@nsc.com Tel: 1-800-272-9959

National Semiconductor

National Semiconductor Europe Technical Support Center Email: europe.support@nsc.com German Tei: +49 (0) 180 5010 771 English Tel: +44 (0) 870 850 4288 National Semiconductor Asia Pacific Technical Support Center Email: ap.support@nsc.com National Semiconductor Japan Technical Support Center Email: jpn.feedback@nsc.com