

# LME49721 Evaluation Board

National Semiconductor  
Application Note 1767  
Gerardine Salazar  
February 22, 2008



## Introduction

This application note provides information on how to use the LME49721 demonstration board for evaluation of the LME49721 Rail-to-Rail Input/Output, high performance, high fidelity operational amplifier. The LME49721 demonstration board is designed for the user to fully evaluate the LME49721 in either inverting, non-inverting, or unity gain voltage follower configuration. This board is shown in Figure 1.

## General Description


The LME49721 is a low distortion (THD+N = 0.00008%,  $A_V = 2$ ,  $V_{OUT} = 4V_{P-P}$ ,  $f_{IN} = 1kHz$ ), low noise (4nV/ $\sqrt{Hz}$ ) Rail-to-Rail Input/Output operational amplifier optimized and fully speci-

fied for high performance, high fidelity applications. The Rail-to-Rail Input/Output operational amplifier delivers superior signal amplification for outstanding performance. The LME49721 has a slew rate of  $\pm 8.5V/\mu s$ , an output current capability of  $\pm 9.7mA$ , and an input bias current of 40fA. This operational amplifier can easily drive 10k $\Omega$  loads to within 10mV of each power supply voltage.

## Operating Conditions

The LME49721 has a supply voltage range from +2.2V to +5.5V single supply or  $\pm 1.1V$  to  $\pm 2.75V$  dual supply. Please note the demonstration board is designed for dual supply operation only.

## Demonstration Board Schematic

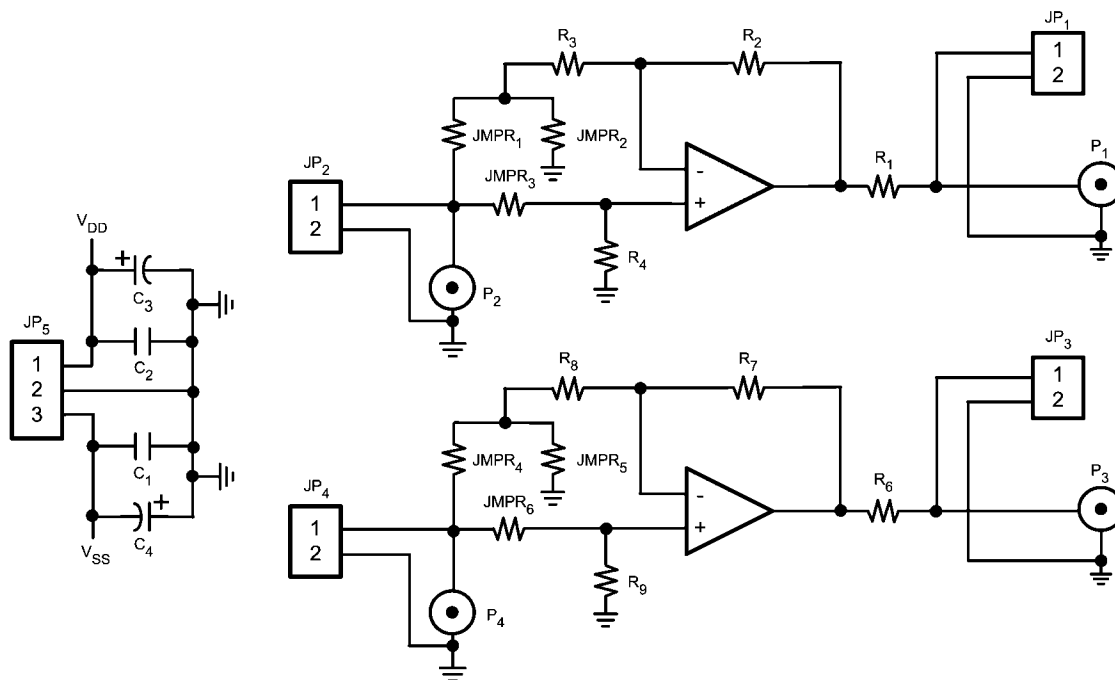

30047120

FIGURE 1. LME49721 Demo Board Schematic

TABLE 1. Demo Board Connections


Designator	Label	Function
JP1	OUT_1	Output Signal A
JP2	IN_1	Input Signal A
JP3	OUT_2	Output Signal B
JP4	IN_2	Input Signal B
JP5	+V <sub>DD</sub> GND -V <sub>SS</sub>	Power Supply Connections
P1	OUT_1	Output Signal A
P2	IN_1	Input Signal A
P3	OUT_2	Output Signal B
P4	IN_2	Input Signal B

## Configuring the LME49721 Amplifier

$R_2/R_3$ . Table 2 shows the recommended Build of Materials for an inverting amplifier.

### INVERTING CONFIGURATION

Figure 2 shows the typical connection for a inverting amplifier. The output voltage is centered on zero with a gain of  $A_V = -$

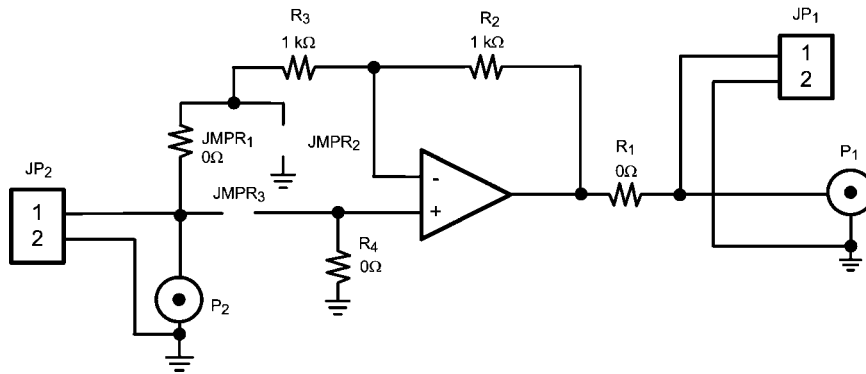

30047121

**FIGURE 2. Inverting Amplifier**

The user configure the LME49721 demonstration board in an inverting configuration by making the following changes:

Place 0Ω resistor (or short) JMPR<sub>1</sub> (JMPR<sub>4</sub>)

Place 0Ω resistor (or short) R<sub>4</sub> (R<sub>9</sub>)

Place the desired value resistor (1kΩ minimum) to set the inverting gain in R<sub>3</sub>(R<sub>8</sub>) and R<sub>2</sub>(R<sub>7</sub>)

Leave the JMPR<sub>2</sub> (JMPR<sub>5</sub>) and JMPR<sub>3</sub> (JMPR<sub>6</sub>) open

Place 0Ω resistor (or short) R<sub>1</sub> (R<sub>6</sub>)


**TABLE 2. Example Demonstration Board Build of Materials for Inverting Configuration**

Description	Designator	Part Number	Mfg.
Ceramic Capacitor 0.1μF, 10% 50V 0805 SMD	C1, C2	C0805C104K3RAC7533	Kemet
Tantalum Capacitor 10μF, 10% 20V, B-size	C3, C4	T491B106K025AT	Kemet
Resistor 0 Ω, 1/8W 1% 0805 SMD	JMPR <sub>1</sub> , JMPR <sub>4</sub> , R <sub>1</sub> , R <sub>4</sub> , R <sub>6</sub> , R <sub>9</sub>	CRCW0805000020EA	Vishay
Resistor 10kΩ, 1/8W, 1% 0805 SMD	R <sub>2</sub> , R <sub>3</sub> , R <sub>8</sub> , R <sub>7</sub>	CRCW080510KOFKEA	Vishay
Header, 2–Pin	JP <sub>1</sub> , JP <sub>2</sub> , JP <sub>3</sub> , JP <sub>4</sub>		
Header, 3–Pin	JP <sub>5</sub>		
SMA standup connectors	P1–P4 (Optional)	132134	Amphenol Connex

### NON-INVERTING CONFIGURATION

Figure 3 shows the typical connection for a non-inverting amplifier. Again the output voltage is centered on zero but with

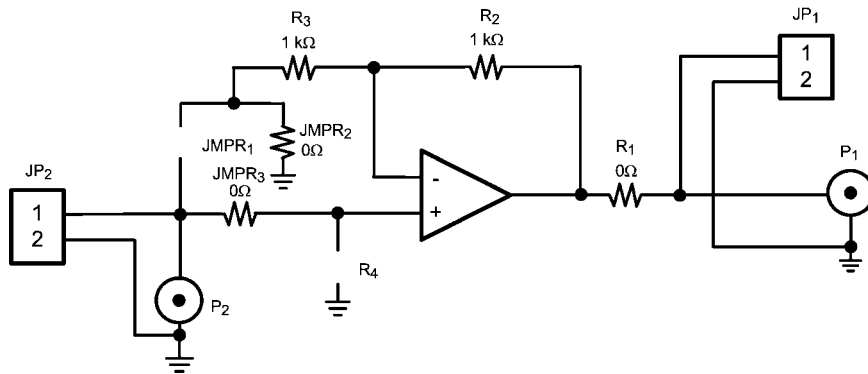a gain of  $A_V = 1 + (R_2/R_3)$ . Table 3 shows the recommended Build of Materials for a non-inverting amplifier.



30047122

FIGURE 3. Non-Inverting Amplifier

The user configure the LME49721 demonstration board in Non-Inverting configuration by making the following changes:

Place 0Ω resistor (or short) Jmpr<sub>2</sub> (Jmpr<sub>5</sub>) and Jmpr<sub>3</sub> (Jmpr<sub>6</sub>)

Place the desired value resistors (1kΩ minimum) to set inverting gain in R<sub>3</sub>(R<sub>8</sub>) and R<sub>2</sub>(R<sub>7</sub>)

Leave the Jmpr<sub>1</sub> (Jmpr<sub>4</sub>) and R<sub>4</sub> (R<sub>9</sub>) open  
Place 0Ω resistor (or short) R<sub>1</sub> (R<sub>6</sub>)


TABLE 3. Example Demonstration Board Build of Materials for Non-Inverting Configuration

Description	Designator	Part Number	Mfg.
Ceramic Capacitor 0.1μF, 10% 50V 0805 SMD	C1, C2	C0805C104K3RAC7533	Kemet
Tantalum Capacitor 10μF, 10% 20V, B-size	C3, C4	T491B106K025AT	Kemet
Resistor 0 Ω, 1/8W 1% 0805 SMD	Jmpr <sub>2</sub> , Jmpr <sub>3</sub> , Jmpr <sub>5</sub> , Jmpr <sub>6</sub> , R <sub>1</sub> , R <sub>6</sub>	CRCW0805000020EA	Vishay
Resistor 10kΩ, 1/8W, 1% 0805 SMD	R <sub>2</sub> , R <sub>3</sub> , R <sub>7</sub> , R <sub>8</sub>	CRCW080510KOFKEA	Vishay
Header, 2–Pin	JP <sub>1</sub> , JP <sub>2</sub> , JP <sub>3</sub> , JP <sub>4</sub>		
Header, 3–Pin	JP <sub>5</sub>		
SMA standup connectors	P1–P4 (Optional)	132134	Amphenol Connex

VOLTAGE FOLLOWER CONFIGURATION

Figure 4 shows the typical connection for a Voltage Follower amplifier or also called a Buffer. A Voltage Follower Amplifier can be used to solve impedance matching problems, to reduce power consumption in the source, or to drive heavy

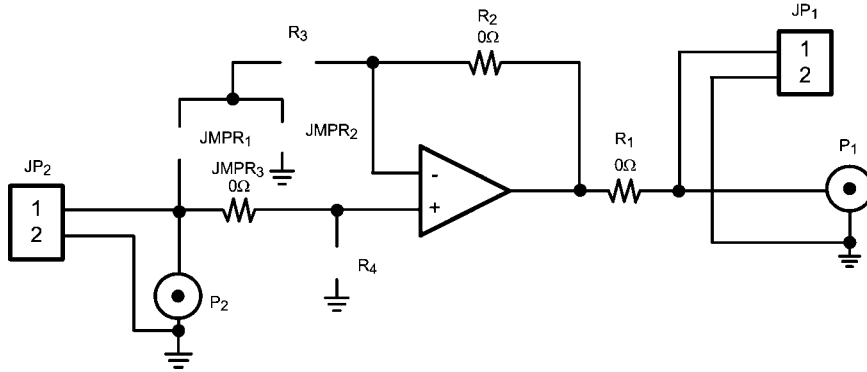loads. The input impedance of the LME49721 is very high. Therefore, the input of the LME49721 does not load down the source. The Voltage Follower is a unity stable amplifier, 1V/V. Table 4 shows the recommended Build of Materials for an inverting amplifier.



30047123

**FIGURE 4. Voltage Follower Amplifier**

The user configure the LME49721 demonstration board in a Voltage Follower configuration by making the following changes:

Place 0Ω resistor (or short) R<sub>2</sub> (R<sub>7</sub>) and R<sub>1</sub> (R<sub>6</sub>)

Place 0Ω resistor (or short) JMPR<sub>3</sub> (JMPR<sub>6</sub>)


Leave R<sub>3</sub>(R<sub>8</sub>) and R<sub>4</sub>(R<sub>9</sub>) open

Leave JMPR<sub>1</sub>(JMPR<sub>4</sub>) and JMPR<sub>2</sub>(JMPR<sub>5</sub>) open

**TABLE 4. Example Demonstration Board Build of Materials for Voltage Follower Configuration**


Description	Designator	Part Number	Mfg.
Ceramic Capacitor 0.1μF, 10% 50V 0805 SMD	C1, C2	C0805C104K3RAC7533	Kemet
Tantalum Capacitor 10μF, 10% 20V, B-size	C3, C4	T491B106K025AT	Kemet
Resistor 0 Ω, 1/8W 1% 0805 SMD	JMPR <sub>3</sub> , JMPR <sub>6</sub> , R <sub>1</sub> , R <sub>2</sub> , R <sub>6</sub> , R <sub>7</sub>	CRCW0805000020EA	Vishay
Header, 2-Pin	JP <sub>1</sub> , JP <sub>2</sub> , JP <sub>3</sub> , JP <sub>4</sub>		
Header, 3-Pin	JP <sub>5</sub>		
SMA standup connectors	P1–P4 (Optional)	132134	Amphenol Connex

## Demonstration Board Layout

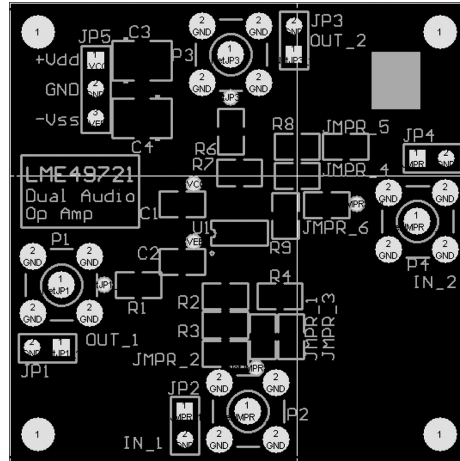


30047118

Top Silkscreen

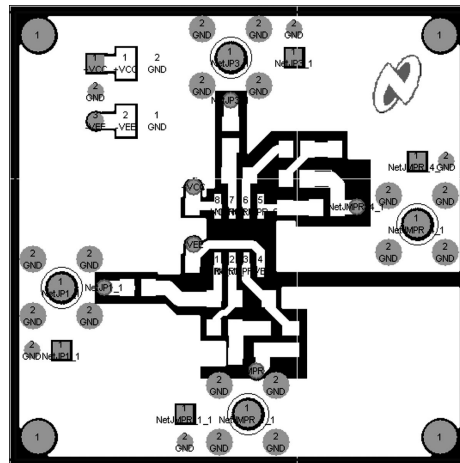

30047119


Top Layer

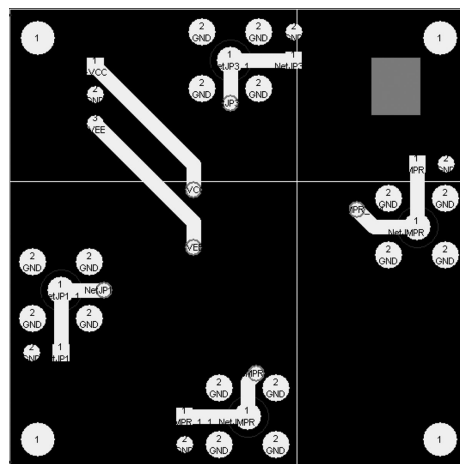


30047117

Bottom Layer


# Typical Performance Characteristics

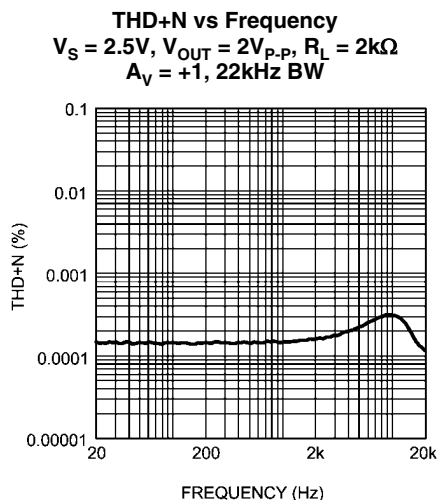


30047124

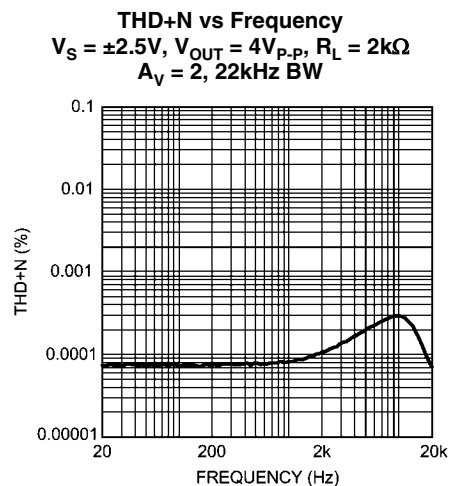


30047134

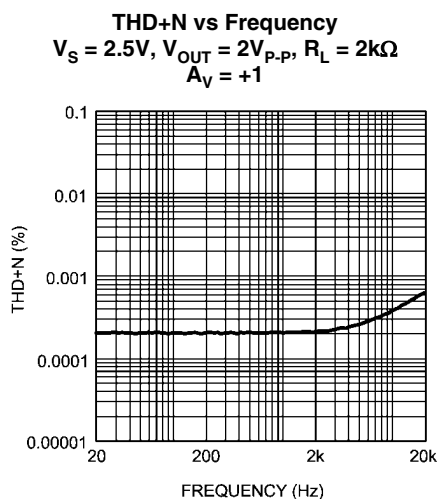


30047125

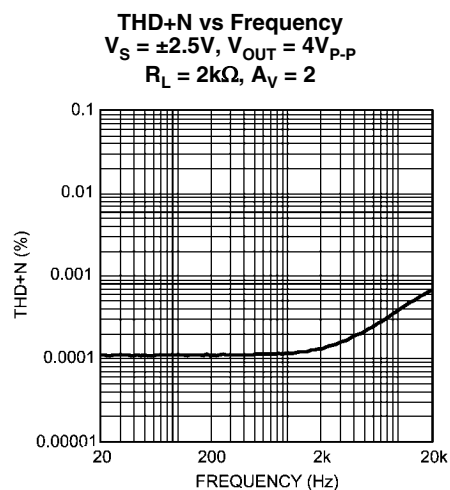

30047133

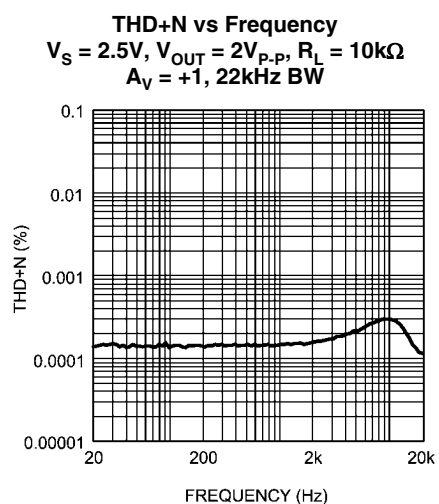


30047126

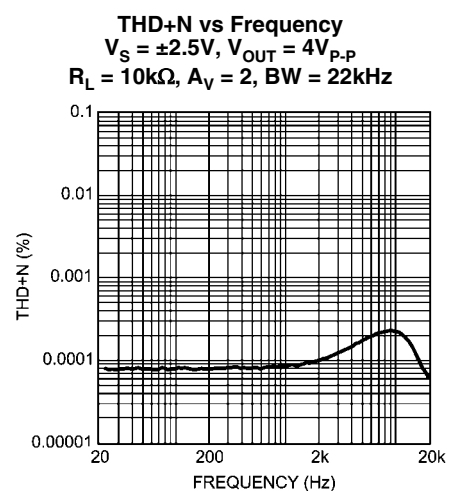


30047136

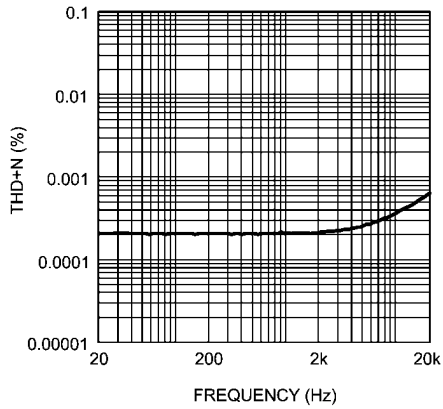**THD+N vs Frequency**  
 $V_S = 2.5V$ ,  $V_{OUT} = 2V_{P-P}$ ,  $R_L = 10k\Omega$   
 $A_V = +1$




30047127

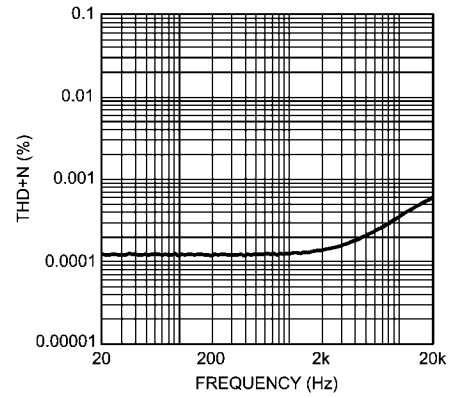**THD+N vs Frequency**  
 $V_S = \pm 2.5V$ ,  $V_{OUT} = 4V_{P-P}$   
 $R_L = 10k\Omega$ ,  $A_V = 2$




30047135

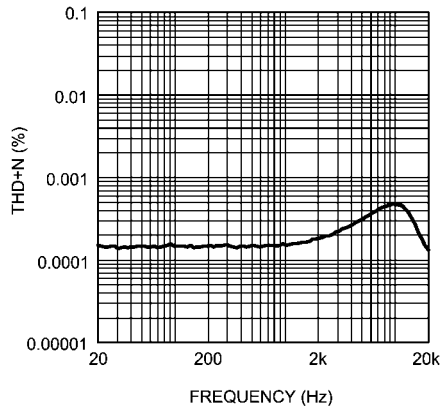**THD+N vs Frequency**  
 $V_S = 2.5V$ ,  $V_{OUT} = 2V_{P-P}$ ,  $R_L = 600\Omega$   
 $A_V = +1$ , 22kHz BW




30047128

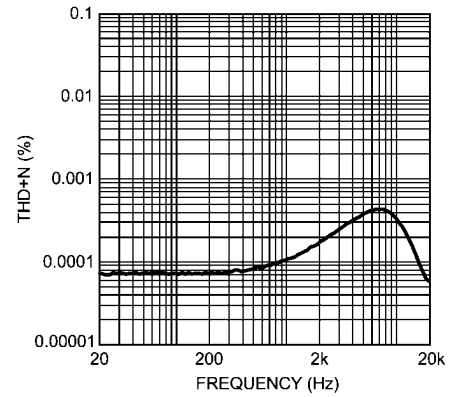**THD+N vs Frequency**  
 $V_S = \pm 2.5V$ ,  $V_{OUT} = 4V_{P-P}$   
 $R_L = 600\Omega$ ,  $A_V = 2$ , BW = 22kHz




30047138

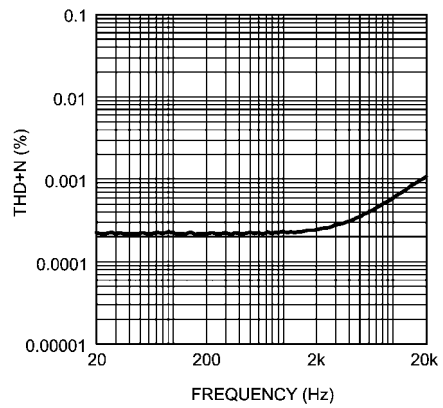**THD+N vs Frequency**  
 $V_S = 2.5V$ ,  $V_{OUT} = 2V_{P-P}$ ,  $R_L = 600\Omega$   
 $A_V = +1$









30047129

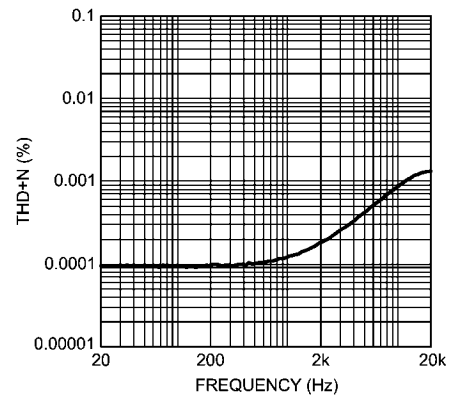**THD+N vs Frequency**  
 $V_S = \pm 2.5V$ ,  $V_{OUT} = 4V_{P-P}$   
 $R_L = 600\Omega$ ,  $A_V = 2$



30047137



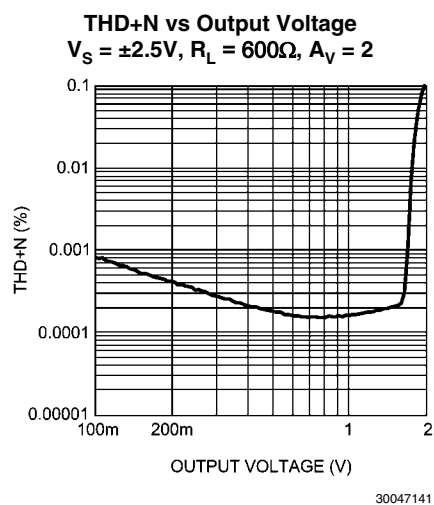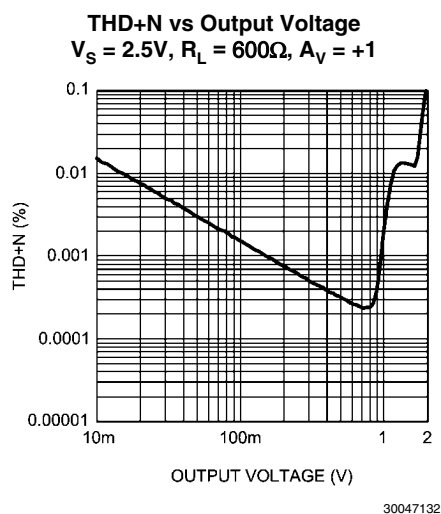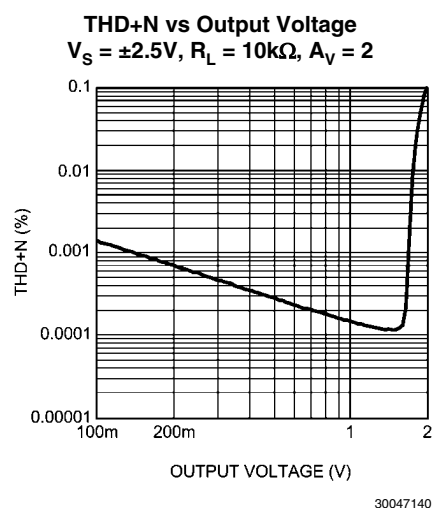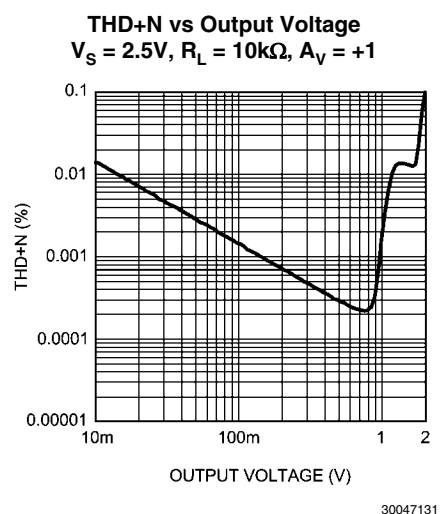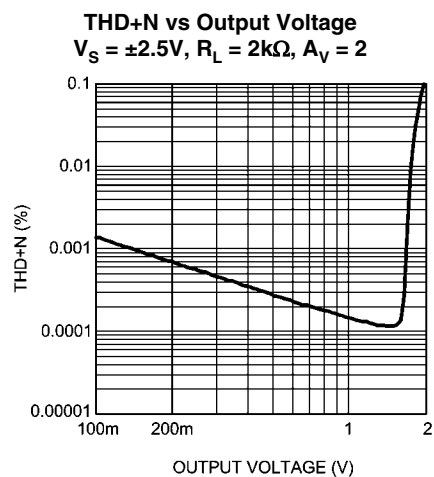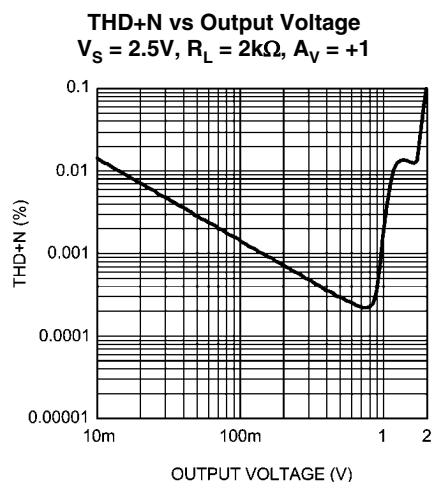

Revision Table

Rev	Date	Description
1.0	02/22/08	Initial release.



# Notes

For more National Semiconductor product information and proven design tools, visit the following Web sites at:

Products		Design Support	
Amplifiers	<a href="http://www.national.com/amplifiers">www.national.com/amplifiers</a>	WEBENCH	<a href="http://www.national.com/webench">www.national.com/webench</a>
Audio	<a href="http://www.national.com/audio">www.national.com/audio</a>	Analog University	<a href="http://www.national.com/AU">www.national.com/AU</a>
Clock Conditioners	<a href="http://www.national.com/timing">www.national.com/timing</a>	App Notes	<a href="http://www.national.com/appnotes">www.national.com/appnotes</a>
Data Converters	<a href="http://www.national.com/adac">www.national.com/adac</a>	Distributors	<a href="http://www.national.com/contacts">www.national.com/contacts</a>
Displays	<a href="http://www.national.com/displays">www.national.com/displays</a>	Green Compliance	<a href="http://www.national.com/quality/green">www.national.com/quality/green</a>
Ethernet	<a href="http://www.national.com/ethernet">www.national.com/ethernet</a>	Packaging	<a href="http://www.national.com/packaging">www.national.com/packaging</a>
Interface	<a href="http://www.national.com/interface">www.national.com/interface</a>	Quality and Reliability	<a href="http://www.national.com/quality">www.national.com/quality</a>
LVDS	<a href="http://www.national.com/lvds">www.national.com/lvds</a>	Reference Designs	<a href="http://www.national.com/refdesigns">www.national.com/refdesigns</a>
Power Management	<a href="http://www.national.com/power">www.national.com/power</a>	Feedback	<a href="http://www.national.com/feedback">www.national.com/feedback</a>
Switching Regulators	<a href="http://www.national.com/switchers">www.national.com/switchers</a>		
LDOs	<a href="http://www.national.com/ldo">www.national.com/ldo</a>		
LED Lighting	<a href="http://www.national.com/led">www.national.com/led</a>		
PowerWise	<a href="http://www.national.com/powerwise">www.national.com/powerwise</a>		
Serial Digital Interface (SDI)	<a href="http://www.national.com/sdi">www.national.com/sdi</a>		
Temperature Sensors	<a href="http://www.national.com/tempsensors">www.national.com/tempsensors</a>		
Wireless (PLL/VCO)	<a href="http://www.national.com/wireless">www.national.com/wireless</a>		

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

## LIFE SUPPORT POLICY

**NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION.** As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

Copyright© 2008 National Semiconductor Corporation

For the most current product information visit us at [www.national.com](http://www.national.com)



**National Semiconductor  
Americas Technical  
Support Center**  
Email:  
[new.feedback@nsc.com](mailto:new.feedback@nsc.com)  
Tel: 1-800-272-9959

**National Semiconductor Europe  
Technical Support Center**  
Email: [europe.support@nsc.com](mailto:europe.support@nsc.com)  
German Tel: +49 (0) 180 5010 771  
English Tel: +44 (0) 870 850 4288

**National Semiconductor Asia  
Pacific Technical Support Center**  
Email: [ap.support@nsc.com](mailto:ap.support@nsc.com)

**National Semiconductor Japan  
Technical Support Center**  
Email: [jpn.feedback@nsc.com](mailto:jpn.feedback@nsc.com)