

Development of an Extensive SPICE Macromodel for "Current-Feedback" Amplifiers

National Semiconductor
Application Note 840
July 1992



Abstract

A current-feedback amplifier macromodel has been developed which simulates the more common small-signal effects such as small-signal transient response and frequency response as well as temperature effects, noise, and power supply rejection ratio. Also modeled are large-signal effects such as non-linear input transfer characteristics and input/output slew rate limiting.

Detailed descriptions of each stage in the model will be presented with examples of model performance and correlation to actual device behavior.

Introduction

With the increasing complexity and shorter design cycles of today's designs, computer modeling with SPICE (Simulation Program with Integrated Circuit Emphasis) is becoming more popular. This is especially true with high-speed designs utilizing the latest in current-feedback amplifiers. However, an accurate, detailed macromodel for current-feedback amplifiers with good convergence characteristics has not yet been available.

Macromodeling Philosophy

The philosophy used in creating this macromodel was a desire to design a model that would simulate the typical behavior of a current-feedback amplifier to within 10% of typical parameters while executing much faster than a device level model. Also, the macromodel would act as a development platform for effects not normally included in other models such as temperature effects, noise, and many

of the other second and third order effects that are characteristic in current-feedback amplifiers such as the LM6181.


The LM6181

National Semiconductor's monolithic current-feedback amplifier, the LM6181, offers the designer an amplifier with the high-performance advantages of current-feedback topology without the high cost associated with hybrid devices. The LM6181 has a bandwidth of 100 MHz, slew rate of 2000 V/ μ s, settling time of 50 ns (0.1%), and 100 mA of output current drive. A special output stage allows the LM6181 to directly drive a 50 Ω or 75 Ω back-terminated coax cable. To understand how this device functions, a description of current-feedback amplifiers is in order.

Current-Feedback Amplifiers

Figure 1 shows the block diagram for the current-feedback amplifier. The main difference when compared to voltage-feedback amplifiers (VFA's) is that in the current-feedback topology, a unity gain buffer drives the inverting input. Since this is an inherently low impedance, the feedback error signal is treated as a current rather than a voltage. During input transients, an error current will flow into or out of the input buffer. This current is then mirrored to a current-to-voltage converter ($Z_t(s)$) which consists of a large ($\approx 2\text{ M}\Omega$) transimpedance and an output buffer. Since the large transimpedance is analogous to the large voltage gain of VFA's, the output voltage is servo'd to a value which causes the current through R_f and R_g to cancel the current in the input buffer.

Current-Feedback Amplifiers (Continued)

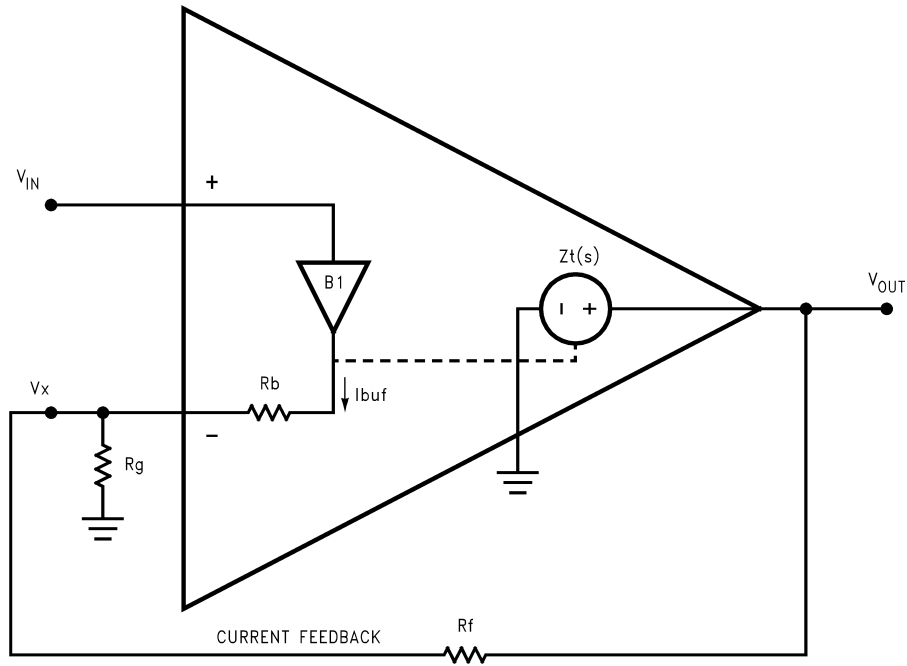

01148801

FIGURE 1. Block Diagram of a Current-Feedback Amplifier

Analysis of Current-Feedback Topology

From the simplified current-feedback amplifier schematic in Figure 2, it can be observed that the inverting ($-IN$) terminal is driven by a unity gain buffer stage. Transistors Q3 and Q4 make up the high-impedance input ($+IN$) to the buffer while Q5 and Q9 comprise a push-pull stage whose low output impedance is determined by $V_T/(I_{CQ5} + I_{CQ9}) = V_T/(I_1 + I_2)$ assuming I_1 and I_2 are equal. The function of the input buffer is to drive the inverting input to the same voltage as the non-inverting input much like a voltage-feedback amplifier does via negative feedback. Transistors Q6, Q7, Q8, Q10, Q11 and Q12 form a pair of Wilson current mirrors which transfer the output current of the input buffer to a high-impedance (Z_t) node. The equivalent capacitance (C_C) at this node is charged to the value of the output voltage. This voltage is then conveyed to a second buffer made up of Q14, Q15, Q17 and Q18 which drives the output pin of the amplifier. Short-circuit current limiting is performed by transistors Q19 and Q20. Back on the input of the amplifier, Q1 and Q2 provide a slew rate enhancement effect. For low closed-loop gains and large input steps these transistors turn on and increase the current available to the input buffer. This causes a transient increase in the current available to charge the compensation capacitor via the current mirrors, resulting in a faster slew rate for low gains. Now that the simplified circuit has been described, it will be informative to analyze the block diagram for the model.

By summing the currents at node V_X in Figure 1 and using the fact that $V_O = I_{buf} \times Z_t(s)$, the transfer function of the non-inverting configuration can be determined to be:

$$\frac{V_o}{V_{in}} = \left(1 + \frac{R_f}{R_g}\right) \times \left[\frac{1}{1 + \frac{R_f + \left[1 + \frac{R_f}{R_g}\right] \times R_b}{Z_t(s)}} \right] \quad (1)$$

where $Z_t(s)$ is the open-loop transimpedance as a function of complex frequency. Notice, in Equation (1), the $1 + R_f/R_g$ term on the left is the standard closed-loop voltage gain equation for non-inverting amplifiers while the term on the right is an error term. The $1 + R_f/R_g$ in the error term is the noise gain of the amplifier and R_b is the input buffer's quiescent output impedance ($\approx 30\Omega$ for the LM6181). If $Z_t(s)$ is assumed to be large, the error term goes to 1. The closed-loop bandwidth is defined as the frequency at which the magnitude of the error term equals $1/\sqrt{2}$ (-3 dB). If $Z_t(s)$ is approximated to be a single pole function, then:

$$Z_t(s) = \frac{Z_t(dc)}{1 + s \times Z_t(dc) \times C_C} \quad (2)$$

where C_C is the value of the internal compensation capacitor in Figure 2. By substituting Equation (2) for $Z_t(s)$ in Equation (1) and assuming $Z_t(dc)$ is much larger than R_f , the closed-loop bandwidth can now be found to be:

$$bw = \frac{1}{2 \times \pi \times C_C \left[R_f + \left(1 + \frac{R_f}{R_g}\right) \times R_b \right]} \quad (3)$$

Analysis of Current-Feedback Topology (Continued)

If the input buffer output resistance (R_b) times the noise gain of the amplifier ($1 + R_f/R_g$) is assumed to be small compared to R_f , Equation (3) reduces to:

$$bw = \frac{1}{2 \times \pi \times C_C \times R_f} \quad (4)$$


Notice that the ideal closed-loop bandwidth in Equation (4) is dependent only on the value of the internal compensation capacitor (C_C) and the feedback impedance (R_f). A recommended value for R_f is usually specified in the manufacturer's datasheet ($R_f = 820\Omega$ for the LM6181). Therefore, if the above assumptions are valid, there is theoretically no reduction in bandwidth as R_g is decreased to increase closed-loop gain.

Another special feature of the current-feedback amplifier is the theoretical absence of slew-rate limiting. Since the total

output current of the input buffer is available to charge the compensation capacitor (C_C), the slew rate is proportional to the output voltage [4].

$$SR = \frac{I_{buf}}{C_C} = \frac{V_{OUT}}{C_C \times R_f} \quad (5)$$

This simplified analysis is adequate for small closed-loop gains; however, since R_b is typically several tens of ohms, the bandwidth and slew rate will be less than ideal for large gains. Also, there are slew-rate characteristics associated with the input buffer that are dominated by the slew-rate enhancement transistors (Q1 and Q2 in Figure 2) and stray package capacitances. All these second order effects are included in the macromodel input stage to achieve accurate simulation results.

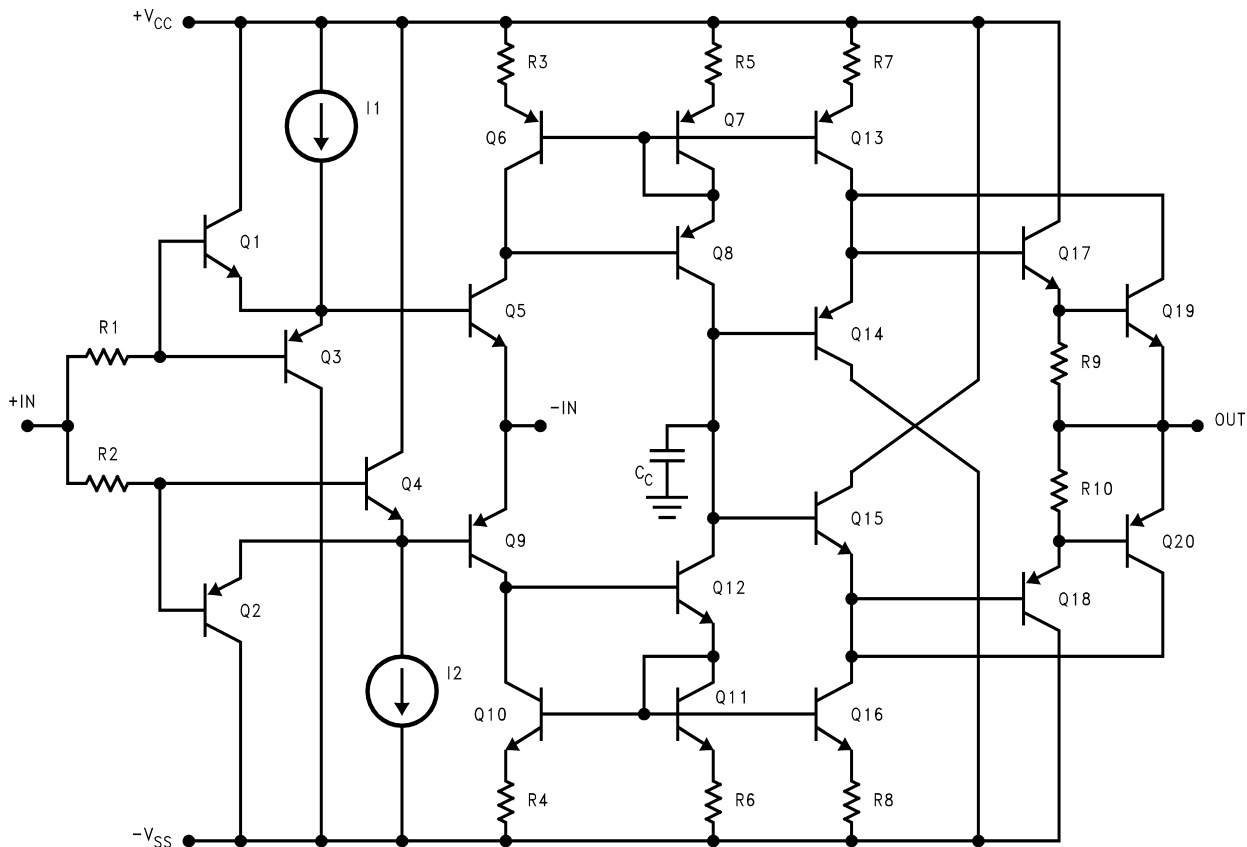

01148802

FIGURE 2. LM6181 Simplified Circuit

The Input Stage

Figure 3 shows the macromodel input stage which performs many important functions such as the simulation of input buffer output impedance, input/output slew rate, supply voltage dependent input bias current and offset voltage, input capacitance, CMRR and noise [2]. Voltage-controlled

current-sources G11 and G12 establish the input buffer's output impedance depending on supply voltage. For a given supply voltage, these current-sources can be determined by rearranging the standard bipolar transistor output resistance equation:

The Input Stage (Continued)

$$I_1 = I_2 = \frac{k \times T}{2 \times q \times R_b} \quad (6)$$

R_b is the output impedance of the input buffer and may be approximated with:


$$R_b = \frac{Z_t}{A_{VOL}} \quad (7)$$

where A_{VOL} is the differential open-loop voltage gain of the amplifier from input to output. *Equation (7)* can be derived by shorting R_g and solving the transfer function in *Equation (1)*.

The input stage slew rate is controlled by R_1 , R_2 , C_1 and C_2 . The total current available to charge the capacitors C_1 and C_2 determines the maximum slew rate of the input stage. To reduce the number of PN junctions in the model, the slew rate enhancement transistors were modeled with diodes DS_1 and DS_2 and current-sources FI_1 and FI_2 .

Input bias currents are simulated with polynomial-controlled current-sources G_{b1} and G_{b2} which are dependent on both supply voltage and temperature. Current-source G_{b2} also models the residual input current (I_b) caused by imbalances in the input buffer as well as the error current caused by the input common mode voltage. The latter is called Inverting Input Bias Current Common Mode Rejection and is designated I_{bCMR} on most datasheets. Fn_1 and Fn_2 transfer the current from the noise-current sources to the inputs of the amplifier.

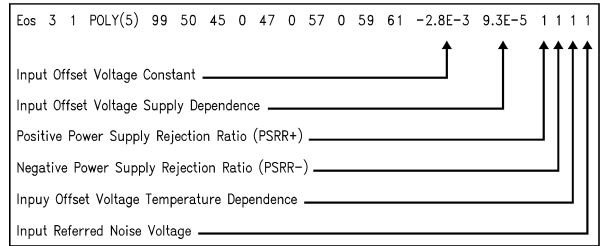The offset voltage-source, Eos , provides a supply voltage dependent input offset voltage and reflects the error voltages from the power supply rejection ratio stage, the thermal effect stage, and the noise-voltage source. Below is a diagram of the Eos polynomial-source and the effects that correspond to each term.



Stray capacitance at the inputs of the amplifier modeled by C_{in1} and C_{in2} has a dramatic effect on the peaking in the amplifier's high frequency response. Common Mode Rejection Ratio can be modeled in the input stage by properly setting the early voltage (V_{af}) of the input transistor models. A good starting point for the value of the early voltage is given by:

$$V_{af} = \frac{2 \times V_T}{10^{\left[\frac{CMRR(dB)}{20} \right]}} \quad (8)$$

Also, in the transistor model, a value for beta (BF) should be chosen. It should be large enough so that the base currents do not interfere with the input bias currents of the model, but not so large as to cause convergence problems during simulation.

The output of the input stage is the sum of the currents flowing through R_3 and R_4 . The voltage across R_3 and R_4 is softly clamped by the V_1 , RE_1 , D_1 and V_2 , RE_2 , D_2 strings respectively. This effectively limits the current to the second stage yet still allows the second stage slew rate to increase for large input signals.

The Input Stage (Continued)

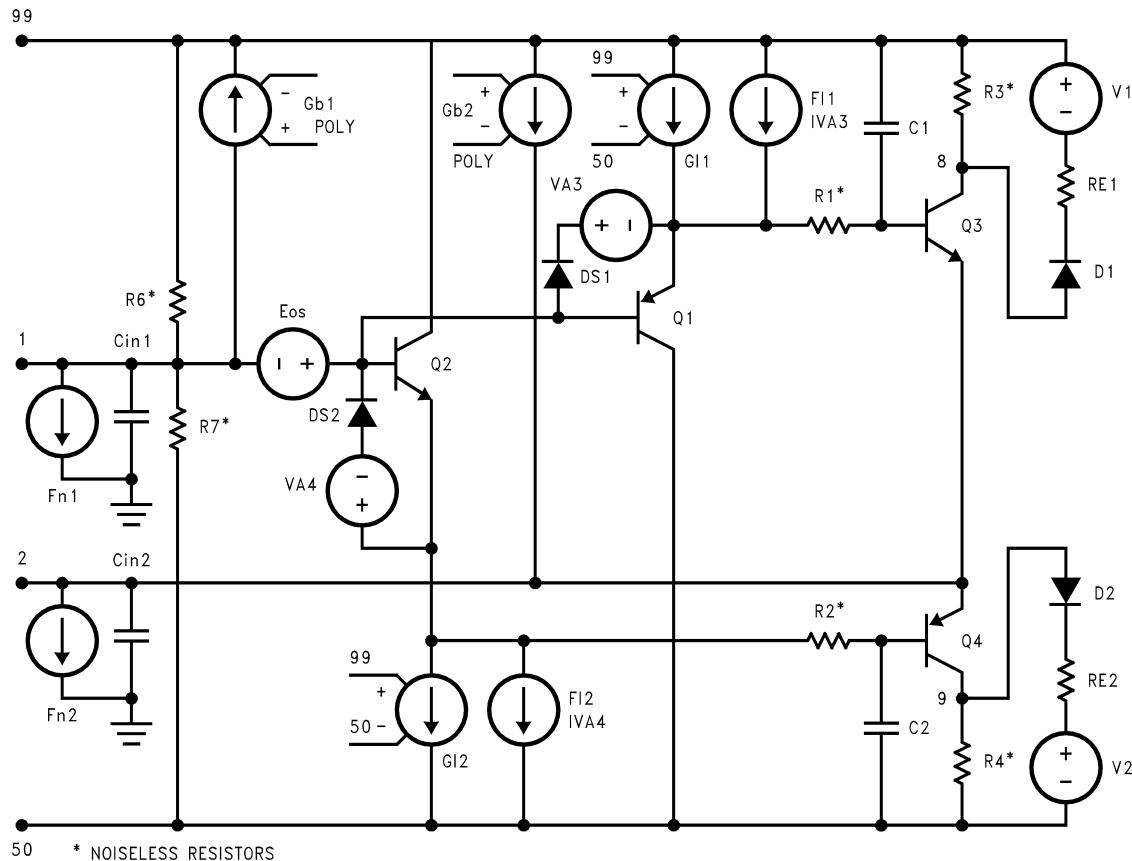


FIGURE 3. Macromodel Input Stage. Simulates Input Impedance, Input Errors, CMRR, Input/Output Slew Rate, Input Capacitance, and Noise.

The Second Stage


The second stage of the macromodel (*Figure 4*) provides the open-loop transimpedance, the first pole, output clamping and supply dependent quiescent supply current. The voltage-controlled current-source G1 is controlled by a second order polynomial equation which calculates the current through R3 and R4 and reflects the sum directly into the second stage. By making the polynomial coefficients equal to the reciprocal of R3 and R4, the DC transimpedance of the model is simply equal to the value of R5. The dominant pole and output slew rate is established with capacitor C3 which is comparable in function to C_C in the LM6181 simplified circuit. Output clamping is performed with two diodes (D3–D4) each in series with a voltage-source (V3–V4). Clamping should be done here at the gain stage to prevent node 15 from reaching several thousands of volts which could cause convergence problems during simulation. Quiescent current is modeled with the combination of I3 and the R8–R9 series resistors. As the supply voltage increases, the current through R8 and R9 will increase effectively simulating that behavior in the real device. The value for resistors

R8 and R9 can be calculated by dividing the change in supply voltage by the change in supply current ($\Delta V_S/\Delta I_S$) anywhere within the operating range of the amplifier. Current-source I3 is evaluated by taking the total supply current at a given voltage and subtracting off the current through all other significant supply loads. These loads are R8, GI1, GI2, and R3 so that:

$$I_3 = I_{VS} @ 15V - \frac{15}{R_8} - 3 \times I_1 \quad (9)$$

The 3 x I1 comes from the fact that the currents through GI1, GI2 and R3 are equal. Resistors R8 and R9 also act as a voltage divider and establish a common-mode voltage (V_H) for the model directly between the rails. If the supply rails are symmetrical, i.e., $\pm 15V$, node 49 will be at zero volts. Voltage-controlled voltage-source EH measures the voltage across R8 and subtracts an equal voltage from the positive supply rail to provide a stiff point between the rails (node 98) to which many other stages in the model are referenced.

The Second Stage (Continued)

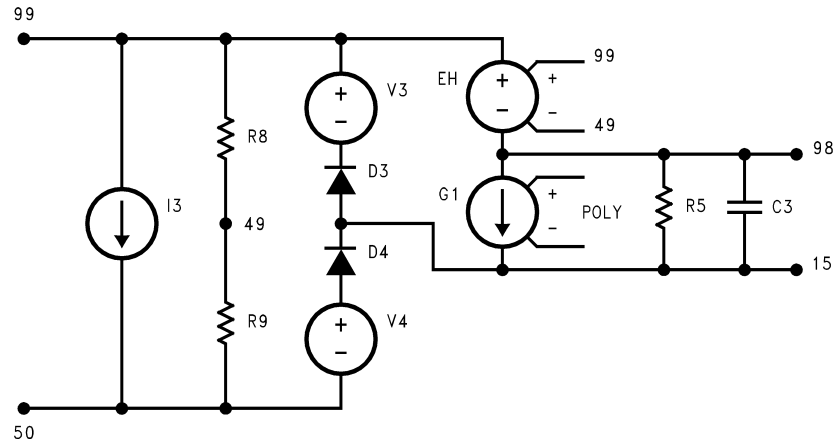

01148804

FIGURE 4. The Macromodel Second Stage Models Open-Loop Transimpedance, First Pole, Output Swing Limiting, and Quiescent Supply Current.

Frequency-Shaping Stages

In keeping with the philosophy of providing a macromodel that is as accurate as possible, it has been determined that the model must be capable of easily accommodating as many poles and zeros that are necessary to precisely shape the magnitude and phase response of the model [5]. This is accomplished with telescopic frequency-shaping stages that each have unity DC gain making it easier to add poles and zeros without changing the DC gain of the model. The LM6181 macromodel has four high frequency pole stages and no zero stages, however, each of the three types of frequency-shaping stages will be discussed in detail should the reader wish to develop macromodels for other amplifiers.

The first type of frequency-shaping stage is a pole. In *Figure 5 (a)*, resistor R14 is set to 1 kΩ. This value is chosen to reduce the thermal noise associated with this resistor and to simplify the calculations for the other components in the stage. Current-source G2 is controlled by the output voltage from the previous stage and its g_m is set to the reciprocal of R14 or 10^{-3} to maintain unity DC gain of the stage. Capacitor


C4 rolls off the gain at high frequencies and is set with the standard pole equation: $C = 1/(2 \times \pi \times f_p \times R)$ where f_p is the -3 dB frequency of the pole in Hz.

Even though SPICE will attempt to process a bare zero stage, in the real world, such a circuit is actually non-causal and SPICE may not converge because an ideal inductor can generate an infinite voltage if the current through it changes instantaneously. To introduce a zero in the frequency response of the model, a pole must be combined with the zero to form a zero/pole or a pole/zero stage. The circuit for the zero/pole stage is shown in *Figure 5 (b)*. This stage will have unity DC gain if the g_m of G5 is set to the reciprocal of R19. As the frequency increases, L1's impedance starts to increase until R18 dominates causing the gain to level off.

The last type of frequency-shaping stage is the pole/zero circuit shown in *Figure 5 (c)*. As the frequency increases, the gain starts at unity and decreases until the impedance of the capacitor is negligible compared to its series resistor. For more information on poles and zeros, see references [7] and [8].

Frequency-Shaping Stages


(Continued)

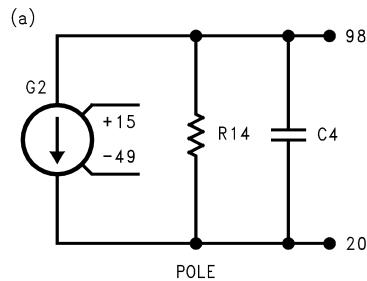

$$R14 = 1 \text{ k}\Omega$$

$$G2 = \frac{1}{R14} = 10^{-3}$$
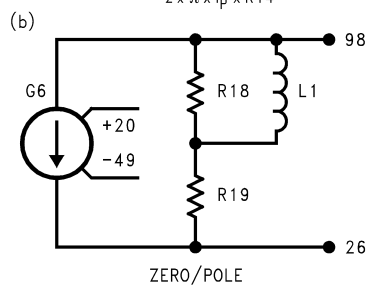
$$C4 = \frac{1}{2 \times \pi \times f_p \times R14}$$




$$R19 = 1 \text{ k}\Omega$$

$$G6 = \frac{1}{R19} = 10^{-3}$$

$$R18 = \left(\frac{f_p}{f_z} - 1 \right) \times R19$$
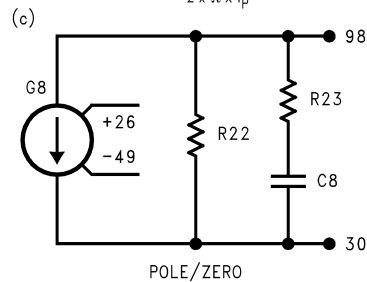
$$L1 = \frac{R18}{2 \times \pi \times f_p}$$



$$R22 = 1 \text{ k}\Omega$$

$$G8 = \frac{1}{R22} = 10^{-3}$$

$$R23 = \frac{R22}{\frac{f_z}{f_p} - 1}$$

$$C8 = \frac{1}{2 \times \pi \times f_z \times R2}$$


01148805

FIGURE 5. Macromodel Frequency-Shaping Stages

PSRR Stage

Power supply rejection ratio is a parameter that many vendors have previously neglected in their SPICE models. Since

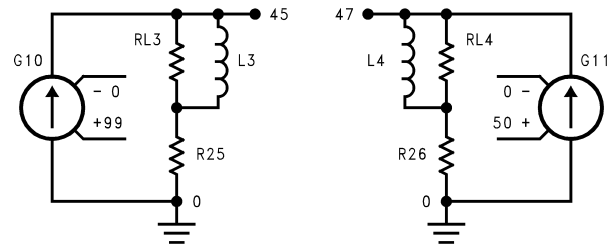AC power supply impedance is extremely critical in high-speed amplifier designs, both DC and AC PSRR were included in this model so that the designer can explore the effects of supply bypassing. The PSRR stage (see Figure 6) consists of two attenuation circuits controlled by the voltage from each rail to ground whose gains increase at 20 dB per decade.



01148808

FIGURE 6. Macromodel PSRR Stage

The signals generated at nodes 45 and 47 are directly reflected to the input of the amplifier via the second and third terms of the Eos polynomial-controlled source. Since the PSRR stages are referenced to ground, a large offset voltage will be developed if the model is operated from asymmetrical supplies. This compromise was necessary in order to include the PSRR effects; however, if operation on asymmetrical supplies is required, the PSRR effects can be disabled by changing the second and third polynomial terms in Eos from 1 to 0. For example, change:

Eos 3 1 POLY(5) 99 50 45 0 47 0 57 0 59 61 -2.8E-3 9.3E-5 1 1 1 1

to:

Eos 3 1 POLY(5) 99 50 45 0 47 0 57 0 59 61 -2.8E-3 9.3E-5 0 0 1 1

To set the component values in the PSRR stages, R25 and R26 are arbitrarily chosen to be 10Ω. The g_m 's of the current sources are set so that the DC gain of each stage is equal to the DC value of the PSRR or:

$$G10 = 10^{\frac{\text{PSRR}}{20}} \times \left[\frac{1}{R25} \right] \quad (10)$$

where PSRR is the typical DC rejection ratio in dB. The inductors, L3 and L4, determine the 3 dB frequency of each stage and can be set with:

$$L = \frac{R}{2 \times \pi \times f_{3\text{dB}}} \quad (11)$$

Resistors RL3 and RL4 cancel the zeros associated with the inductors at a frequency above the unity gain frequency of the amplifier. This helps with transient convergence when simulating inductive or resistive power supply lines.

Thermal Effects

The predominant thermal effects of a current-feedback amplifier are the change in offset voltage and input bias current as a function of temperature. The macromodel stages in Figure 7 are used to simulate these effects by utilizing the SPICE temperature dependent resistor model which is controlled with the Equation (9):

Thermal Effects (Continued)

$$R(\Omega) = \langle \text{value} \rangle \times (1 + TC1 \times (T - T_{nom}) + TC2 \times (T - T_{nom})^2) \quad (12)$$

where $\langle \text{value} \rangle$ is the value of the resistor at T_{nom} (usually 27°C), T is the temperature in °C, $TC1$ is the linear temperature coefficient, and $TC2$ is the quadratic temperature coefficient. The equation will fit a quadratic curve through three points in a temperature graph by solving three equations with three unknowns. Since SPICE will give an error message if a resistor goes negative at any temperature, an offset bias is added to the resistor value whose voltage is then subtracted from the respective input error source ($Gb1$, $Gb2$, or Eos).

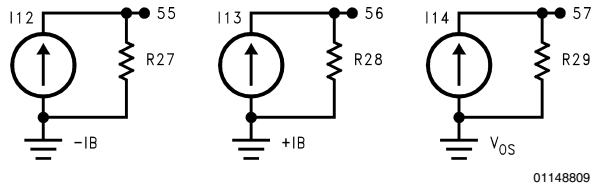


FIGURE 7. Macromodel Thermal Effect Stages

The voltages generated at nodes 55, 56, and 57 are scaled and used to control the input error sources $Gb2$, $Gb1$, and Eos respectively. The simulated results compare quite closely to the typical curves for the actual device as can be seen in *Figures 16, 17*.

Noise Stages

The addition of noise effects to any macromodel is similar to the techniques used for input offset voltage and drift. The total amplifier noise is lumped together and referred to the input of the model. Before noise sources are added, however, the model has to be rendered essentially noiseless. This is easier than it sounds, though, because noise adds vectorially. The total contribution of several noise sources can be found by:

$$E_{n_{total}} = \sqrt{(E_{n1})^2 + (E_{n2})^2 + (E_{n3})^2 \dots}$$

So, a latent noise source within the model will have to be reduced to only 1/4 of the desired noise level to maintain an accuracy of less than 3% ($\sqrt{1 + 0.25^2} = 1.03$). Most of the latent amplifier model noise comes from thermal noise generated by large-value resistors commonly used in macromodels. To reduce this noise, the resistor values are scaled so their thermal noise is negligible compared to the desired noise of the amplifier. If resistor scaling is not possible, as was the case with several resistors in the input stage of the LM6181 macromodel, a *noiseless resistor* can be used. A noiseless resistor is created by utilizing a voltage-controlled current-source (G device) with the same input and output terminals whose gm is set to the reciprocal of the required value of resistance (see *Figure 3* and the LM6181 netlist). The only caveat with using noiseless resistors is that a current-source is considered an open circuit when SPICE calculates the initial bias point of the circuit. Therefore, at least one other device must be connected to the nodes of the noiseless resistor to avoid “floating node” errors.

Now that the macromodel is rendered essentially noiseless, lumped noise sources can be added and referred to the input sources. *Figure 8* shows the equivalent noise model which consists of an ideal noiseless amplifier, two noise-current generators (i_{n+} and i_{n-}), from each input to ground and a noise-voltage generator (e_n) in series with non-inverting input.

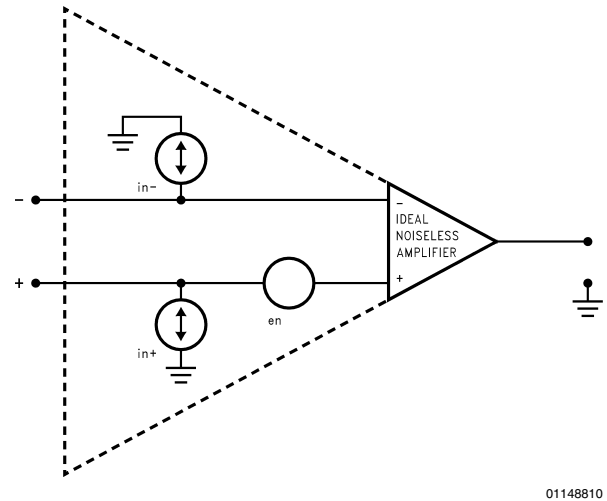


FIGURE 8. Equivalent Amplifier Noise Model

The noise-current generators are called F_{n1} and F_{n2} in the macromodel input stage (*Figure 3*), while the noise-voltage generator is included in the Eos polynomial-controlled source. The noise voltage or current which is actually referred to the input generators comes from separate noise source stages in the macromodel.

The noise-voltage circuit (*Figure 9*) generates both 1/f and white noise by using a 0.1V voltage-source which lightly biases a diode-resistor series combination. White noise is simply the thermal noise-current generated in the resistor which follows the spectral power density (per unit bandwidth) equation below:

$$i_n^2 = \frac{4 \times k \times T}{\text{Resistance}} \quad (13)$$

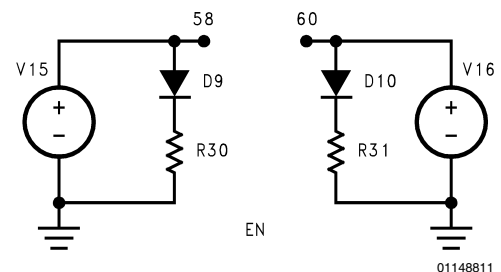


FIGURE 9. Macromodel Noise Voltage Stage

where i_n is the noise-current through the resistor, k is Boltzmann's constant (1.381×10^{-23}), and T is the temperature in °K ($^{\circ}\text{C} + 273.2^{\circ}$). By taking the square root of both

Noise Stages (Continued)

sides of the equation and multiplying by resistance, the required value of resistance can be found for a given noise-voltage spectral density with:

$$R = \frac{e_n^2}{2 \times 4 \times k \times T} \quad (14)$$

where e_n is the white noise voltage of the amplifier per $\sqrt{\text{Hz}}$. The "2" in the denominator comes from the fact that the voltage is taken differentially across two identical circuits of the noise-voltage source (nodes 58 and 60). The reason for using two identical circuits is so that a DC voltage would not be created which would be seen as an offset voltage on the input.

Flicker noise or $1/f$ noise-voltage comes from the SPICE diode model. By setting the flicker noise exponent (AF) to 1 and properly setting the flicker noise coefficient (KF), the resulting noise voltage will accurately simulate the $1/f$ noise-voltage spectral density with the correct "corner frequency". Equation (15) shows the noise-current that results from the SPICE diode model where I_d is the DC diode current and the $2 \times q \times I_d$ term is negligible compared to the $1/f$ noise of the amplifier.

$$i_n^2 = 2 \times q \times I_d + KF \times \frac{I_d^{AF}}{\text{FREQUENCY}} \quad (15)$$

To determine the value for KF in the macromodel, the following equation can be used:

$$KF = \frac{E_a^2}{R^2 \times I_d \times 2} \quad (16)$$

where E_a is the noise-voltage spectral density of the amplifier at 1 Hz and I_d is the DC current through the diode which can be determined with the standard Schottky diode equation. Again, the "2" in the denominator comes from the fact that the noise output is taken differentially across two identical circuits.

The white portion of the amplifier's noise current is modeled by utilizing the thermal noise current of a resistor in series with a zero volt voltage-source (see Figure 10).

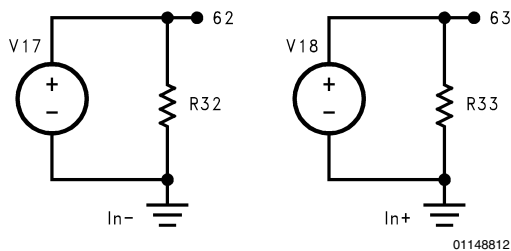


FIGURE 10. Macromodel White Noise-Current Generators

Since the noise-current through each of the resistors is measured with the voltage-sources and directly referred to

the respective current-controlled current-source on the input, the value for each resistor can be found by rearranging Equation (13) or:

$$R = \frac{4 \times k \times T}{i_n^2} \quad (17)$$

The term is the broad-band or white noise-current spectral density at the respective input of the amplifier.

To simulate the $1/f$ component of the noise-current, the flicker noise coefficient (KF) in the model for each pair of input transistors is set to obtain the correct corner frequency. In the LM6181 macromodel, KF is set to 4.13×10^{-13} for Q1 and Q2 while KF is set to 6.7×10^{-14} for Q3 and Q4. The flicker noise exponent (AF) is left at its default value of 1.

The macromodel's noise curves are compared to the actual amplifier's curves in Figures 18, 19, 20, 21. The simulation results are quite close to the actual noise characteristics of the amplifier. For more information on calculating and modeling amplifier noise, see references [3] and [9].

Output Stage

After the input signal is amplified and frequency shaped, it is further processed by the output stage shown in Figure 11. The output stage performs three important functions, namely, simulation of output impedance, short-circuit current limiting, and dynamic supply current.

The intermediate output signal appears at the output of the last frequency-shaping stage as a high-source-impedance voltage referenced to V_{IH} . Voltage-controlled voltage-source, E1, level shifts the intermediate output signal down from the positive rail and provides the output drive for the model. Output impedance is modeled with the combination of R35 and L5. Resistor R35 simulates the DC output impedance which determines the behavior of the model when driving heavy loads. Additionally, inductor L5 models the characteristic rise in output impedance as a function of frequency which is common to the emitter-follower output stage found in many amplifiers. Since an ideal inductor as modeled by SPICE has infinite Q, a bare inductor in the signal path can cause convergence problems if the current through it can change instantaneously. To lower the Q of the inductor and prevent convergence problems during simulation, a large value resistor, RL5, is placed across L5. Capacitor CF1 models stray capacitance across the feedback resistor which dramatically affects the high frequency response of the amplifier.

Short-circuit current limiting is also a necessary feature of any good amplifier macromodel. The diodes D5 and D6 each in series with a voltage-source V5 and V6 accomplish this function by effectively clamping the maximum voltage across R35. The value of the voltage-sources can be set with the following equation which was derived with the Schottky diode equation and summing the currents at node 40 assuming the output is shorted to ground.

$$V = R35 \times I_{SC} - \ln \left[\frac{V_{CC} - R35 \times I_{SC}}{I_S \times Z_{ofr}} + 1 \right] \times V_T \quad (18)$$

LM6181 Macromodel Netlist (Continued)

*NOTE: Due to the addition of PSRR effects, model must be operated
 * with symmetrical supply voltages. To avoid this limitation
 * and disable the PSRR effects, see Eos below.

***** INPUT STAGE *****

*
 GI1 99 5 POLY(1) 99 50 243.75U 2.708E-6
 GI2 4 50 POLY(1) 99 50 243.75U 2.708E-6
 FI1 99 5 VA3 100
 FI2 4 50 VA4 100
 Q1 50 3 5 QPN
 Q2 99 3 4 QNN
 GR1 5 6 5 6 2.38E-4
 *^4.2K noiseless resistor
 C1 6 99 .468P
 GR2 4 7 4 7 2.38E-4
 *^4.2K noiseless resistor
 C2 7 50 .468P
 GR3 99 8 99 8 1.58E-3
 *^633ohm noiseless resistor
 V1 99 10 .3
 RE1 10 30 130
 D1 30 8 DX
 GR4 50 9 50 9 1.58E-3
 *^633ohm noiseless resistor
 V2 11 50 .3
 RE2 11 31 150
 D2 9 31 DX
 Q3 8 6 2 QNI
 Q4 9 7 2 QPI
 DS1 3 12 DY
 VA3 12 5 0
 DS2 13 3 DY
 VA4 4 13 0
 GR6 1 99 1 99 5E-8
 *^20MEG noiseless resistor
 GR7 1 50 1 50 5E-8
 *^20MEG noiseless resistor
 GB1 1 99 POLY(2) 99 50 56 0 -1.2E-6 4E-8 1E-3
 FN1 1 0 V18 1
 GB2 99 2 POLY(3) 99 50 1 49 55 0 18.5E-6 -1.5E-7 -1E-7 -1E-6
 FN2 2 0 V17 1
 EOS 3 1 POLY(5) 99 50 45 0 47 0 57 0 59 61 -2.8E-3 9.3E-5 1 1 1 1
 *To run on asymmetrical supplies, change to 0..... ^ ^
 CIN1 1 0 2P
 CIN2 2 0 5.75P
 *

***** SECOND STAGE *****

*
 I3 99 50 4.47M
 R8 99 49 7.19K
 R9 49 50 7.19K
 V3 99 16 1.7
 D3 15 16 DX
 D4 17 15 DX
 V4 17 50 2.0
 EH 99 98 99 49 1
 G1 98 15 POLY(2) 99 8 50 9 0 1.58E-3 1.58E-3
 *Fp1 = 27.96 KHz
 R5 98 15 2.372MEG
 C3 98 15 2.4P
 *

***** POLE STAGE *****

*
 *Fp = 250 MHz

LM6181 Macromodel Netlist (Continued)

```

G2 98 20 15 49 1E-3
R14 98 20 1K
C4 98 20 .692P
*
***** POLE STAGE *****
*
*Fp = 250 MHz
G3 98 21 20 49 1E-3
R15 98 21 1K
C5 98 21 .692P
*
***** POLE STAGE *****
*
*Fp = 275 MHz
G4 98 22 21 49 1E-3
R16 98 22 1K
C6 98 22 .5787P
*
***** POLE STAGE *****
*
*Fp = 500 MHz
G5 98 23 22 49 1E-3
R17 98 23 1K
C7 98 23 .3183P
*
***** PSRR STAGE *****
*
G10 0 45 99 0 1.413E-4
L3 44 45 26.53U
R25 44 0 10
RL3 44 45 10K
G11 0 47 50 0 1.413E-4
L4 46 47 2.27364U
R26 46 0 10
RL4 46 47 10K
*
***** THERMAL EFFECTS *****
*
I12 0 55 1
R27 0 55 10 TC = 3.453E-3 7.93E-5
I13 0 56 1E-3
R28 0 56 1.5 TC = 9.303E-4 8.075E-5
I14 0 57 1E-3
R29 0 57 3.34 TC = 3.111E-3
*
***** NOISE SOURCES *****
*
V15 58 0 .1
D9 58 59 DN
R30 59 0 726.4
V16 60 0 .1
D10 60 61 DN
R31 61 0 726.4
V17 62 0 0
R32 62 0 73.6
V18 63 0 0
R33 63 0 1840
*
***** OUTPUT STAGE *****
*
F6 99 50 VA7 1
F5 99 35 VA8 1
D7 36 35 DX
VA7 99 36 0
D8 35 99 DX

```

LM6181 Macromodel Netlist (Continued)

```

E1 99 37 99 23 1
VA8 37 38 0
R35 38 40 50
V5 33 40 5.3V
D5 23 33 DX
V6 40 34 5.3V
D6 34 23 DX
CF1 41 2 2.1P
L5 40 41 31N
RL5 40 41 100K
*
***** MODELS USED *****
*
.MODEL QNI NPN(IS = 1E-14 BF = 10E4 VAF = 62.9 KF = 6.7E-14)
.MODEL QPI PNP(IS = 1E-14 BF = 10E4 VAF = 62.9 KF = 6.7E-14)
.MODEL QNN NPN(IS = 1E-14 BF = 10E4 VAF = 62.9 KF = 4.13E-13)
.MODEL QPN PNP(IS = 1E-14 BF = 10E4 VAF = 62.9 KF = 4.13E-13)
.MODEL DX D(IS = 1E-15)
.MODEL DY D(IS = 1E-17)
.MODEL DN D(KF = 1.667E-9 AF = 1 XTI = 0 EG = .3)
.ENDS

```

Simulation Accuracy

The real test of a macromodel is how the simulation results compare with the real-world device. The table below shows some of the amplifier parameters and how the simulation compares to actual device behavior. As can be seen, the goal of a 10% match between the model and the actual device was achieved.

A good figure of merit for a macromodel is the accuracy of its small-signal transient response. *Figures 14, 15* show the small-signal response of the real LM6181 and the simulation output. Notice that the simulated over-shoot and frequency of ringing closely match that of the actual device. This is due to the accurate modeling of the frequency response and output impedance capabilities of the model.

romodel includes effects such as accurate input transfer response, accurate AC response, temperature effects, DC and AC PSRR, and noise. Even with the addition of all these features, the macromodel's simulation speed is still more than twice as fast as a device level micromodel. The speed advantage of this macromodel mainly comes from the fact that it converges extremely well. Since careful attention was paid to convergence during the development of the model, there is no difficulty establishing a bias point or dealing with large input signals. With detailed and accurate vendor supplied macromodels such as the one described in this paper, the designer can easily verify the effects of strays and amplifier limitations in his circuit.

Conclusion

A truly comprehensive SPICE compatible macromodel for current-feedback amplifiers has been developed. The mac-

Parameter	Typical Value	Simulation Results	% Error
$Z_{t(dc)}$ $RI = 1\text{ k}\Omega$	127 dB Ω	126.6 dB Ω	4.5%
$BW_{3\text{ dB}}$ $A_V = -1$ $RI = 1\text{ k}\Omega$	100 MHz	103.9 MHz	3.9%
I_{B+}	1.5 μA	1.5 μA	0.0%
I_{B-}	-4.0 μA	-4.0 μA	0.0%
V_{OS}	-3.4 mV	-3.3 mV	1.2%
I_{supp}	7.5 mA	7.7 mA	2.7%
Pulse Resp. Overshoot	35%	34.8%	0.6%
Slew Rate $V_{IN} = \pm 10\text{V}$	1400 V/ μs	1468 V/ μs	4.8%
I_{SC}	130 mA	136.8 mA	5.2%
e_n	5 nV/ $\sqrt{\text{Hz}}$	4.9 nV/ $\sqrt{\text{Hz}}$	2.0%
i_{n+}	3 pA/ $\sqrt{\text{Hz}}$	2.96 pA/ $\sqrt{\text{Hz}}$	1.3%
i_{n-}	16 pA/ $\sqrt{\text{Hz}}$	15.1 pA/ $\sqrt{\text{Hz}}$	5.6%

Conclusion (Continued)

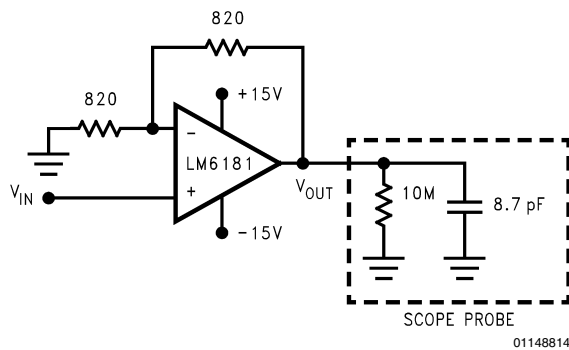


FIGURE 12. Non-inverting amplifier. $A_v = +2$. It is very important to include a model of the scope probe on the output of the amplifier to obtain reasonable results from the simulation.

```
*LM6181 Small-Signal Response.  $A_v = +2$ .
*Rf = Rg = 820ohm.
*
XAR1 3 2 7 4 6 LM6181
VP 7 0 15V
VN 4 0 -15V
VIN 3 0 PULSE (-.2V .2V 40N .2N .2N)
RF 6 2 820ohm
RI 2 0 820ohm
RL 6 0 10MEG
CL 6 0 8.7pF
.LIB CF.LIB
.OPTIONS RELTOL = .0001 CHGTOL = 1E-20
.TRAN/OP .1N 200N
.PROBE
.END
```

FIGURE 13. Non-Inverting Amplifier Netlist [9]

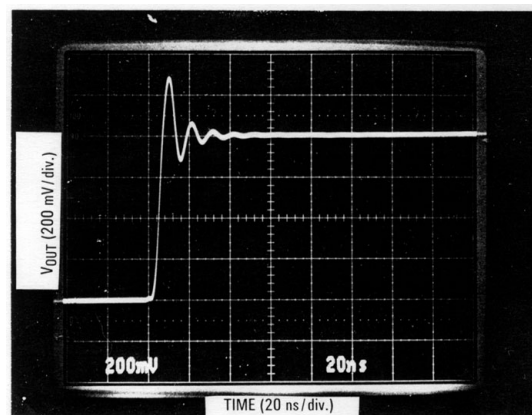


FIGURE 14. LM6181 Small-Signal Transient Response

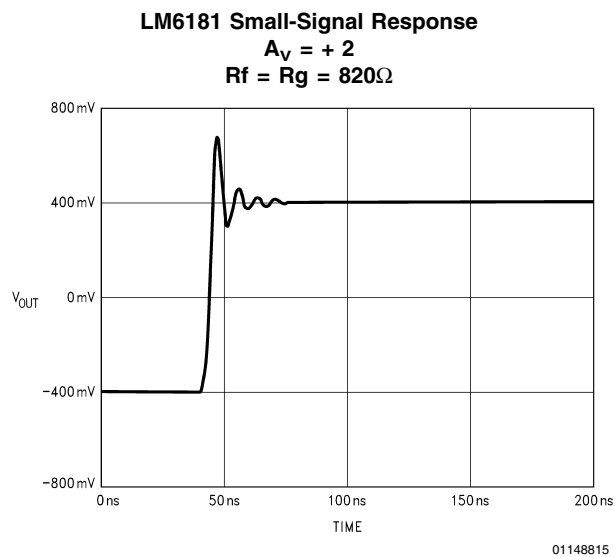


FIGURE 15. LM6181 Simulated Transient Response

Conclusion (Continued)

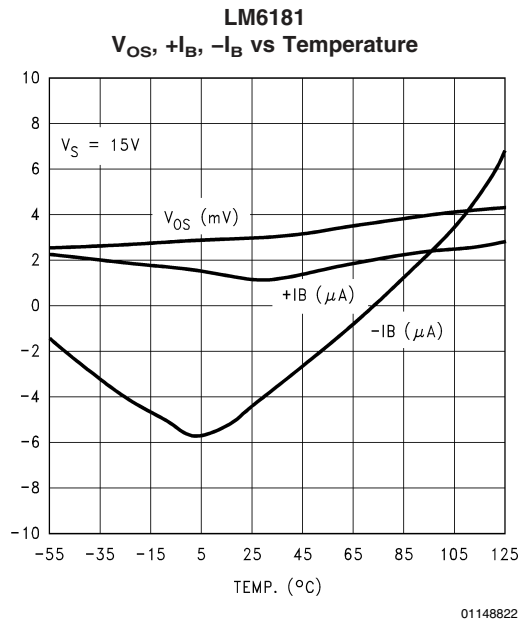


FIGURE 16. LM6181 Temperature Effects

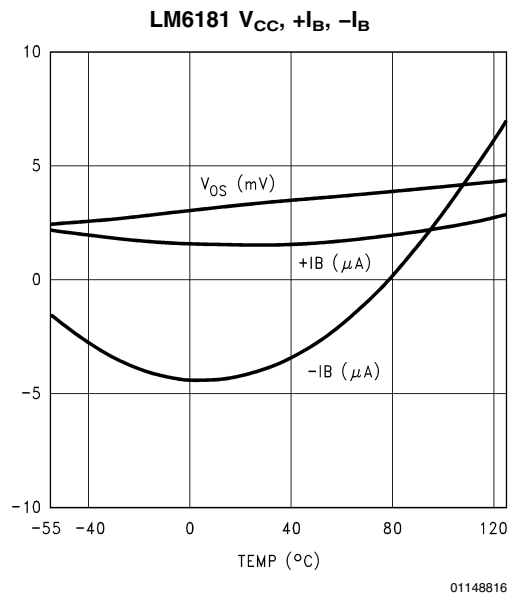


FIGURE 17. LM6181 Simulated Temperature Effects

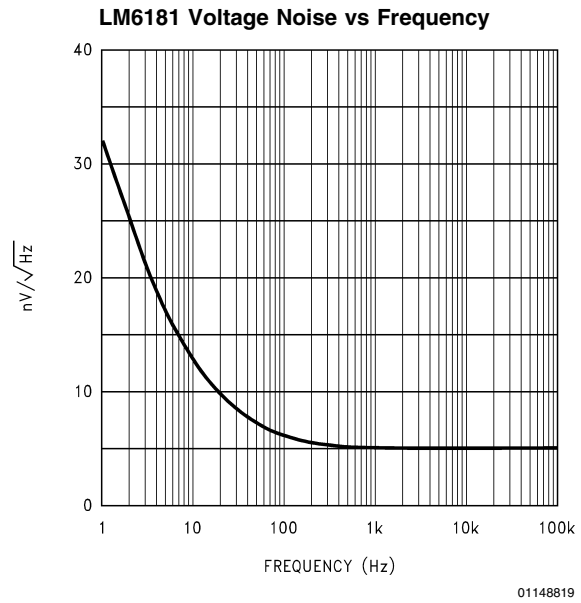


FIGURE 18. LM6181 Voltage-Noise Response

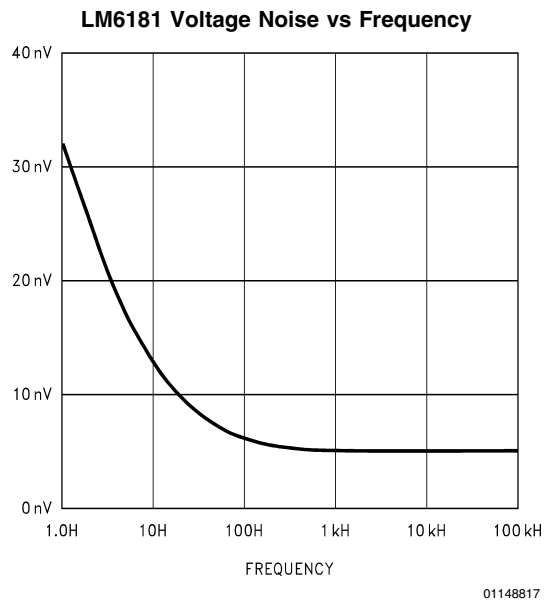


FIGURE 19. LM6181 Simulated Voltage-Noise Response

Conclusion (Continued)

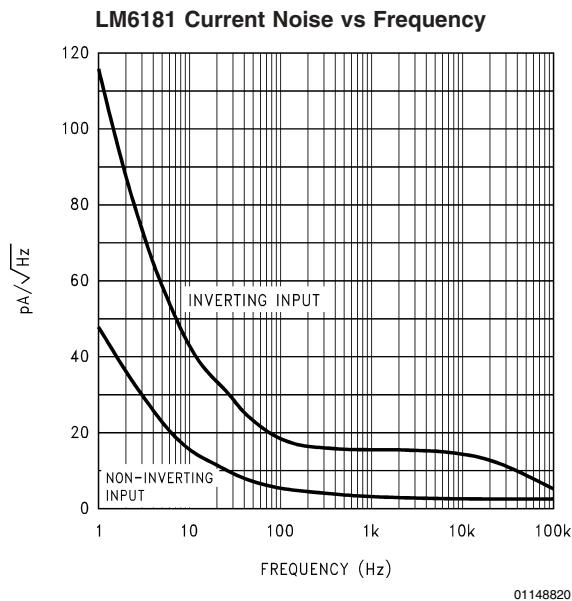


FIGURE 20. LM6181 Current-Noise Response

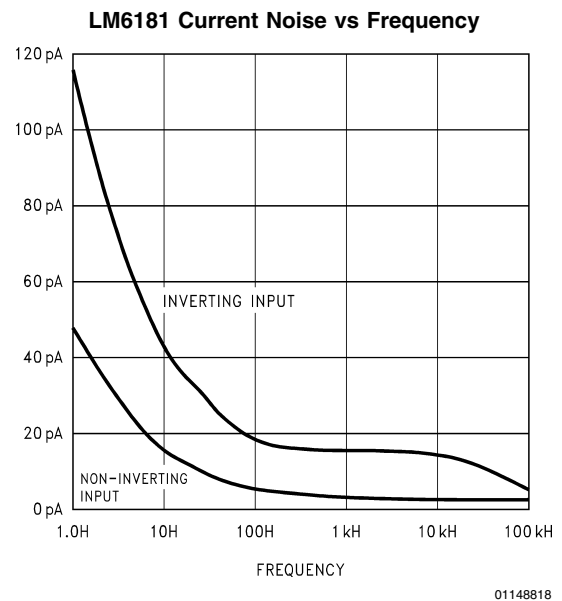


FIGURE 21. LM6181 Simulated Current-Noise Response

References

1. Boyle, G.R., "Macromodeling of Integrated Circuit Operational Amplifiers", IEEE Journal of Solid-State Circuits, Dec. 1974 Vol. SC-9
2. Bowers, D.F., "A Comprehensive Simulation Macro-model for 'Current-Feedback' Operational Amplifiers", IEEE Proceedings, Vol. 137, Apr. 1990, pp. 137-145
3. Ryan, Al, "D-C Amplifier Noise Revisited", Analog Dialogue, Vol. 18, Num. 1, 1984, pp. 3-10
4. Tabor, Joe, "Macromodels Aid in Use of Current-Mode Feedback Amps", Electronic Products, Apr. 1992, pp. 25-30
5. Alexander, Mark, "AN-138 SPICE-Compatible Op Amp Macromodels", Precision Monolithics Inc., Application Note 138
6. Palouda, Hans, "Current Feedback Amplifiers Meet High Frequency Requirements", Powerconversion & Intelligent Motion, Sep. 1990, pp. 27-31
7. Franco, Sergio, *Design with Operational Amplifiers and Analog IC's*, McGraw-Hill, New York, NY, 1988
8. Williams, Arthur B., *Electronic Filter Design Handbook*, McGraw-Hill, New York, NY, 1981
9. Tuinenga, Paul W., *SPICE: A Guide to Circuit Simulation & Analysis Using PSpice®*, Prentice-Hall, 1992

Notes

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.



National Semiconductor Corporation
Americas
Email: support@nsc.com

www.national.com

National Semiconductor Europe

Fax: +49 (0) 180-530 85 86
Email: europe.support@nsc.com
Deutsch Tel: +49 (0) 69 9508 6208
English Tel: +44 (0) 870 24 0 2171
Français Tel: +33 (0) 1 41 91 8790

National Semiconductor Asia Pacific Customer Response Group

Tel: 65-2544466
Fax: 65-2504466
Email: ap.support@nsc.com

National Semiconductor Japan Ltd.

Tel: 81-3-5639-7560
Fax: 81-3-5639-7507