## Video Transmission Over Twisted Pair Wire

The circuits in *Figure 1* and *Figure 2* transmit NTSC video signals over twisted pair wire. They were designed and tested for transmitting video on inexpensive CAT-3 twisted pair wire. Even when transmitting on 1000 feet of wire, good quality color video was displayed on a monitor with an NTSC input. Both the transmit and receive circuits use the LMH6643 dual op-amp which has the proper bandwidth and slew rate for this application.

The Video Driver is shown in *Figure 1*. It converts a single-ended input signal from a camera or DVD player into a differential signal that drives the twisted-pair line. The input receives an NTSC composite video signal with  $1V_{PP}$  amplitude, and the output drives the twisted-pair with a  $2V_{PP}$  differential signal. A 50 $\Omega$  source resistor is in series with the outputs of both op-amps, matching the Video Driver output resistance to the twisted-pair characteristic impedance.



FIGURE 1. Twisted Pair Video Driver

In the receiver circuit of *Figure 2*, R2 is adjusted so that the overall gain of the system is unity (gain of the last op-amp is greater than one to compensate for signal loss). C1 and R1 provide a zero-pole function that compensates for attenuation of higher frequency signals in the twisted pair. The proper values for R1, C1, and R2 can be set by transmitting a 1V<sub>PP</sub> square wave with a frequency of about 300KHz, and adjusting these components for an optimized square wave at the output. This can be done with the following procedure. First, adjust R2 so that the square wave at the receiver output has an amplitude of  $1V_{PP}$  (with the output driving a 75 $\Omega$  load). Next, set C1 and R1 to optimize the risetime/ falltime and damping of this square wave. In the demonstration circuit that transmits video on 1000 feet of wire, R1 = 3.9k, C1 = 68pF, and R2 = 3.6k.

National Semiconductor Application Note 1240 John Bittner August 2002



# Video Transmission Over Twisted Pair Wire

### FIGURE 2. Twisted Pair Video Receiver

*Figure 3* shows the response of this system when transmitting a square wave. The transitions of the output signal have rise and fall times of 160ns with about 5% of overshoot. Note that 1,000 feet of twisted pair wire delays the input signal by  $1.4\mu s$ .



### FIGURE 3. System Square Wave Response

Differential gain and phase of the system was measured with an HP3577A Network Analyzer. A  $0.55V_{PP}$  sinewave test signal was applied to the input, and the gain and phase were measured at 3.58MHz (NTSC reference frequency). When the DC offset of the test signal changed from 0 to 1V, the gain changed -0.028dB (differential gain), and phase changed 0.23° (differential phase).

# AN-1240

### LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.

2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

AN-1240

National Semiconductor National Semiconductor Corporation Europe Americas Email: support@nsc.com www.national.com

Fax: +49 (0) 180-530 85 86 Email: europe.support@nsc.com Deutsch Tel: +49 (0) 69 9508 6208 English Tel: +44 (0) 870 24 0 2171 Français Tel: +33 (0) 1 41 91 8790

National Semiconductor Asia Pacific Customer **Response Group** Tel: 65-2544466 Fax: 65-2504466 Email: ap.support@nsc.com National Semiconductor Japan Ltd. Tel: 81-3-5639-7560 Fax: 81-3-5639-7507

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.