

LM3405A Demo Board

National Semiconductor
Application Note 1685
Alex Gao
October 2007



Introduction

The LM3405A demo board is configured to drive a series string of high power, high brightness LEDs at a forward current of 1A using the LM3405A constant current buck regulator. The board can accept a full input operating range of 3V to 22V. The converter output voltage adjusts as needed to maintain a constant current through the LED array. The LM3405A is a step-down regulator with an output voltage range extending from a $V_{O(MIN)}$ of 205mV (the reference voltage) to a $V_{O(MAX)}$ determined by the maximum duty cycle (typically 94%). It can drive up to 5 LEDs in series at 1A forward current, with the single LED forward voltage of approximately 3.7V (Typical of white, blue, and green LEDs using InGaN technology).

As shown in the demo board schematic circuit in *Figure 1*, the board is configured with the boost voltage derived from V_{IN} through a shunt zener (D3). This will ensure that the gate drive voltage $V_{BOOST} - V_{SW}$ falls in the recommended range of 2.5V to 5.5V when V_{IN} varies from 5V to 22V. When input voltage is in the range of 3V to 5V, the anode of boost diode (D2) should be directly connected to V_{IN} by replacing R3 with a jumper and removing C4 and D3, to obtain sufficient gate drive voltage for best performance.

Table 1 lists the bill of materials of this demo board. The measured performance characteristics and layout of this board are also included below. Additional Circuit Configuration Schematics section illustrates other possible circuit configurations of this board to accommodate various input and output requirements as discussed in the LM3405A datasheet.

Connecting to LED Array

The LM3405A demo board includes a female 6-position SIP connector **P1** as well as two standard 72mil turret connectors

for the cathode and anode connections of the LED array. Solid 18 or 20 gauge wire with about 1cm of insulation stripped away makes a convenient, solderless connection to **P1**.

Setting the LED Current

The default forward current I_F delivered to the LED array is 1.0A. To adjust this value the current setting resistor R1 can be changed according to the following equation:

$$I_F = V_{FB} / R1$$

The feedback voltage V_{FB} is regulated at 0.205V typically. The resistor R1 should be rated to handle the power dissipation of the LED current. R1 should be less than approximately 1Ω , to ensure that the LED current is kept above 200mA. If average LED currents of less than 200mA are desired, the EN/DIM pin should be used for PWM dimming.

PWM Dimming

The default connection of the PWM terminal is tied to V_{IN} through a 100k Ω resistor (R2) to enable the chip, which allows the set current to flow through the LEDs continuously. This PWM terminal can also be connected to a periodic pulse signal at different frequencies and/or duty cycle for PWM dimming. A typical LED current waveform in PWM dimming mode is shown in *Figure 2*. *Figure 3* shows the average LED current versus duty cycle of various dimming signal frequencies. Due to an approximately 100 μ s delay between the dimming signal and LED current, the dimming ratio reduces dramatically if the applied PWM dimming frequency is greater than 5kHz.



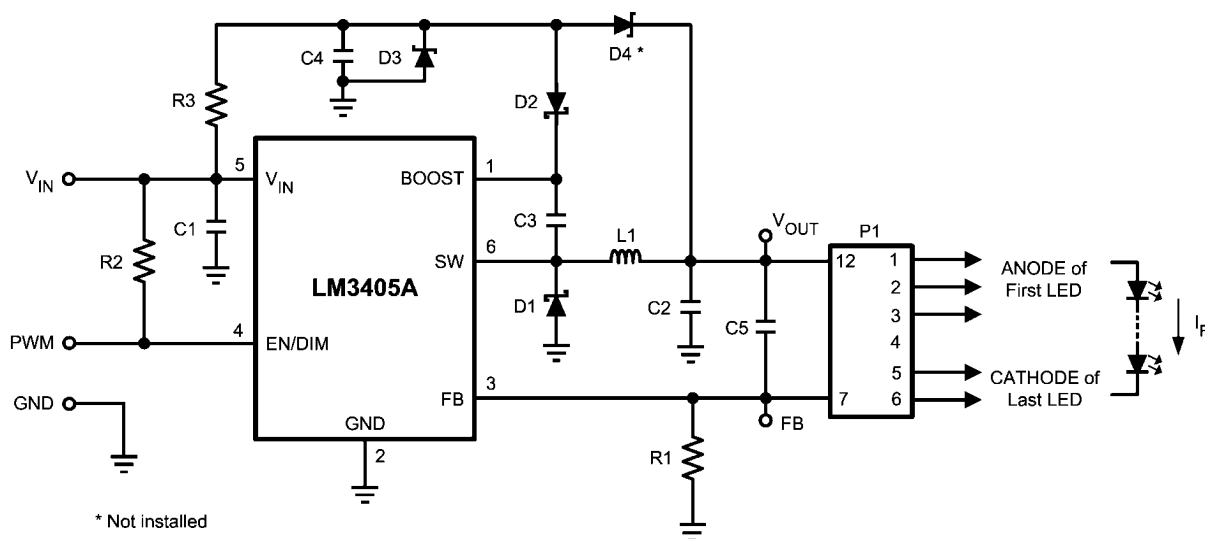


FIGURE 1. LM3405A Demo Board Schematic

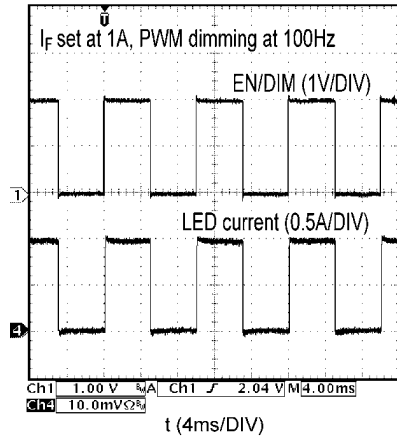

30031802

FIGURE 2. PWM Dimming of LEDs

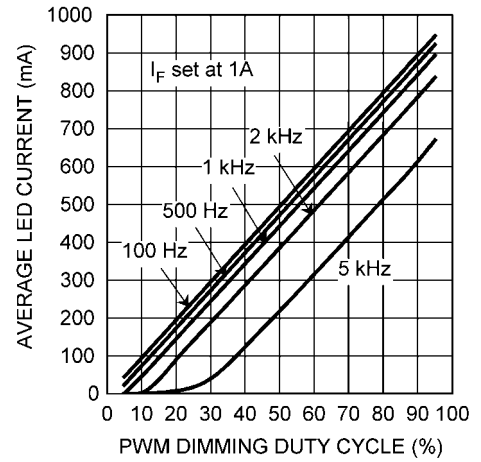


30031803

FIGURE 3. Average LED Current versus Duty Cycle of PWM Dimming Signal at PWM Terminal


TABLE 1. Bill of Materials

Part ID	Part Value	Part Number	Manufacturer
U1	1A constant current buck regulator, TSOT-6	LM3405A	National Semiconductor
L1	10 μ H, 1.3A, 53m Ω , 6.0 x 6.0 x 2.8mm	SLF6028T-100M1R3-PF	TDK
C1	10 μ F, 25V, X5R, 1206	GRM31CR61E106KA12L	Murata
C2	1 μ F, 35V, X7R, 1206	GMK316BJ105KL-T	Taiyo Yuden
C3	0.01 μ F, 16V, X7R, 0805	0805YC103KAT2A	AVX
C4	0.1 μ F, 16V, X7R, 0805	GRM219R71C104KA01D	Murata
C5	1 μ F, 35V, X7R, 0805	GMK212BJ105KG-T	Taiyo Yuden
D1	Schottky, 40V, 1A, SMA	SS14-E3/61T	Vishay
D2	Schottky, 30V, 200mA, SOD-323	BAT54WS-TP	Micro Commercial Co.
D3	5.1V, 0.35W, SOT23	MMBZ5231B-7-F	Diodes
D4	Not installed		
R1	0.5W, 0.2 Ω , 1%, 2010	WSL2010R2000FEA	Vishay
R2	100k Ω , 1/8W, 1%, 0805	CRCW0805100KFKEA	Vishay
R3	1.0k Ω , 1%, 1/8W, 0805	CRCW08051K00FKEA	Vishay
P1	6-position connector	5535676-5	Tyco/AMP


Typical Performance Characteristics

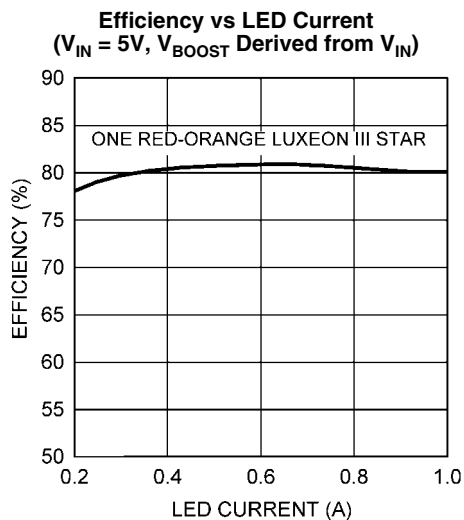


30031804

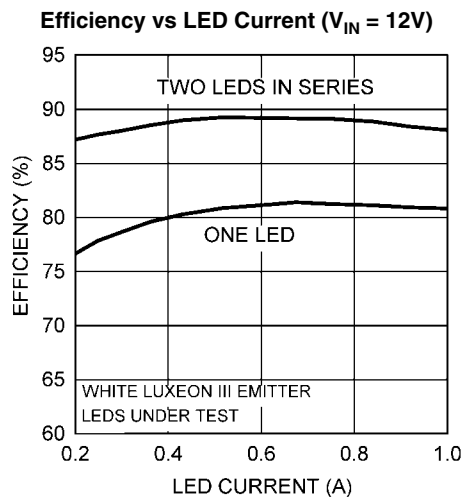


30031805

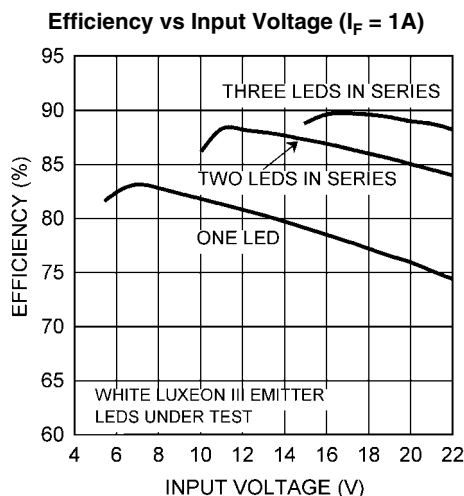


30031806

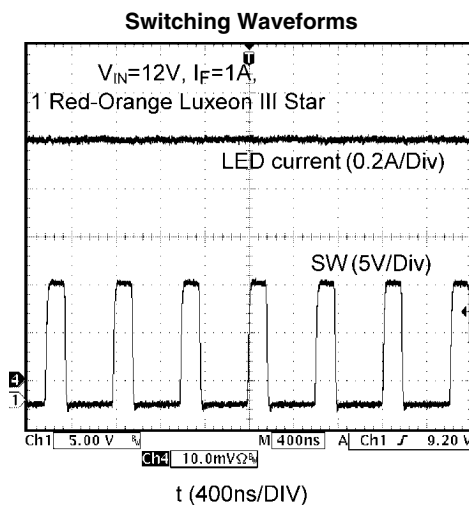

30031807

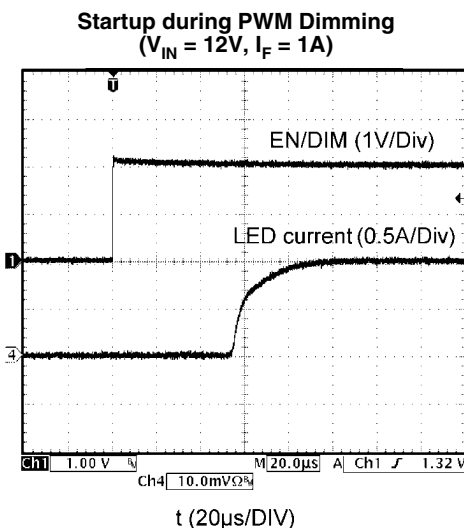


30031808

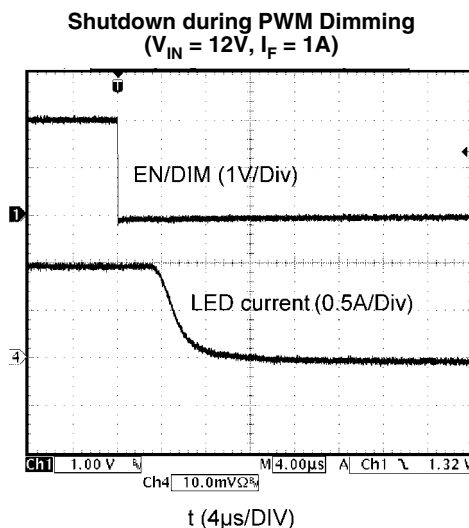


30031809

Layout

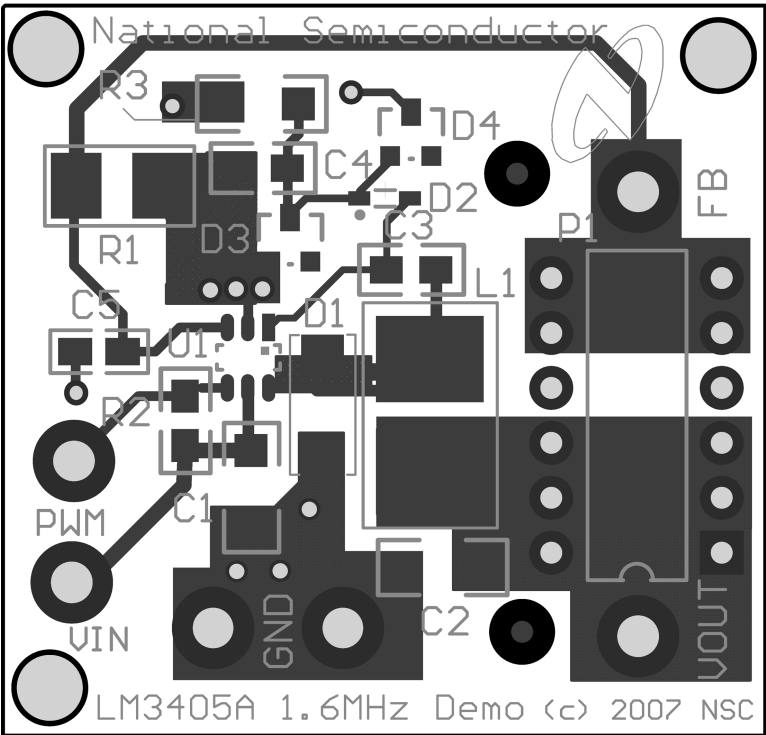


Top Layer and Top Overlay

30031810

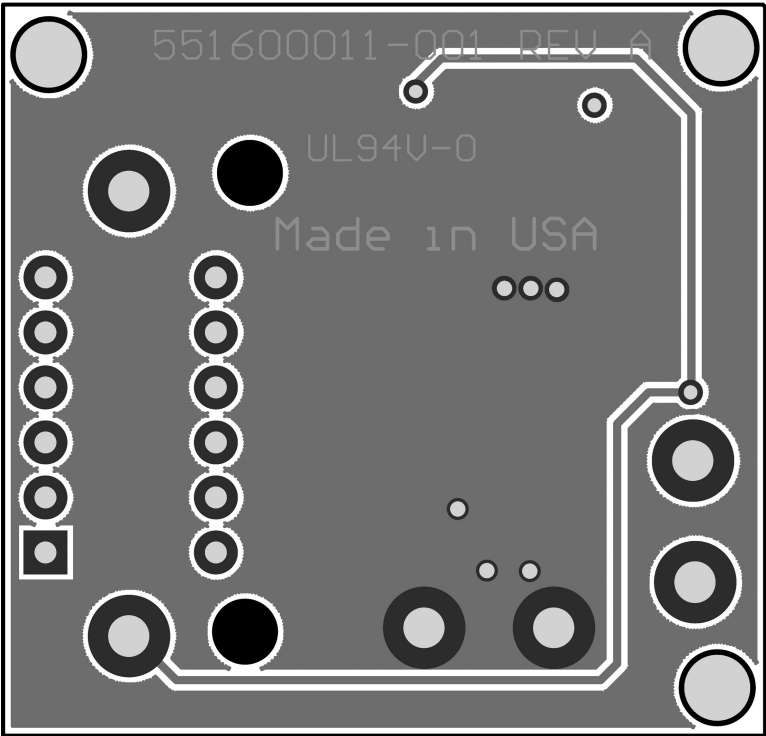


Bottom Layer and Bottom Overlay

30031811

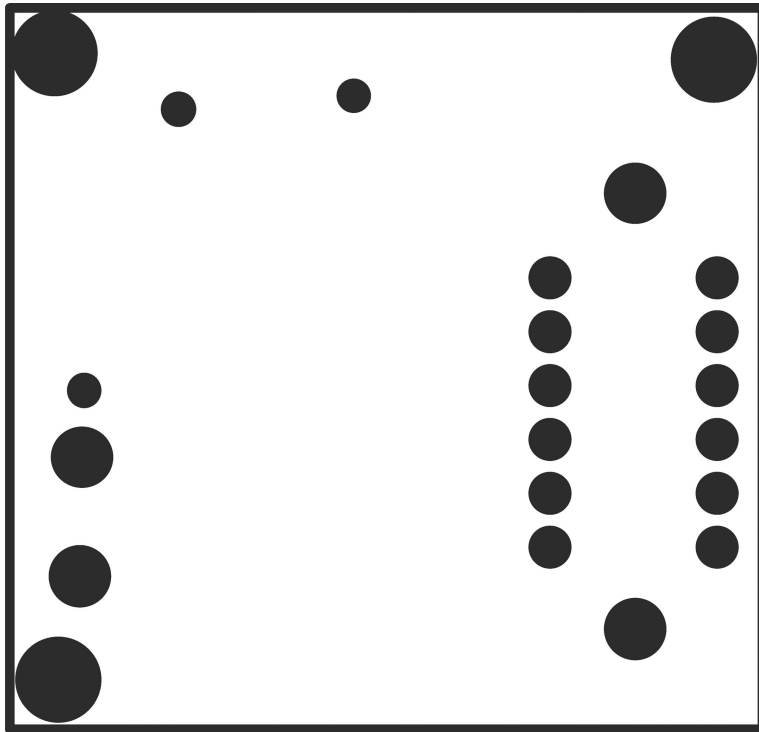

30031812


Internal Plane 1 (GND)

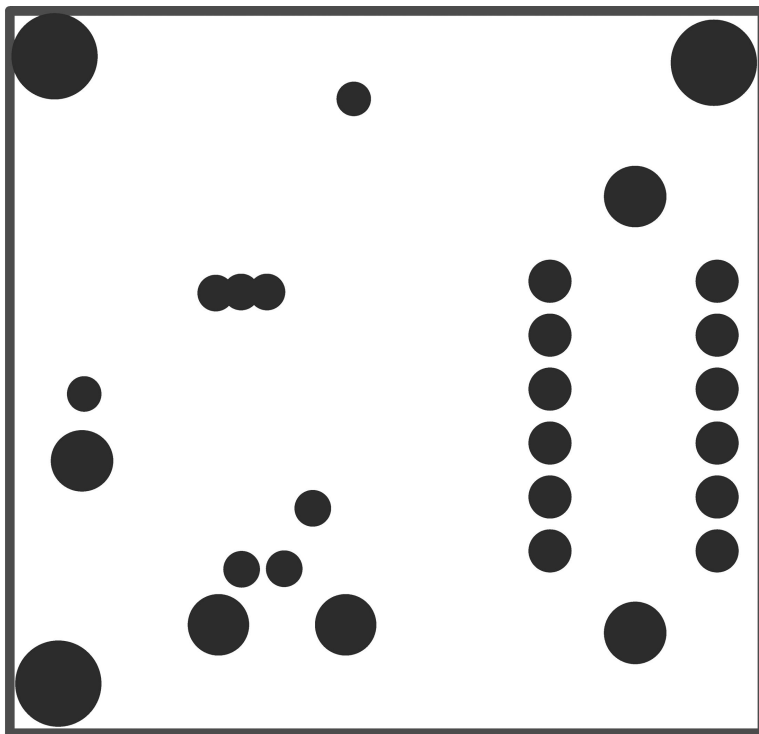

30031813


Internal Plane 2 (V_{IN})

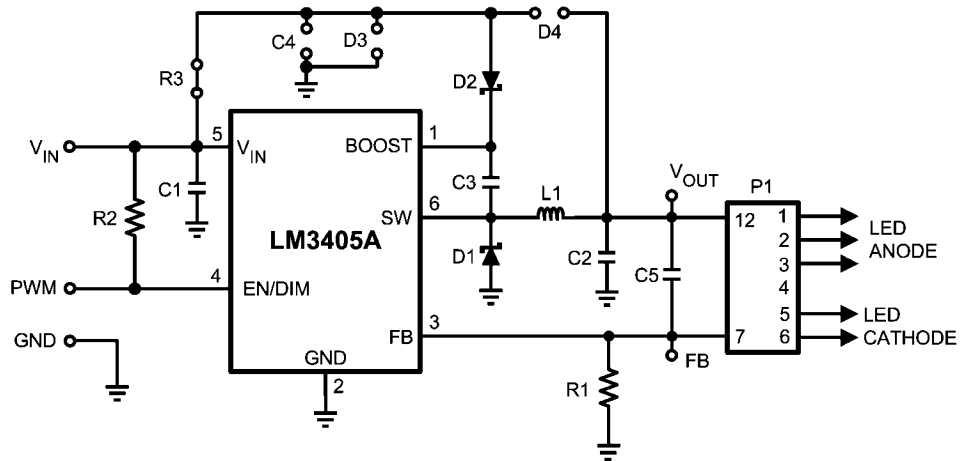Additional Circuit Configuration Schematics




V_{BOOST} Derived from V_{IN}

30031814

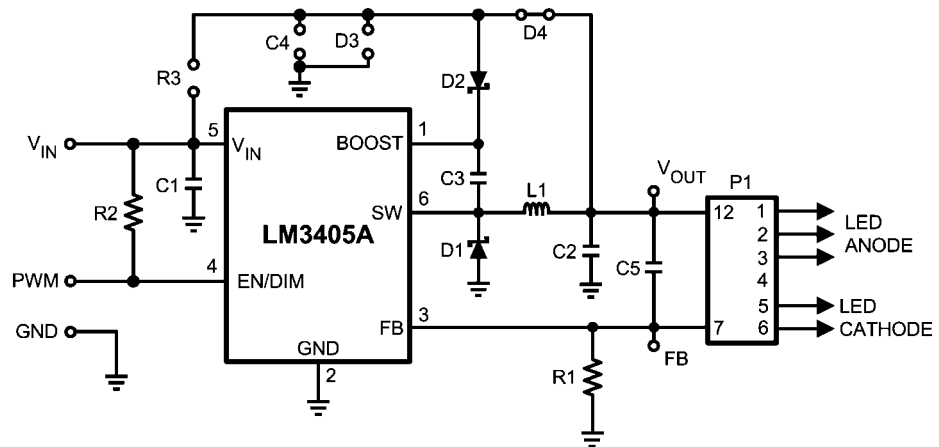


V_{BOOST} Derived from V_{OUT}

30031815

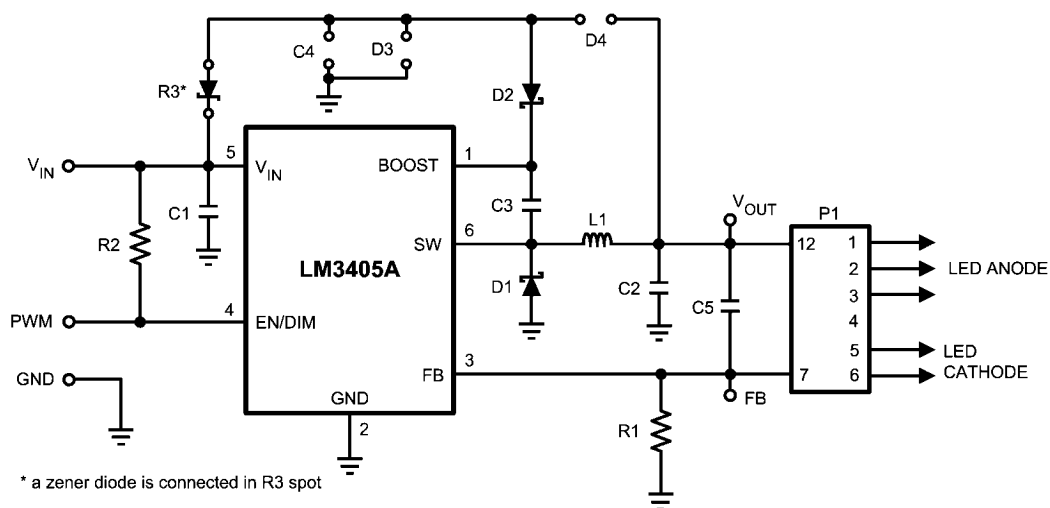

30031816

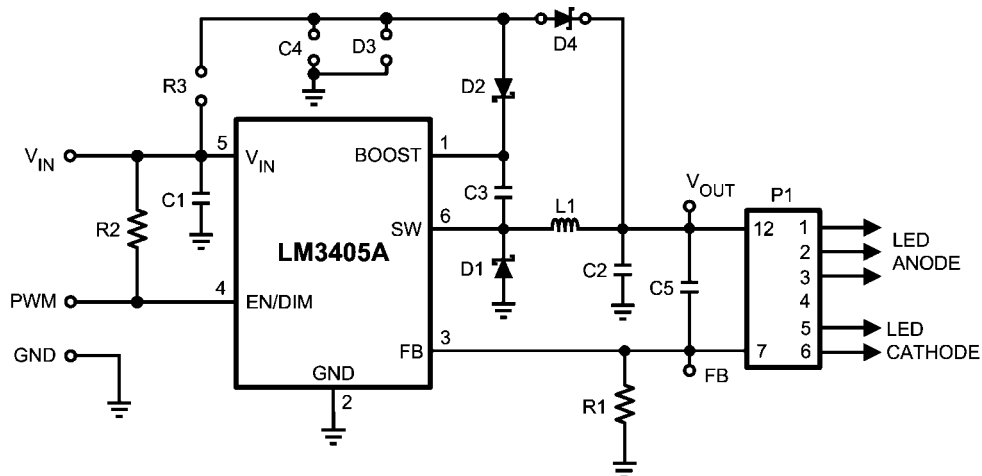 V_{BOOST} Derived from V_{IN} through a Series Zener Diode

30031817

 V_{BOOST} Derived from V_{OUT} through a Series Zener Diode

Notes

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

Copyright© 2007 National Semiconductor Corporation

For the most current product information visit us at www.national.com



**National Semiconductor
Americas Customer
Support Center**
Email:
new.feedback@nsc.com
Tel: 1-800-272-9959

**National Semiconductor Europe
Customer Support Center**
Fax: +49 (0) 180-530-85-86
Email: europe.support@nsc.com
Deutsch Tel: +49 (0) 69 9508 6208
English Tel: +49 (0) 870 24 0 2171
Français Tel: +33 (0) 1 41 91 8790

**National Semiconductor Asia
Pacific Customer Support Center**
Email: ap.support@nsc.com

**National Semiconductor Japan
Customer Support Center**
Fax: 81-3-5639-7507
Email: jpn.feedback@nsc.com
Tel: 81-3-5639-7560