

# 5A LM20k Reference Designs

National Semiconductor  
Application Note 1752  
Daniel Tennant and Dennis Hudgins  
November 13, 2007



## Introduction

The LM20125, and LM20145 are a full-featured family of high performance 5A synchronous buck converters. These devices are tailored to operate over an input voltage range of 2.95V to 5.5V and each can be optimized to meet many different performance requirements. The LM20125 operates at a fixed frequency and only requires 11 components to generate a solution. The LM20145 is similar to the LM20125 except the frequency of the device can be varied from 250 kHz to 750 kHz with an external resistor. This gives the power supply designer the flexibility to trade-off inductor size, efficiency, as well as AC performance.

The reference designs discussed will show how the 5A devices can be optimized for size, efficiency and transient response. The trade-offs made for each design will be discussed as well as possible tweaks to interchange the various 5A devices. Test results for including efficiency, output voltage ripple, and transient response will be shown for each design

## Solution Optimized for Size and Efficiency

To minimize the switching losses and reduce the solution size the LM20125 device was selected. This device operates at a fixed frequency of 500kHz keeping the switching losses down; while also allowing use of a relatively small inductor. Therefore, this solution can offer both small size, as well as, high efficiency.

### INDUCTOR SELECTION

As per the datasheet recommendations, the inductor value should initially be chosen to give a peak-to-peak ripple current equal to roughly 30% of the maximum output current. The peak-to-peak inductor ripple current can be calculated by the equation:

$$\Delta I_{P-P} = \frac{(V_{IN} - V_{OUT}) \times D}{L \times f_{SW}} \quad (1)$$

Rearranging the above equation and solving for the inductance reveals that for this application ( $V_{IN} = 5V$ ,  $V_{OUT} = 3.3V$ ,  $f_{SW} = 500 \text{ kHz}$ , and  $I_{OUT} = 5A$ ) the nominal inductance value is roughly 1.5  $\mu H$ . Once an inductance value is calculated, an actual inductor needs to be selected based on a trade-off between physical size, efficiency, and current carrying capability. Since the purpose of this design is to maximize the efficiency and keep the solution size small the inductor values

smaller than 1.5  $\mu H$  can be examined, provided the output current plus one-half the peak to peak ripple current does not exceed the device current limit. Examining several inductor vendors a TDK SPM6530T-1R5M100 inductor was selected. This 1.5  $\mu H$  inductor results in a peak-to-peak ripple current of 1.5A when doing a 5V to 3.3V conversion. For the LM20125 demo board, a TDK SPM6530T-1R5M100 inductor offers a good balance between efficiency (9.7 m $\Omega$  DCR), size, and saturation current rating (10A  $I_{SAT}$  rating).

### OUTPUT CAPACITOR SELECTION

The value of the output capacitor in a buck regulator influences the voltage ripple that will be present on the output voltage, as well as the large signal output voltage response to a load transient. Given the peak-to-peak inductor current ripple (which can be calculated using equation 1) the output voltage ripple can be approximated by the equation:

$$\Delta V_{OUT} = \Delta I_{P-P} \times \left[ R_{ESR} + \frac{1}{8 \times f_{SW} \times C_{OUT}} \right] \quad (2)$$


The variable  $R_{ESR}$  above refers to the ESR of the output capacitor. As can be seen in the above equation, the ripple voltage on the output can be divided into two parts, one of which is attributed to the AC ripple current flowing through the ESR of the output capacitor and another due to the AC ripple current actually charging and discharging the output capacitor. The output capacitor also has an effect on the amount of droop that is seen on the output voltage in response to a load transient event.

For this design a TDK 100  $\mu F$  ceramic capacitor is selected for the output capacitor to provide good transient and DC performance in a relatively small package. From the technical specifications of this capacitor, the ESR at the 500 kHz switching frequency is roughly 2 m $\Omega$ , and the effective in-circuit capacitance is approximately 45  $\mu F$  (reduced from 100  $\mu F$  due to the 3.3V DC bias). With these values, the peak-to-peak voltage ripple on the output when operating from a 5V input can be calculated to be 8 mV.
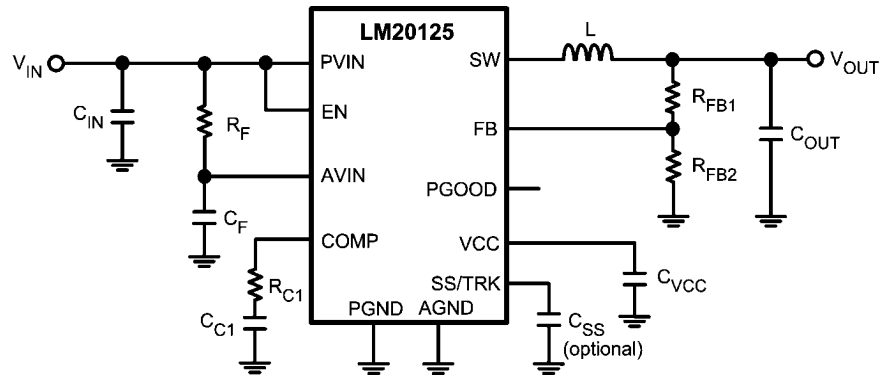
### COMPENSATION SELECTION

The compensation network was selected using the excel design tool (available online) to give a crossover frequency of 59 kHz. For this target crossover frequency, operating conditions, and filter components the excel design tool suggested a value of  $C_{C1}$  of 1.2 nF and a value of  $R_{C1}$  of 19.6 k $\Omega$ .

The final schematic for a 5V to 3.3V conversion is shown in Figure 1.




30044543


FIGURE 1. 3.3V Output Solution Optimized for Size and Efficiency

High Efficiency Bill of Materials ( $V_{IN} = 5V$ ,  $V_{OUT} = 3.3V$ ,  $I_{OUT(MAX)} = 5A$ )

| Designator | Description                  | Part Number       | Manufacturer           | Qty |
|------------|------------------------------|-------------------|------------------------|-----|
| U1         | Synchronous Buck Regulator   | LM20125           | National Semiconductor | 1   |
| $C_{IN}$   | 47 $\mu$ F, 1206, X5R, 6.3V  | C3216JB0J476M     | TDK                    | 1   |
| $C_{OUT}$  | 100 $\mu$ F, 1206, X5R, 6.3V | C3225X5R0J107M    | TDK                    | 1   |
| L          | 1.5 $\mu$ H, 9.7m $\Omega$   | SPM6530T-1R5M100  | TDK                    | 1   |
| $R_F$      | 1 $\Omega$ , 0402            | CRCW04021R0J-e3   | Vishay-Dale            | 1   |
| $C_F$      | 1 $\mu$ F, 0402, X7R, 10V    | GRM155R61A105KE15 | Murata                 | 1   |
| $C_{VCC}$  | 1 $\mu$ F, 0402, X7R, 10V    | GRM155R61A105KE15 | Murata                 | 1   |
| $R_{C1}$   | 19.6k $\Omega$ , 0402        | CRCW06031962F     | Vishay-Dale            | 1   |
| $C_{C1}$   | 1.2nF, 0402, X7R, 25V        | VJ0603Y122KXA     | Vishay-Vitramon        | 1   |
| $C_{SS}$   | 33nF, 0402, X7R, 25V         | VJ0402G333KXJA    | Vishay-Vitramon        | 1   |
| $R_{FB1}$  | 30.9k $\Omega$ , 0402        | CRCW04023092F-e3  | Vishay-Dale            | 1   |
| $R_{FB2}$  | 10k $\Omega$ , 0402          | CRCW04021002F-e3  | Vishay-Dale            | 1   |

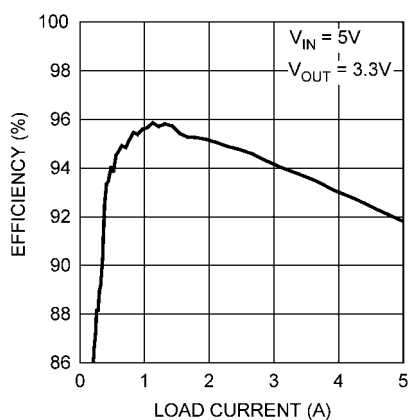


30044548

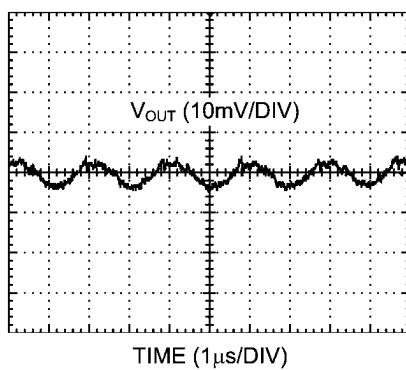FIGURE 2. Efficiency vs  $I_{OUT}$ 

30044549

FIGURE 3. Output Voltage Ripple

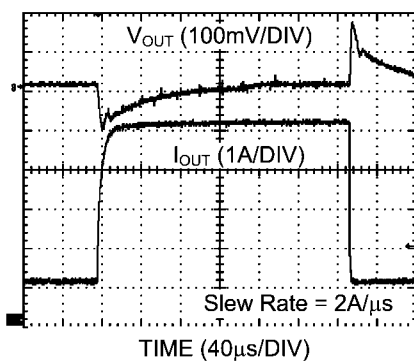

30044550

FIGURE 4. Transient Response

## Solution Optimized for Transient Response

To optimize the transient response the switching frequency should be as high as possible. A high switching frequency allows the crossover frequency to be maximized and the inductor size to be minimized. A small inductor permits also permits the inductor current to quickly ramp during a load step change.

### INDUCTOR SELECTION

The inductor should be sized for approximately 30% ripple current. For  $V_{IN} = 5V$ ,  $V_{OUT} = 1.2V$ ,  $f_{SW} = 750\text{ kHz}$ , and  $I_{OUT} = 5A$ , the ideal inductance value can be calculated from equation 1 to be of  $0.81\text{ }\mu\text{H}$ . Once an inductance value is calculated, an actual inductor needs to be selected based on a trade-off between physical size, efficiency, and current carrying capability. Since the purpose of this design is to select the smallest value inductor, values smaller than  $0.81\text{ }\mu\text{H}$  can be examined as long as the output current plus one-half the peak to peak ripple current does not exceed the device current limit. Examining several inductor vendors a TDK SPM6530T-1R0M120 inductor was selected. This  $1\text{ }\mu\text{H}$  inductor results in a peak-to-peak ripple current of  $1.22\text{ A}$  when

the converter is operating from  $5V$  and  $3.3V$ . For this design, the TDK SPM6530T-1R0M120 inductor offers a good balance between efficiency ( $7.1\text{ m}\Omega\text{ DCR}$ ), size, and saturation current rating ( $12A\text{ }I_{SAT}$  rating).


### OUTPUT CAPACITOR SELECTION

A Sanyo  $680\text{ }\mu\text{F}$  POSCAP capacitor with  $18\text{ m}\Omega$  of series resistance (ESR) is selected for the output capacitor to provide good transient and DC performance in a relatively small package. To further reduce the output voltage ripple a  $47\text{ }\mu\text{F}$  ceramic capacitor is placed in parallel with the Sanyo POSCAP.
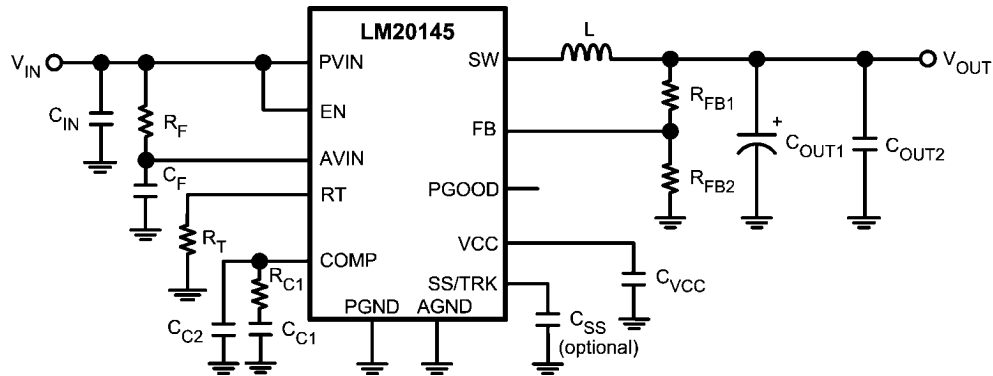
### COMPENSATION SELECTION

The compensation network was selected using the excel design tool (available online) to give a crossover frequency of  $91\text{ kHz}$ . For this target crossover frequency, operating conditions, and filter components a value for  $C_{C1}$  of  $0.68\text{ nF}$  and a value for  $R_{C1}$  of  $82.5\text{ k}\Omega$  were selected. Since the output capacitor value and ESR are large an additional capacitor  $C_{C2}$  is recommended. For this design  $C_{C2}$  is  $27\text{ pF}$ .

The final schematic for a  $5V$  to  $1.2V$  or  $3.3V$  to  $1.2V$  conversion is shown in Figure 1.



30044551

FIGURE 5. 1.2V Output Solution Optimized for Load Transients

Transient Response Bill of Materials ( $V_{IN} = 5V$ ,  $V_{OUT} = 1.2V$ ,  $I_{OUT(MAX)} = 5A$ ,  $f_{SW} = 750\text{ kHz}$ )

| Designator | Description                                     | Part Number       | Manufacturer           | Qty |
|------------|---|-------------------|------------------------|-----|
| U1         | Synchronous Buck Regulator                      | LM20145           | National Semiconductor | 1   |
| $C_{IN}$   | $47\text{ }\mu\text{F}$ , 1206, X5R, 6.3V       | C3216JB0J476M     | TDK                    | 1   |
| $C_{OUT1}$ | $680\text{ }\mu\text{F}$ , D4D, POSCAP, 6.3V    | 6TPE680MIL        | Sanyo                  | 1   |
| $C_{OUT2}$ | $47\text{ }\mu\text{F}$ , 1206, X5R, 6.3V       | C3216JB0J476M     | TDK                    | 1   |
| L          | $1.0\text{ }\mu\text{H}$ , $7.1\text{ m}\Omega$ | SPM6530T-1R0M120  | TDK                    | 1   |
| $R_F$      | $1\text{ }\Omega$ , 0603                        | CRCW06031R0J-e3   | Vishay-Dale            | 1   |
| $C_F$      | $1\text{ }\mu\text{F}$ , 0603, X7R, 10V         | GRM188R71A105KA01 | Murata                 | 1   |
| $C_{VCC}$  | $1\text{ }\mu\text{F}$ , 0603, X7R, 10V         | GRM188R71A105KA01 | Murata                 | 1   |
| $R_{C1}$   | $82.5\text{ k}\Omega$ , 0603                    | CRCW06038252F-e3  | Vishay-Dale            | 1   |
| $C_{C1}$   | $0.68\text{ nF}$ , 0603, X7R, 25V               | VJ0603Y681KXXA    | Vishay-Vitramon        | 1   |
| $C_{C2}$   | $27\text{ pF}$ , 0603, 50V, COG                 | GRM18885C1H2701   | Murata                 | 1   |
| $C_{SS}$   | $33\text{ nF}$ , 0603, X7R, 25V                 | VJ0603Y333KXXA    | Vishay-Vitramon        | 1   |
| $R_{FB1}$  | $4.99\text{ k}\Omega$ , 0603                    | CRCW06034992F-e3  | Vishay-Dale            | 1   |

| Designator       | Description  | Part Number      | Manufacturer | Qty |
|------------------|--------------|------------------|--------------|-----|
| R <sub>FB2</sub> | 10kΩ, 0603   | CRCW06031002F-e3 | Vishay-Dale  | 1   |
| R <sub>T</sub>   | 48.7kΩ, 0603 | CRCW06034872F-e3 | Vishay-Dale  | 1   |

The calculated component PCB area for this design is 134 mm<sup>2</sup>. The efficiency vs.  $I_{OUT}$ , output voltage ripple, and transient response are shown below for this solution.

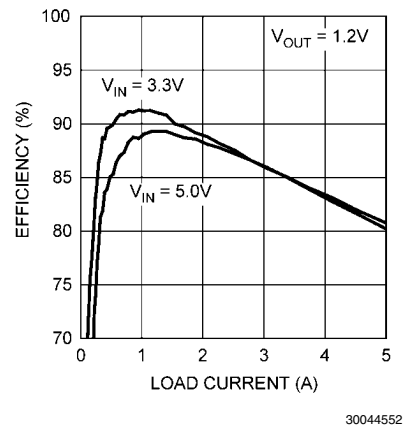


FIGURE 6. Efficiency vs  $I_{OUT}$

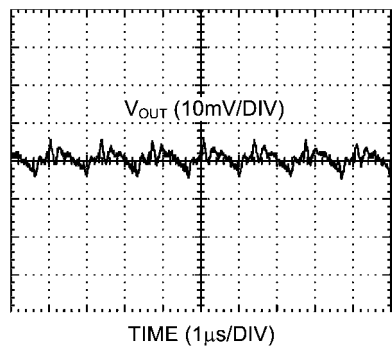


FIGURE 7. Output Voltage Ripple

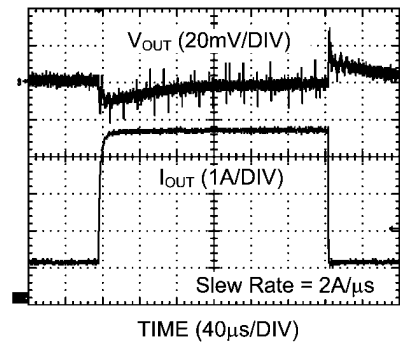


FIGURE 8. Transient Response

# Notes

For more National Semiconductor product information and proven design tools, visit the following Web sites at:

| Products                       |  | Design Support          |  |
|--------------------------------|--|-------------------------|--|
| Amplifiers                     | <a href="http://www.national.com/amplifiers">www.national.com/amplifiers</a>   | WEBENCH                 | <a href="http://www.national.com/webench">www.national.com/webench</a>             |
| Audio                          | <a href="http://www.national.com/audio">www.national.com/audio</a>             | Analog University       | <a href="http://www.national.com/AU">www.national.com/AU</a>                       |
| Clock Conditioners             | <a href="http://www.national.com/timing">www.national.com/timing</a>           | App Notes               | <a href="http://www.national.com/appnotes">www.national.com/appnotes</a>           |
| Data Converters                | <a href="http://www.national.com/adac">www.national.com/adac</a>               | Distributors            | <a href="http://www.national.com/contacts">www.national.com/contacts</a>           |
| Displays                       | <a href="http://www.national.com/displays">www.national.com/displays</a>       | Green Compliance        | <a href="http://www.national.com/quality/green">www.national.com/quality/green</a> |
| Ethernet                       | <a href="http://www.national.com/ethernet">www.national.com/ethernet</a>       | Packaging               | <a href="http://www.national.com/packaging">www.national.com/packaging</a>         |
| Interface                      | <a href="http://www.national.com/interface">www.national.com/interface</a>     | Quality and Reliability | <a href="http://www.national.com/quality">www.national.com/quality</a>             |
| LVDS                           | <a href="http://www.national.com/lvds">www.national.com/lvds</a>               | Reference Designs       | <a href="http://www.national.com/refdesigns">www.national.com/refdesigns</a>       |
| Power Management               | <a href="http://www.national.com/power">www.national.com/power</a>             | Feedback                | <a href="http://www.national.com/feedback">www.national.com/feedback</a>           |
| Switching Regulators           | <a href="http://www.national.com/switchers">www.national.com/switchers</a>     |                         |  |
| LDOs                           | <a href="http://www.national.com/ldo">www.national.com/ldo</a>                 |                         |  |
| LED Lighting                   | <a href="http://www.national.com/led">www.national.com/led</a>                 |                         |  |
| PowerWise                      | <a href="http://www.national.com/powerwise">www.national.com/powerwise</a>     |                         |  |
| Serial Digital Interface (SDI) | <a href="http://www.national.com/sdi">www.national.com/sdi</a>                 |                         |  |
| Temperature Sensors            | <a href="http://www.national.com/tempsensors">www.national.com/tempsensors</a> |                         |  |
| Wireless (PLL/VCO)             | <a href="http://www.national.com/wireless">www.national.com/wireless</a>       |                         |  |

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

## LIFE SUPPORT POLICY

**NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION.** As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

Copyright© 2007 National Semiconductor Corporation

For the most current product information visit us at [www.national.com](http://www.national.com)



**National Semiconductor  
Americas Customer  
Support Center**  
Email:  
[new.feedback@nsc.com](mailto:new.feedback@nsc.com)  
Tel: 1-800-272-9959

**National Semiconductor Europe  
Customer Support Center**  
Fax: +49 (0) 180-530-85-86  
Email: [europe.support@nsc.com](mailto:europe.support@nsc.com)  
Deutsch Tel: +49 (0) 69 9508 6208  
English Tel: +49 (0) 870 24 0 2171  
Français Tel: +33 (0) 1 41 91 8790

**National Semiconductor Asia  
Pacific Customer Support Center**  
Email: [ap.support@nsc.com](mailto:ap.support@nsc.com)

**National Semiconductor Japan  
Customer Support Center**  
Fax: 81-3-5639-7507  
Email: [jpn.feedback@nsc.com](mailto:jpn.feedback@nsc.com)  
Tel: 81-3-5639-7560