

# A Simple Method to Reduce DC Power Consumption in CDMA RF Power Amplifiers Through the LMV225 and an Efficient Switcher

## Introduction

The need for higher wireless data rates is driving the migration of 2G to 3G mobile communication systems. The higher data rates in these systems impose additional performance constraints on the radio design of mobile phones.

In order to achieve the highest bandwidth efficiency of the allocated spectrum, these 3rd generation mobile communication systems use spectrum efficient linear modulation schemes, such as Quadrature Phase Shift Keying, 8-Phase Shift Keying and Quadrature Amplitude Modulation.

In IS-95 and CDMA2000 systems, the RF power amplifier typically operates at 6 dB to 40 dB back-off from the peak power or 1 dB compression point. (This means that it operates from 6 dB to 40 dB below the 1 dB compression point.) Consequently, the RF power amplifier operates with very low efficiency most of the time and is one of the most power consuming components in a handset. Studies show that the RF power amplifier consumes as much as 20% to 40% of the battery energy in regular phone operation.

Now, we can see that it is supremely important to reduce the power consumption of RF power amplifiers in order to achieve a long battery life or 'talk time' in a mobile phone.

This article presents a simple power tracking technique for efficiency enhancement in CDMA RF power amplifiers. This technique involves the use of a linear-in-dB RF power detector and a DC-DC converter switch. This enhancement scheme switches the DC supply voltage,  $V_{CC}$ , of an RF power amplifier into two different levels through a DC-DC converter. National Semiconductor's RF power detector LMV225 determines the supply voltage of the RF power amplifier. An off-the-shelf CDMA2000 RF power amplifier

National Semiconductor  
Application Note 1438  
Barry Yuen  
January 2006




can be used in this technique to improve the energy efficiency of the mobile phone.

## RF Power Amplifier

An RF power amplifier is the centerpiece of this application. An off-the-shelf CDMA2000 RF power amplifier, such as the SKY77152, is used in the evaluation. It can have more than 40% power added efficiency near the 1 dB compression point as specified in the datasheet.

In a CDMA RF power amplifier there are usually two supply voltage pins,  $V_{CC}$  and  $V_{BIAS}$ , as shown in *Figure 1*. There is also one reference voltage pin, which is usually called  $V_{REF}$ . The  $V_{REF}$  has to be at 2.85V in all conditions. The power amplifier can be turned off by setting  $V_{REF}$  equal to ground level. Since most of the CDMA RF power amplifiers have two operation modes, High Power Mode and Low Power Mode, a  $V_{CONT}$  pin is used to set the operation mode of the power amplifier. When the RF output power is in the high level, the CDMA RF power amplifier needs to operate in High Power Mode to keep the right distortion performance. The CDMA RF power amplifier can be switched to Low Power Mode if the output signal level is relatively low. However, an undesired side effect is that the signal path phase shifts have too much difference between the two paths. This may cause problems in base-band processing and correction.


*Figure 2* depicts the typical  $P_{OUT}$  vs.  $P_{IN}$  performance of a CDMA RF power amplifier when the DC supply voltages,  $V_{CC}$  and  $V_{BIAS}$ , are lowered. It shows that output RF power can still be obtainable by reducing the DC supply voltage of the RF power amplifier.

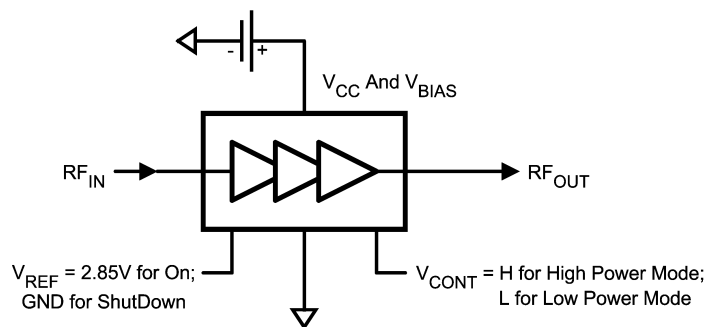

20178401

FIGURE 1. CDMA RF Power Amplifier

## RF Power Amplifier (Continued)

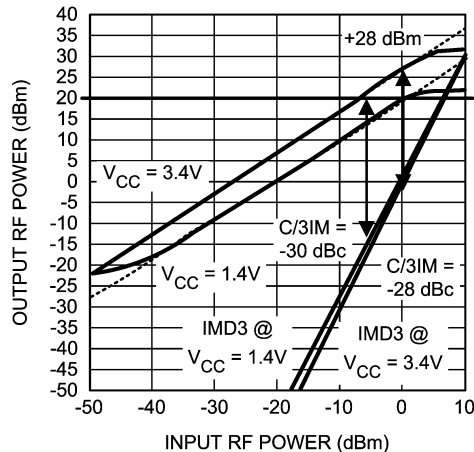

20178402

FIGURE 2. Linearity of CDMA RF Power Amplifier

### Power Added Efficiency

The DC-to-RF efficiency or Power Added Efficiency, PAE, is defined by

EQ\_1:

$$PAE = \frac{P_{OUT} - P_{IN}}{P_{DC}} \cdot 100\%$$

The DC power consumption is defined by

EQ\_2:

$$P_{DC} = V_{CC} \cdot I_{CC}$$


Although the peak DC-to-RF efficiency of the PA occurs at the peak output power level as specified by all RF power amplifier manufacturers, the RF power amplifier itself rarely operates at this peak power level. Nevertheless, the peak power added efficiency contributes significantly to minimizing power dissipation for heat constraints in the handset. On the other hand, the PAE of the RF power amplifier goes downhill when the output RF power is lower.

In battery powered cellular phones, the output RF power probability distribution, as depicted in Figure 3, should be considered to estimate the average efficiency of the mobile system.

As Figure 3 shows, most of the time the RF power amplifier in a handset is operating at  $P_{OUT} = +15$  dBm and below for an IS-95 handset. Therefore, it makes sense to improve the PAE of RF power amplifiers at small signal levels.

EQ\_1 and EQ\_2 reveal the idea that the DC power consumption  $P_{DC}$  can be reduced by lowering the supply voltage of the RF power amplifier.

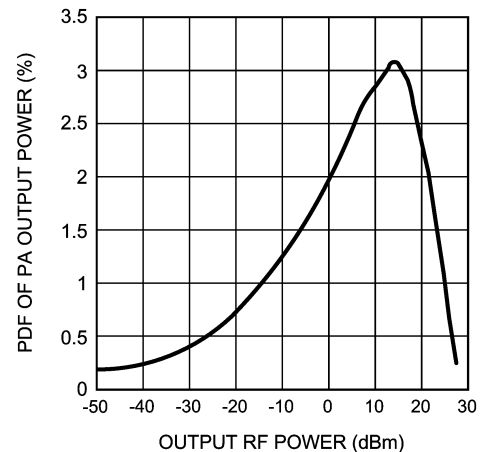It may sound very simple to improve the PAE of an RF power amplifier; however, there are a few major specifications that need to be considered while reducing the supply voltage of the RF power amplifier. These include the ACPR, the EVM and the switching time from one supply voltage level to another.



20178404

FIGURE 3. RF Output Power Distribution

## Power Added Efficiency (Continued)

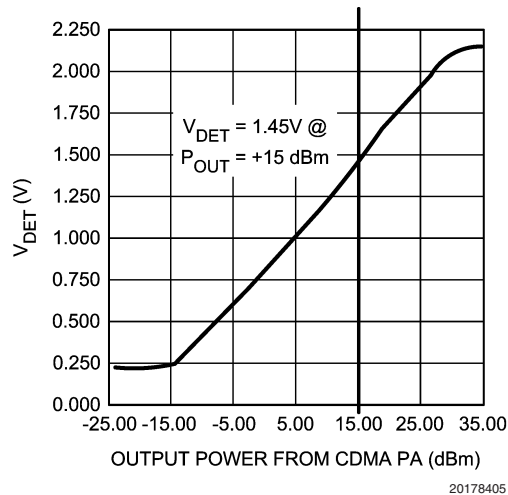


FIGURE 4. LMV225 Detected Voltage vs.  $P_{OUT}$

TABLE 1. Adjacent Channel Power Rejection

Air Interface	Frequency	Channel Bandwidth	Offset Frequency @ ACPR1	Offset Frequency @ ACPR2	Measurement Resolution Bandwidth
IS-95	824–849 MHz	1.25 MHz	$\pm 885 \text{ KHz}$	$\pm 1.98 \text{ MHz}$	30 KHz
PCS	1850–1910 MHz	1.25 MHz	$\pm 1.25 \text{ MHz}$	$\pm 1.98 \text{ MHz}$	30 KHz

ACPR1 = -42 dBc and ACPR2 = -54 dBc

## Power Detector

The RF power detector, which uses the RF output signal, generates a rectified DC voltage that determines the output voltage of a DC-DC converter or switcher.

In this application, National Semiconductor's LMV225 is chosen as an example since it provides 40 dB linear-in-dB detection range from 0 dBm down to -40 dBm.

RF power control in handsets is essential to ensure that the CDMA system operates smoothly. Since all users share the same radio frequency band, 1.25 MHz in IS-95, then each user appears to others as random noise. The power of an individual user must, therefore, be carefully controlled to prevent any one user from unnecessarily interfering with the others who share the same radio frequency band.

National's LMV225, as used in the suggested application block diagram in Figure 6, provides two different functions. The first function is related to the output RF power control as mentioned previously. The second function is to determine the supply voltage of the RF power amplifier. The next section of this article is going to deal with the second function of the LMV225.

## Switcher or DC/DC Converter

In general, a switcher used for this application has a Pulse Width Modulation (PWM) Mode and a Bypass Mode. The switcher normally operates in PWM mode to improve the efficiency of the handset. In PWM mode, the programmable output voltage is a function of  $V_{CON}$ . Equation EQ\_3 shows the relationship between the programmable output (SW) and control voltage ( $V_{CON}$ ) of LM3200.

## Adjacent Channel Power Rejection

The Adjacent Channel Power Rejection, known as ACPR, is defined as the ratio of the average power in a specific offset frequency to the average power in the transmitted frequency. Table 1 shows the performance requirements from the CDMA2000. Although ACPR is not officially required by the IS-95 or the IS-98 air interface standards as it is in the CDMA2000, it is still suggested that the handset RF designer verifies to see if the components meet the specifications of Table 1.

$$\text{EQ\_3: } V_{OUT} = 3 \cdot V_{CON}$$

National Semiconductor has switchers for RF Power Amplifiers that are perfect for this application. One of National's recent products is the LM3200. The LM3200 is capable of generating a dynamically variable output voltage between 0.8V and 3.6V with load currents up to 300 mA in PWM mode and 500 mA in Bypass Mode.

## Design Considerations

After a brief discussion of each building block in this application, we are ready to move to an explanation of the design procedure.

Assume that we are requested to design simple efficiency enhancement circuitry for an IS-95 RF power amplifier. The maximum output RF power level is +28 dBm and the LMV225 is used as an RF power detector. The switcher's Programmable Output Voltage equation would be EQ\_3.

Figure 3 is the handset PA's probability graph and will be used as the efficiency optimization guideline. This probability graph reveals that the CDMA RF power amplifier operates at +15 dBm output power and below most of the time. If we can reduce the DC power consumption of the CDMA RF power amplifier in this operating range, the handset will save significant battery energy and then talk time will be longer.

The simplest solution is to set the supply voltage,  $V_{CC}$ , of the CDMA RF power amplifier to be the lowest level possible when the output RF power is +15 dBm and below.

Figure 2 shows the CDMA RF power amplifier performance at two different supply voltages,  $V_{CC} = 3.4V$  and  $V_{CC} = 1.4V$ . The 1 dB compression point at  $V_{CC} = 3.4V$  is about +28 dBm

## Design Considerations (Continued)


and at  $V_{CC} = 1.4V$  it is about +20 dBm. The graph includes plots of the 3rd order intermodulation distortions for both cases.

A typical CDMA RF power amplifier can pass the ACPR requirements for a small output power level all the way to a +28 dBm power level with  $V_{CC} = 3.4V$  as specified in its datasheet. In the case of  $V_{CC} = 3.4V$ , the 3rd order intermodulation distortion level is 28 dBc below the fundamental,  $C/3IM = -28$  dBc, at  $P_{OUT} = +28$  dBm. In the case of  $V_{CC} = 1.4V$ , the 3rd order intermodulation distortion is 30 dBc below the fundamental,  $C/3IM = -30$  dBc, at  $P_{OUT} = +15$  dBm.

Since ACPR is a function of intermodulation distortion, we can predict that the ACPR at  $P_{OUT} = +15$  dBm with  $V_{CC} = 1.4V$  should be as good as that at  $P_{OUT} = +28$  dBm with  $V_{CC} = 3.4V$ . Based on this information and the statistics in Figure 3, we can reduce the use of the battery of the CDMA RF power amplifier by setting its  $V_{CC} = 1.4$  for power levels from +15 dBm and below.

Figure 5 shows the DC power consumption of the supply voltage at  $V_{CC} = 3.4V$  and  $V_{CC} = 1.4V$  and it demonstrates the saving of battery energy. The operating point 'A' is  $P_{OUT} = +15$  dBm when  $V_{CC} = 3.4V$ ; its  $P_{DC}$  can be found to be +27 dBm from the secondary Y-axis. When the supply voltage is changed to  $V_{CC} = 1.4V$ , the operating point for  $P_{OUT} = +15$  dBm is 'AA.' Its  $P_{DC}$  is +22.5 dBm.

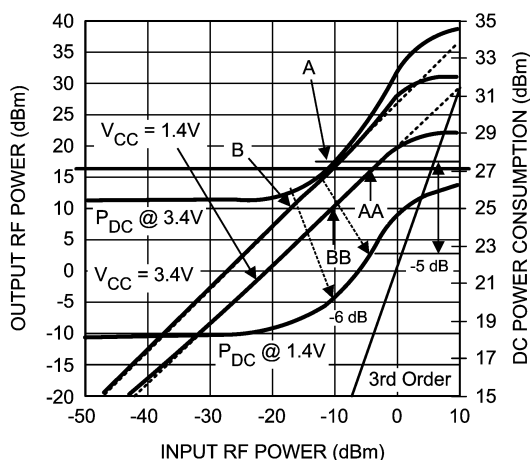Therefore, the power saving from  $V_{CC} = 3.4$  to  $V_{CC} = 1.4V$  is  $27 - 22.5 = 4.5$  dB. This 4.5 dB power saving corresponds to more than 50% saving in power.



20178406

FIGURE 5.  $P_{OUT}$  and  $P_{DC}$  vs.  $P_{IN}$


## Application Circuit

Figure 6 is the proposed application circuit for reducing the use of battery energy in a CDMA RF power amplifier. We set the control voltage of the switcher to be  $V_{CON} = 0.467V$ . This 0.467V can be obtained from a voltage divider in the supply voltage of  $V_{DD} = 2.8V$ . This 0.467V will generate a  $V_{OUT} = 3 * 0.467 = 1.4V$  according to EQ\_3. This  $V_{OUT} = 1.4V$  is then supplied to the  $V_{CC}$  of the RF power amplifier. When  $P_{OUT} = +15$  dBm and below, we need to set the switcher in PWM mode by setting  $BYPASS = Low$ .

The LMV225 is used to determine if the switcher needs to be in Bypass mode. We use  $R1 = 1.8k\Omega$  as a tapping resistor to achieve 31 dB coupling between the output of the RF power amplifier and the input of the LMV225. Figure 4 is the LMV225 response vs.  $P_{OUT}$  of an RF power amplifier. At  $P_{OUT} = +15$  dBm, the detected voltage  $V_{DET} = 1.45V$ .

In this application circuit, the base-band chip needs to check the value of  $V_{DET}$ . When  $V_{DET}$  is above 1.45V, the base-band chip will set the switcher in Bypass mode by sending a logic high signal to  $BYPASS$ .

## Application Circuit (Continued)

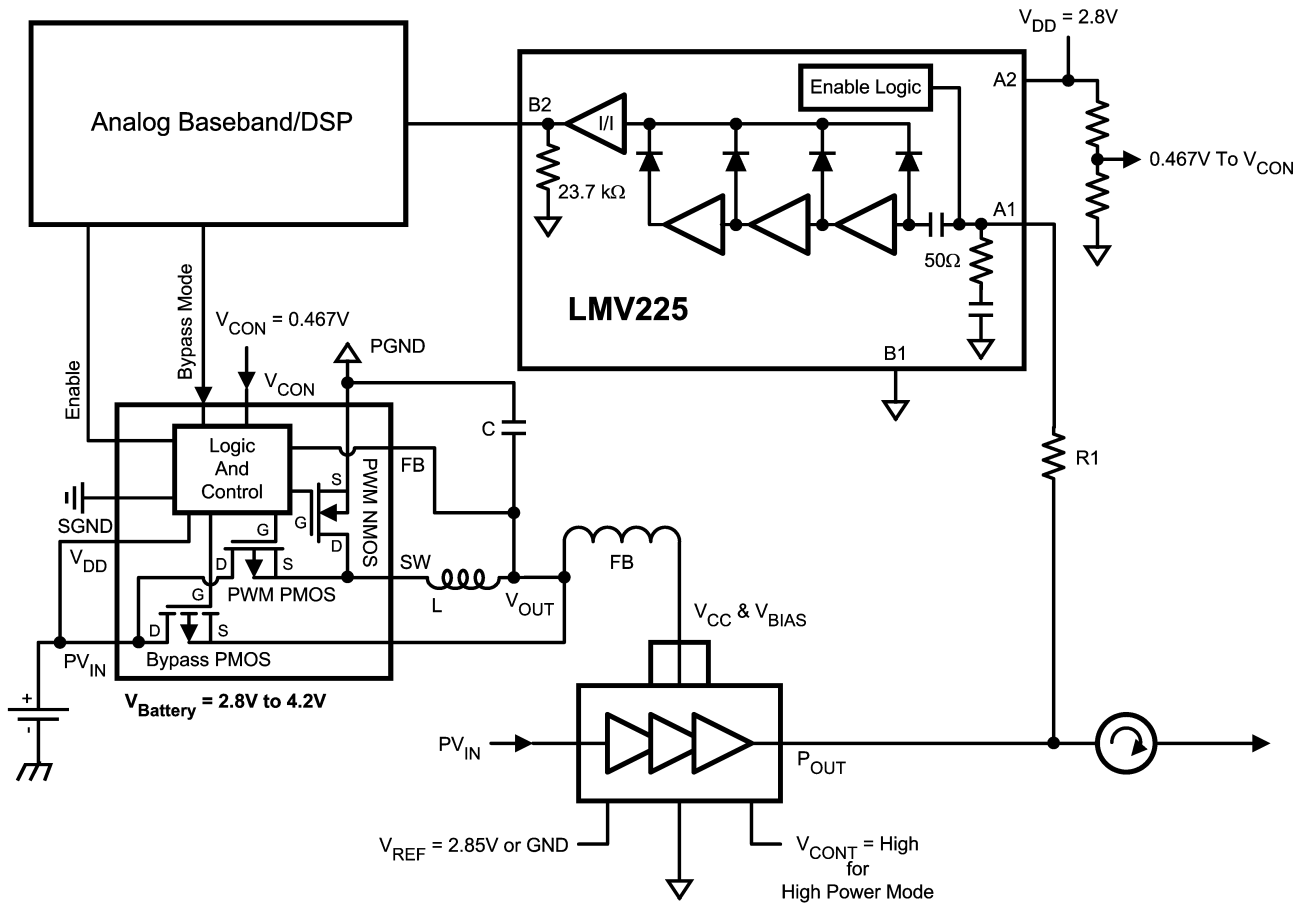

20178407

FIGURE 6. Efficiency Enhancement Circuit Diagram

### Power Saving at 10 dBm

Here is another illustration of battery saving. The operating point at 'B' is  $P_{\text{OUT}} = +10\text{ dBm}$  with  $V_{\text{CC}} = 3.4\text{V}$ . At this supply voltage level, the  $P_{\text{DC}}$  for  $P_{\text{OUT}} = +15\text{ dBm}$  is about 26 dBm. If we lower the supply voltage to  $V_{\text{CC}} = 1.4\text{V}$ , the operating point becomes 'B' and the  $P_{\text{DC}}$  for  $P_{\text{OUT}} = +15\text{ dBm}$  is about 20 dBm. This shows a 6 dB saving in power or 75% less power in watts.

### Conclusion

We have demonstrated the flexibility and benefits of using National Semiconductor's LMV225 together with a switcher in reducing battery energy consumption in a CDMA RF power amplifier. By adding this simple circuitry, we can save 50% of DC power consumption of the CDMA RF power amplifier at the most common operating points of IS-95 and CDMA2000 handsets.

## Notes

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.

For the most current product information visit us at [www.national.com](http://www.national.com).

### LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

### BANNED SUBSTANCE COMPLIANCE

National Semiconductor manufactures products and uses packing materials that meet the provisions of the Customer Products Stewardship Specification (CSP-9-111C2) and the Banned Substances and Materials of Interest Specification (CSP-9-111S2) and contain no "Banned Substances" as defined in CSP-9-111S2.

Leadfree products are RoHS compliant.



**National Semiconductor**  
Americas Customer  
Support Center  
Email: [new.feedback@nsc.com](mailto:new.feedback@nsc.com)  
Tel: 1-800-272-9959

[www.national.com](http://www.national.com)

**National Semiconductor**  
Europe Customer Support Center  
Fax: +49 (0) 180-530 85 86  
Email: [europa.support@nsc.com](mailto:europa.support@nsc.com)  
Deutsch Tel: +49 (0) 69 9508 6208  
English Tel: +44 (0) 870 24 0 2171  
Français Tel: +33 (0) 1 41 91 8790

**National Semiconductor**  
Asia Pacific Customer  
Support Center  
Email: [ap.support@nsc.com](mailto:ap.support@nsc.com)

**National Semiconductor**  
Japan Customer Support Center  
Fax: 81-3-5639-7507  
Email: [jpn.feedback@nsc.com](mailto:jpn.feedback@nsc.com)  
Tel: 81-3-5639-7560