LM3743 High Performance Controller with Comprehensive Fault Protection Features Designed for High Reliability Systems Introduction

The LM3743 is a DC-DC voltage mode PWM buck controller featuring synchronous rectification at 300 kHz or 1 MHz. It can deliver current as high as 20A and step down from an input voltage between 3V and 5.5V down to a minimum output voltage of 0.8V. It is a highly integrated device in a small MSOP-10 package. Features include; pre-biased soft-start, tracking capability, and comprehensive fault protection features suitable for high reliability systems such as rack mounted servers and telecom base station subsystems.



FIGURE 1. Typical Application Circuit

Data center facilities and telecom base station subsystems must manage the balance of two essential commodities power and cooling capacity. For example, processors in rack mounted servers demand large amounts of power and are one of the greatest sources of heat during normal operation. Substantial increases in heat during normal operation and fault conditions will reduce the reliability of many components in the server racks including semiconductor components, hard drives, and fans. The LM3743 will minimize power consumption during fault conditions thereby reducing thermal loads and increasing reliability.

LM3743 Comprehensive Fault Protection Features

The LM3743 provides the following comprehensive fault protection features: high side current limit (HSCL), output undervoltage protection (UVP), and low side current limit (LSCL). When engaged, these three features can each independently initiate a hiccup protection mode which disables both the highside and low-side FETs and begin a cool down period of 5.5 ms, see Figure 2. At the conclusion of this cool down period, the LM3743 performs an internal 3.6 ms soft-start to check for the removal of the fault condition and to continue normal operation. Hiccup protection mode enables the system designer to avoid the need to over design components due to thermal runaway during fault conditions resulting in a lower bill of material cost. National Semiconductor Application Note 1669 Ricardo Capetillo June 2007





30027002

FIGURE 2. Hiccup Time Out and Internal Soft-Start

To help quantify the power consumption during a persistent fault condition, let us examine an application with a 10A lowside current limit. Once in overload, the low-side current limit controls the valley current and only allows an average of 10A plus the ripple current to pass through the inductor and MOS-FETs. Hiccup mode initializes after 15 switching cycles allowing only a very small temperature rise. Once in hiccup mode, the average current through the high-side FET is:

 $I_{HSF-AVE} = (I_{CLIM} + \Delta I) \times [D(15 \text{ cycles } x \text{ T}_{SW})] / 5.5 \text{ ms} = 71 \text{ mA}$ With an arbitrary D = 60%, ripple current of 3A, and a 300 kHz switching frequency.

The average current through the low-side FET is:

$$I_{LSF-AVE} = (I_{CLIM} + \Delta I) \times [(1-D) \times (15 \text{ cycles } \times T_{SW})] / 5.5 \text{ ms} = 47 \text{ mA}$$

And the average current through the inductor is:

 $I_{L-AVE} = (I_{CLIM} + \Delta I) x [(15 \text{ cycles x } T_{SW})] / 5.5 \text{ ms} = 118 \text{ mA}$

Protecting Typical Fault Conditions in High-Reliability Systems

Server racks and telecom base station subsystems require high reliability to enable uninterrupted flow of data and communication. When unexpected failures occur, the LM3743 fault protection features can help to prevent further electrical and thermal stress. Examining some typical system fault conditions, we can elaborate on the protection modes of the LM3743 device and the operational benefit:

- 1. A capacitor such as a POS-cap located at the output of the LM3743 fails as a short circuit after an over-voltage surge exceeds the maximum capacitor voltage rating, refer to Figure 3. In such a situation duty cycle and the inductor current increase cycle by cycle, but fortunately input current is decreased because the LM3743s' UVP initializes Hiccup-Mode.
- 2. A small piece of metal falling into the product from the outside or a piece of metal that was loose in the product changes positions during shipment and lands across the

switch node (V_{SW}) and ground, see Figure 4. High side current limit immediately senses the short circuit fault condition.

 Excessive load and/or incorrect selection of the MOSFET results in an open circuit failure. For example; if the low side MOSFET (Q2) fails, depicted in Figure 5, the inductor current will not flow during the time Q2 should be on, thus the inductor current will increase cycle by cycle. The high side current limit will capture the over current event, thereby protecting the high side MOSFET (Q1) from over heating and failure.



FIGURE 3. Output Short-Circuit to Ground



FIGURE 4. Switch Node Short-Circuit to Ground



FIGURE 5. Low Side MOSFET Open-Circuit Failure

In all these situations the LM3743 provides fault protection, reduces the average input current and relieves the power components from thermal stress during persistent fault conditions. After the removal of the fault condition, the LM3743 performs an automatic self test and recovery sequence. User intervention is not required, in so reduces maintenance cost and designed in circuit complexity.

The LM3743 provides comprehensive fault protection and a reduction in server power consumption during fault conditions. It also combines high efficiency with high drive capabilities for loads up to 20A. With the LM3743, the balance between power and cooling capacity are much more manageable during device failure and short circuit conditions.

For datasheet, evaluation board, application note, and reference design information go to: www.national.com/pf/LM/LM3743.html.

Notes

AN-1669

Notes

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

Copyright© 2007 National Semiconductor Corporation

For the most current product information visit us at www.national.com



AN-1669

National Semiconductor Americas Customer Support Center Email: new.feedback@nsc.com Tel: 1-800-272-9959 National Semiconductor Europe Customer Support Center Fax: +49 (0) 180-530-85-86 Email: europe.support@nsc.com Deutsch Tei: +49 (0) 69 9508 6208 English Tel: +49 (0) 870 24 0 2171 Français Tei: +33 (0) 1 41 91 8790 National Semiconductor Asia Pacific Customer Support Center Email: ap.support@nsc.com National Semiconductor Japan Customer Support Center Fax: 81-3-5639-7507 Email: jpn.feedback@nsc.com Tel: 81-3-5639-7560