

Minimizing FET Losses For a High Input Rail Buck Converter

National Semiconductor
Application Note 1628
William Stokes
September 2007



Engineers often face the challenge of choosing the input voltage rail that works best for the DC-DC converter at the Point-of-Load (POL). High voltage rails, above 12V, usually demand intermediate regulation stages that reduce overall efficiency and add to cost. However, the new generation of regulator and controller ICs afford POL regulation from these high input rails directly. Typically the buck regulator is employed as the POL workhorse but its efficiency is highly dependent on the optimization of the High-Side (HS) and Low-Side (LS) MOSFET (FET) combinations. At lower input voltages it is often possible to use the same HS and LS FETs, yet for higher input voltages the selection criteria for these FETs are different, and will be the subject of this application note.

Buck Converter Loss Mechanisms

The schematic in *Figure 1* shows the basic architecture for a DC-DC buck (or step-down) voltage regulator circuit that employs the LM5116 as the Pulse Width Modulator (PWM) switch controller. The critical current path is from V_{IN} through the HS FET to the output via the inductor; and alternately, from ground through R_s and the LS FET to the output. Power losses due to the FETs along this path tend to dominate all other losses.

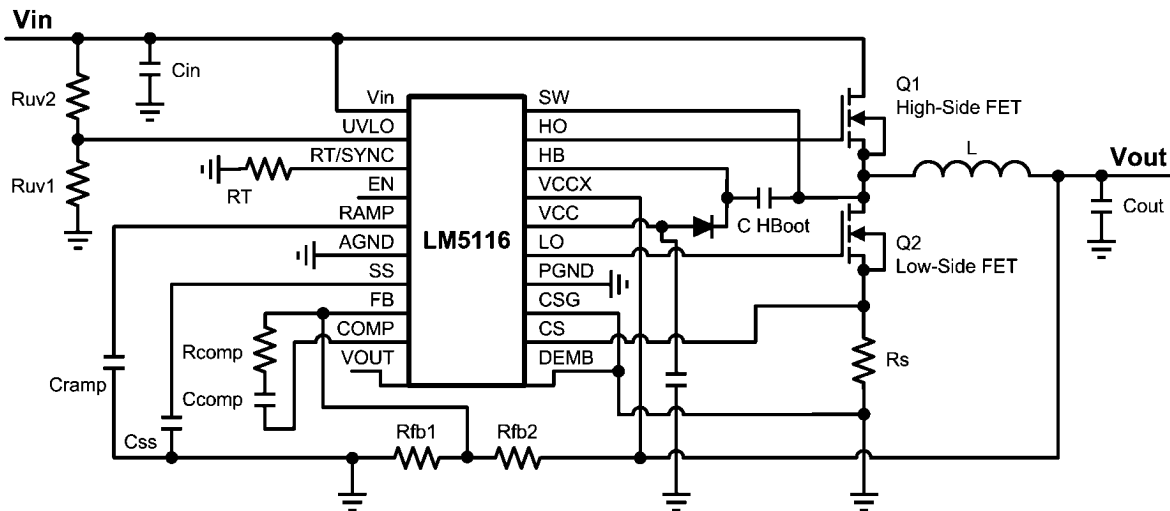


FIGURE 1. Synchronous Buck Regulator Schematic

Losses occurring in the FETs are a combination of conduction losses in the channel of the FET and switching losses during the turn-on and turn-off transitions. Conductive losses are proportional to the RMS current through each FET, and ignoring the ripple current in the output inductor, are often approximated (for the HS and LS respectively) by the following:

$$P_{QHS} = I_{OUT}^2 \cdot R_{DHS} \cdot D$$

$$P_{QLS} = I_{OUT}^2 \cdot R_{DLS} \cdot (1 - D)$$


In these equations I_{OUT} is the output current, R_{DHS} and R_{DLS} are respectively the on-resistances of the HS and LS FETs,

D is the duty cycle of the HS FET and $(1-D)$ is the duty cycle of the LS FET.

The duty cycle, D , is given by

$$D = \frac{V_{IN}}{V_{OUT}}$$

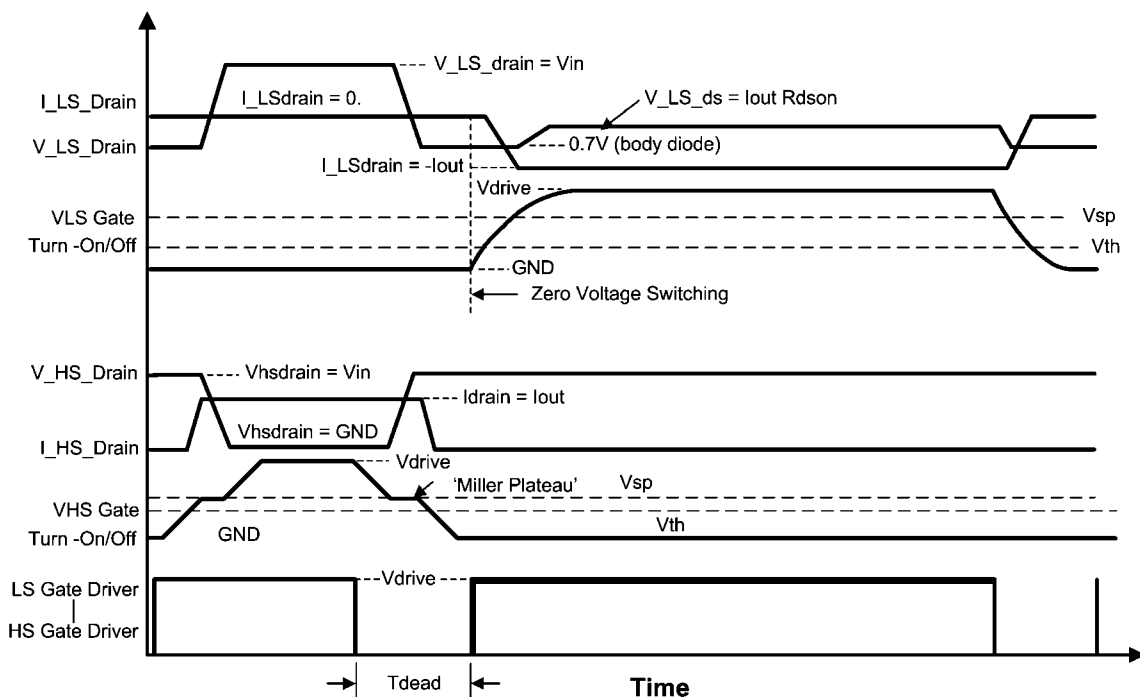The switching behaviors of the HS and LS FETs in the buck regulator differ from each other and this difference can be understood with the aid of *Figure 2*



30019105

FIGURE 2. Basic Switching Characteristics (not to scale) for HS and LS FET Operating in a DC-DC Converter Application

The LS FET exhibits zero-voltage switching. First of all, the gate voltage, V_{LSgate} , turns the FET on while the FET's body diode is conducting. Then, when the gate turns the FET off, the load current will continue to flow in the same direction but now through the body diodes, such that the drain voltage stays near zero. Thus the attendant switching losses are negligible in both cases.

The main switching loss caused by the LS FET occurs in the gate driver due to the charging and discharging of its gate capacitance. At higher frequencies in high power systems this

can impose an upper limit on the number of LS FETs that can be used in parallel to reduce the on-resistance. The increase in gate drive power required as more FETs are used in parallel can exceed the reduction in conduction losses.

Switching losses are significant in the HS FET because its drain-source voltage is equal to V_{IN} and its drain current is approximately equal to I_{OUT} at both turn on and turn off, leading to large overlap losses. The switching losses are approximated by

$$P_{sw_{Q1}} = \frac{1}{2} \cdot V_{IN} \cdot I_{OUT} \cdot f_{SW} \cdot (t_{sw_{HS_rise}} + t_{sw_{HS_fall}}) + Q_{gs} \cdot V_{GH} \cdot f_{SW} + \frac{1}{2} \cdot C_{OSS} \cdot V_{IN}^2 \cdot f_{SW}$$

where f_{SW} is the switching frequency; $t_{sw_{HS_rise}}$ is the time it takes the gate voltage to rise from its threshold value to the end of the plateau interval; $t_{sw_{HS_fall}}$ is the time it takes the gate voltage to fall from the beginning of the plateau interval to the threshold value; Q_{gs} is the total gate charge of the FET; C_{OSS} is the FET's drain-source capacitance; and V_{GH} is its gate drive voltage. The determination of the fall and rise times is beyond the scope of this article, but the relevant equations can be found in the web-published application notes of various MOSFET vendors.

The first term on the right hand side in Eq. 3 is the power lost in the FET due to the simultaneous high drain current and drain-source voltage at turn on and off already mentioned. The second term is the power required by the FET's gate, (which is dissipated in the gate driver). The third term is the power dissipated in charging the parallel combination of the LS and HS FETs' output capacitance.

Another switching loss that occurs in the HS FET is due to the reverse recovery of the LS FET's body diode. This loss can be virtually eliminated at low currents (<5A) by paralleling a schottky diode with the LS FET.


Design Lessons

The following generalizations are based on the above equations and should give further insight into FET selection:

 - 1) Switching losses increase for larger gate and drain capacitance and these capacitance are inversely proportional to the on-resistance. FETs with the lowest on-resistance inevitably have the higher capacitance hindering HS switching speed.
- 2) Reducing the switching clock frequency reduces switching losses; that is, at lower frequencies the losses during on/off transitions become a diminishing proportion of the total on-time of the FET causing conduction losses to increasingly dominate.
- 3) For higher input voltages relative to the output voltage the duty cycle of the HS FET decreases causing the switching losses to increasingly dominate.
- 4) In order to further reduce conduction losses, multiple, parallel, LS FETs are often employed. The number of parallel FETs is determined ultimately by cost, the gate driver's ability to drive them, and the point of diminishing returns.

The engineer should be aware that in most POL applications, especially for input voltages higher than 12V, the switching

losses will likely dominate all other losses. *Equation 3* shows that under these circumstances the lowest overall losses in the HS FET are not necessarily achieved by using a device with the lowest on-resistance. The FET must be selected to minimize the sum of all the losses. The FET's on-resistance must be optimized at a higher value to achieve reduced capacitance and so reduce the switching losses. The major MOSFET vendors now provide "reduced charge, fast switching" MOSFETs which are optimized in this way for high-side buck applications.



30019106

FIGURE 3. DC-DC Converter Measured Data Showing the Efficiency as a Function of the Switching Frequency

If optimizing the FETs does not enable high enough efficiency in a system, the switching frequency can be reduced to decrease the switching losses and improve the efficiency. This, however, can result in a physically larger system. *Figure 3* is an example of measured data from a generic evaluation board. The efficiency of this board was measured at various switching frequencies without changing any components on it except for the frequency-setting resistor. Though the conduction losses increased as the switching frequency was reduced (due to increased ripple currents), the overall efficiency went up because the switching losses in the HS FET decreased. The graph shows that changing the switching frequency has a dramatic effect on the switching losses.

The foregoing discussions have made clear that to achieve maximum efficiency in a high input voltage buck converter, the high side MOSFET must be carefully selected to minimize the sum of the switching and conduction losses.

Notes

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

Copyright© 2007 National Semiconductor Corporation

For the most current product information visit us at www.national.com



**National Semiconductor
Americas Customer
Support Center**
Email:
new.feedback@nsc.com
Tel: 1-800-272-9959

**National Semiconductor Europe
Customer Support Center**
Fax: +49 (0) 180-530-85-86
Email: europe.support@nsc.com
Deutsch Tel: +49 (0) 69 9508 6208
English Tel: +49 (0) 870 24 0 2171
Français Tel: +33 (0) 1 41 91 8790

**National Semiconductor Asia
Pacific Customer Support Center**
Email: ap.support@nsc.com

**National Semiconductor Japan
Customer Support Center**
Fax: 81-3-5639-7507
Email: jpn.feedback@nsc.com
Tel: 81-3-5639-7560