LM3464 and LM5021 DHC **25W Reference Designs**

National Semiconductor Application Note 2102 David Zhang March 31, 2011



Introduction

This evaluation board consists of a National Semiconductor LM5021 based 120Vac 24W AC/DC flvback converter and a LM3464 based dynamic head room control (DHC) four channel LED driver IC. This demonstration platform was developed so that the customers could evaluate the LM3464 with an AC/DC supply. Once familiar with the operation of the LM3464 and its control of the AC/DC converter's control loop, the type of AC/DC power supply and the converter's output power becomes less relevant. The evaluation board contains eight CREE XLamp MC-E LEDs. Each XLamp MC-E LED has four separate LEDs in each package for a total of 32 LEDs. The CREE MC-E LED allows for an easy demonstration of the LM3464 four channel operation with eight packaged LEDs. each LED string is regulated to 200mA. A heat sink is mounted on the back of the PCB to dissipate the heat generated by the LEDs. The LM3464 regulates each LED string current and adjust the secondary output voltage of the AC/DC power supply 0.9V above the LED string forawrd voltage. The LM3464 monitors the output voltage and adjusts the feedback voltage to the LM5021 primary control. This evaluation also demonstreates the LM3464 thermal fold-back feature which reduces the average LED current when the LED temperature is over 80°C. The AC/DC flyback power supply works in the discontinuous conduction mode and achieves power factor (PF) greater than 0.98.

The schematic, bill of materials, layout and measured performance characteristics are included.

Performance Specifications

Key Features

- Drive four strings of LEDs from 120Vac
- Overall Efficiency greater than 82%
- DC/LED Efficiency greater than 90%
- Power Factor greater than 0.98
- Dynamic Headroom Control (DHC) Thermal foldback control

Symbol	Parameter	Min	Тур	Мах
V _{IN}	Input voltage	90 V _{RMS}	120 V _{RMS}	132 V _{RMS}
V _{OUT}	LED string voltage	22 V	26 V	30 V
I _{LED}	LED string average current per string	-	200 mA	-
P _{OUT}	Output power	-	21 W	-
f _{sw}	Switching frequency	-	67 kHz	-

AN-2102

Demo Board



30143905



Warning: The LM3464 evaluation board has exposed high voltage components that present a shock hazard. Caution must be taken when handling the evaluation board. Avoid touching the evaluation board and removing any cables while the evaluation board is operating.

Warning: The ground connection on the evaluation board is NOT referenced to earth ground. If an oscilloscope ground lead is connected to the evaluation board ground test point for analysis and the mains AC power is applied (without any isolation), the fuse (F1) will fail open. For bench evaluation, either the input AC power source or the bench measurement equipment should be isolated from the earth ground connection. Isolating the evaluation board (using 1:1 isolation line isolation transformer) rather than the oscilloscope is highly recommended.

AN-2102

Bill of Materials

Designator	Description	Manufacturer	Part Number
C1	CAP .10UF 305VAC EMI SUPPRESSION	EPCOS	B32921C3104M
C2	CAP, CERM, 0.33uF, 50V, +/-10%, X7R, 0805	MuRata	GRM219R71H334KA88D
C3, C18	CAP, CERM, 0.22uF, 250V, +/-10%, X7R, 1210	MuRata	GRM32DR72E224KW01L
C4	CAP, 33UF, 35V, ELECT, 5mmx11mm	Panasonic	EEUFM1V330
C5, C14,C15	CAP, CERM, 0.22uF, 100V, +/-10%, X7R, 0805	MuRata	GRM21AR72A224KAC5L
C6, C13	CAP, CERM, 1uF, 25V, +/-10%, X5R, 0805	AVX	08053D105KAT2A
C7	CAP, CERM, 47pF, 50V, +/-5%, C0G/NP0, 0805	Yageo America	CC0805JRNP09BN470
C8, C16	CAP, CERM, 0.068uF, 50V, +/-10%, X7R, 0805	AVX	08055C683KAT2A
C9, C10	CAP, 1000UF, 35V, ELECT, 12.5mmx25mm	Panasonic	EEU-FC1V102
C11	CAP, CERM, 1000pF, 250VAC, +/-10%, X7R, 1808	Syfer Technology	1808JA250102KXBSY2
C12	CAP, CERM, 0.15uF, 50V, +/-10%, X7R, 0805	Murata	GRM21BR71H154KA01L
C17	CAP, CERM, 1uF, 50V, +/-10%, X7R, 1206	TDK	C3216X7R1H105K
C19	CAP, CERM, 220pF, 500V, +/-10%, X7R, 1206	Vishay	VJ1206Y221KXEAT5Z
D1	Diode, Switching-Bridge, 400V, 0.8A, MiniDIP	Diodes Inc.	HD04-T
D2, D7	Diode, Schottky, 100V, 0.2A, SOD-123	ST Microelectronics	BAT41ZFILM
D3	DIODE TVS 150V 600W UNI 5% SMA	Littlefuse	SMAJ150A
D4	DIODE, 1000V, 1A, Mini SMA	Comchip Technology	CGRM4007-G
D5	Diode, Schottky, 100V, 2A, SMB	Diodes Inc.	B2100-13-F
D6	Diode, Zener, 10V, 500mW, SOD-123	ON Semiconductor	MMSZ4697T1G
D8	Diode, Zener, 8.2V, 500mW, SOD-123	Central Semiconductor	CMHZ4694
F1	CMHZ4694	Cooper/ Bussman	6125FA1A
H1	Heat Sink	CUI Inc.	VHS-45
J1, J2, J3, J4, J5, J6, J12	Terminal, Turret, TH, Double	Keystone Electronics	1502-2
J7, J8, J9, J10, J11	Test Point, SMT	Keystone Electronics	5016
JP1, JP2, JP3	Jumper	Samtec	TSW-102-07-G-S
L1	Common Mode Choke, 10mH, 0.3A	Coilcraft	BU09-103B25BL
L2	Inductor, Shielded Drum Core, 1mH, 0.45A,SMD	Coilcraft	MSS1038-105KLB
LED1 - LED8	LED	Cree	MCE4WT-A2-0000-000M02
Q1	MOSFET, N-CH, 500V, 6A, DPAK	Fairchild Semiconductor	FDD6N50TM
Q2	Transistor, NPN, 40V, 0.2A, SOT-23	Fairchild Semiconductor	MMBT3904
Q3, Q4, Q5, Q6	MOSFET, N-CH, 100V, 32A, DPAK	Fairchild Semiconducto	FDD3682
R1	RES, 150k ohm, 1%, 0.25W, 1206	Vishay-Dale	CRCW1206150KFKEA
R2	RES, 100k ohm, 1%, 0.125W, 0805	Vishay-Dale	CRCW0805100KFKEA
R3, R4	RES, 10.0 ohm, 1%, 0.125W, 0805	Vishay-Dale	CRCW080510R0FKEA
R5	RES, 0.1 ohm, 5%, 0.25W, 1206	Panasonic	ERJ-8RSJR10V
R7	RES, 10.5k ohm, 1%, 0.1W, 0603	Vishay/Dale	CRCW060310K5FKEA
R8, R12	RES, 1.00k ohm, 1%, 0.125W, 0805	Vishay/Dale	CRCW08051K00FKEA
R9	RES, 5.11k ohm, 1%, 0.125W, 0805	Vishay/Dale	CRCW08055K11FKEA
R10, R11	RES, 10.0k ohm, 1%, 0.125W, 0805	Vishay-Dale	CRCW080510K0FKEA

Designator	Description	Manufacturer	Part Number
R13	RES, 105k ohm, 1%, 0.1W, 0603	Vishay-Dale	CRCW0603105KFKEA
R14, R15	RES, 25.5k ohm, 1%, 0.125W, 0805	Vishay-Dale	CRCW080525K5FKEA
R16	RES, 2.67k ohm, 1%, 0.125W, 0805	Vishay-Dale	CRCW08052K67FKEA
R18	RES, 3.01k ohm, 1%, 0.125W, 0805	Vishay-Dale	CRCW08053K01FKEA
R19	RES, 8.06k ohm, 1%, 0.125W, 0805	Vishay-Dale	CRCW08058K06FKEA
R20	RES, 0 ohm, 5%, 0.125W, 0805	Vishay-Dale	CRCW08050000Z0EA
R21, R22, R23,	RES, 1.0 ohm, 1%, 0.125W, 0805	Vishay-Dale	CRCW08051R00FKEA
R24			
R25	RES, 0 ohm, 5%, 0.25W, 1206	Vishay-Dale	CRCW12060000Z0EA
R26	RES, 22.1k ohm, 1%, 0.125W, 0805	Vishay-Dale	CRCW080522K1FKEA
RT1	Thermistor NTC, 10k ohm, 2%, 0603	Panasonic	ERT-J1VG103GA
T1	Transformer, Flyback, 540UH	Wurth Elektornik	750311959
U1	AC-DC Current Mode PWM Controller	National	LM5021MM-1
		Semiconductor	
U2	Dynamic Headroom Controller w/Therm Control	National	LM3464MH
		Semiconductor	
U3	Opto Coupler	NEC	PS2501L-1-Q-A
U4	Low-Voltage Adjustable Precision Shunt Regulator	National	LMV431AIMF
		Semiconductor	
VR1	Varistor, 150V, 25J, 10mm	Littlefuse	V150LA5P

AN-2102

Typical Performance Characteristics



Total LED Current vs. LED Temperature

1.000

Power Factor vs. Line Voltage



30143939

Output Voltage & LED Forward Voltage vs. LED Temperature

26.5

26.0







Ch1: Output Voltage (10 V/div); Ch3: Total LED Current (500 mA/div); Time (10 ms/div)

Chi

Ch1: Line Voltage (100 V/div); Ch3: Line Current

(200 mĂ/div); Time (10 ms/div)





Ch1: Output Voltage (10 V/div); Ch3: Total LED Current (500 mV/div); Time (100 ms/div)

PCB Layout

AN-2102



Top Layer



Bottom Layer

30143908

Design Information

1ST STAGE - DCM FLYBACK

The evaluation board is considered a two stage LED driver system. The first stage is the AC/DC flyback converter and the second stage is the LM3464 LED currenr regulator. The first stage employs a NSC LM5021-1 in a discontinuous mode flyback and operates at fixed switching frequency and constant duty cycle. The input current follows the rectified AC input voltage and achieves power factor of 0.98 and higher. To ensure LM5021-1 operates at constant duty cycle, R7 and R1 need to be properly sized so that the slope compensation ramp is bigger than the current sense voltage. In this design, R7 is chosend to be 10.5Kohm and R1 is chosen to be 0.1 ohm. At 40% duty cycle, the peak ramp voltage is 246mV and the peak current sense voltage is around 150mV.

The transformer is designed to keep the flyback converter operating in discontinuous mode at peak output power. For a single stage PFC flyback converter, the peak output power occurs at peak input voltage and is twice the average output power. The transformer used in the evaluation board can handle up to 48W peak output power without saturation.

The feedback loop of the flyback converter includes U4 the LMV431 shunt regulator and U3 the opto coupler. When LM3464 is not controlling the output voltage (during initial power up), the flyback converter output voltage is set by resistor divider R13, R26 and R11 (approximately 17V). Once the LM3464 begins to control the LM5021 and therefore the output voltage by sink/source current through OutP pin and pushes the output voltage up to as high as 33V. In order to have good power factor, the control loop bandwidth has to be lower than 120Hz. For further explanation of LM3464 operation, please refer to thr LM3464 datasheet.

2ND STAGE - DYNAMIC HEADROOM CONTROL

The second stage of the evaluation board features the LM3464 which is a linear LED driver controller. The LM3464 is a four string controller, and in this particular demonstration board the LM3464 controls four strings of eight LEDs at 200mA. The internal ampiliers of LM3464 compare the voltages of the current sense resistors to a 200mV reference voltage and control the gate voltages of four external MOSFETs (Q3 - Q6) to achieve linear current regulations.

The voltage headroom which the voltage difference between the seondary output voltage of the AC/DC power supply and the LED string forward voltage is minimized by the LM3464 controller.By minimizing this voltage, the efficiency of the system is maximized. The LM3464 regulates the drain voltage of the external MOSFET to the voltage of the VDHC pin which is equal to 0.9V, therefore the headroom is about 0.9V.

LM3464 has thermal fold-back function to prevent the LEDs from overheating. When the voltage at the thermal pin (pin #3) is less than 3.25V, the average LED current is reduced by PWM dimming. For this evaluation board, the thermal fold-back function starts to kick in when the resistance of the NTC thermistor RT1 reaches 3.2kohm.

JUMPER/FAULT INFORMATION

Jumpers JP1, JP2 and JP3 are provided for the customers to short or disconnect LED strings. One string of LED can be disconnected to the power supply by open connector JP1. One LED each on LED string number one can be shorted by short connctors JP2 or JP3.

LM3464 will continue to regulate the currents of the remaining strings of LEDs when one or more strings of LEDs are shorted or disconnected. It will also continue to regulate the LED current when one or more LEDs in that string are shorted.

Electromagnetic Interference (EMI)

In order to get a quick estimate of the EMI filter performance, only the PEAK conductive EMI scan was measured and the data was compared to the Class B conducted EMI limits published in FCC – 47, section 15.



30143932



Thermal Analysis

The board temperature was measured using an IR camera (HIS-3000, Wahl) while running under the following conditions:

 $V_{IN} = 120 V_{RMS}$

The results are shown in the following figure.



30143933

FIGURE 2. Top Side Thermal Scan

AN-2102

Notes

For more National Semiconductor product information and proven design tools, visit the following Web sites at: www.national.com

Products		Design Support		
Amplifiers	www.national.com/amplifiers	WEBENCH® Tools	www.national.com/webench	
Audio	www.national.com/audio	App Notes	www.national.com/appnotes	
Clock and Timing	www.national.com/timing	Reference Designs	www.national.com/refdesigns	
Data Converters	www.national.com/adc	Samples	www.national.com/samples	
Interface	www.national.com/interface	Eval Boards	www.national.com/evalboards	
LVDS	www.national.com/lvds	Packaging	www.national.com/packaging	
Power Management	www.national.com/power	Green Compliance	www.national.com/quality/green	
Switching Regulators	www.national.com/switchers	Distributors	www.national.com/contacts	
LDOs	www.national.com/ldo	Quality and Reliability	www.national.com/quality	
LED Lighting	www.national.com/led	Feedback/Support	www.national.com/feedback	
Voltage References	www.national.com/vref	Design Made Easy	www.national.com/easy	
PowerWise® Solutions	www.national.com/powerwise	Applications & Markets	www.national.com/solutions	
Serial Digital Interface (SDI)	www.national.com/sdi	Mil/Aero	www.national.com/milaero	
Temperature Sensors	www.national.com/tempsensors	SolarMagic™	www.national.com/solarmagic	
PLL/VCO	www.national.com/wireless	PowerWise® Design University	www.national.com/training	

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

Copyright© 2011 National Semiconductor Corporation

For the most current product information visit us at www.national.com



National Semiconductor Americas Technical Support Center Email: support@nsc.com Tel: 1-800-272-9959

National Semiconductor Europe Technical Support Center Email: europe.support@nsc.com National Semiconductor Asia Pacific Technical Support Center Email: ap.support@nsc.com National Semiconductor Japan Technical Support Center Email: jpn.feedback@nsc.com