Wide Adjustable Range PNP Voltage Regulator

What happens when the need arises for a regulator voltage that isn't matched by your stock of fixed voltage I/C regulators? For the standard NPN pass transistor regulators (LM340 for example) the answer may be as simple as adding a resistor (R1) in the ground pin *(Figure 1)*. The new output voltage (V_O) will then be:

$$= V_{REG} + I_{Q} \times R1$$

(1)

TL/H/5723-1

where: V_{REG} is the original regulator output voltage, I_Q is the regulator's quiescent current.

Vo

But if the need is also for a low drop across the regulator, then a PNP pass regulator is required. Simply adding a resistor in the ground pin doesn't work, since the regulator internal current varies too much because of increased base drive to compensate for lower PNP beta. However, if a zener is used instead of a resistor, the higher voltages can be accommodated *(Figure 2).* The new output voltage (V_O) is: $V_O = V_{BEG} + V_Z$ (2)

where V_Z is the zener voltage.

As V_{REG} is constant, the output voltage regulation will depend largely on the zener voltage (V_Z) and its dynamic impedance.

The zener voltage will vary slightly with the current flowing through. Let's take the popular LM2931Z PNP regulator from National Semiconductor as an example of variation of the quiescent current. When the regulator load changes from 50 mA to 150 mA, the zener current will increase by



FIGURE 1. NPN Regulator

National Semiconductor Application Brief 12 February 1984



12.5 mA. The zener voltage variation due to this current change will only be a few hundred mV. That is, the output voltage will vary slightly, but not as much (as high as a few volts) as with a resistor to ground. Thus, a much better regulated output voltage is maintained.

One advantage inherent to this circuit is the ability to achieve higher output voltages than the normal regulator rating. The maximum regulator output is limited by the breakdown of its internal circuitry. However, carefully selecting the zener to keep the input and ground pin differential voltage well below the breakdown, the input is allowed to exceed its maximum rating. For example, a 5V 3-terminal LM2931Z PNP regulator (maximum operating input voltage = 26V) can become a 56V regulator with a 51V zener. And the input voltage can be as low as 56.6V with a load current of 150 mA or less. Most of the PNP regulator's features are still maintained. The short circuit protection may or may not be there, depending on the output voltage and the safe operating area of the output pass PNP transistor.

Capacitors C1 and C2 should have the same values as those specified for normal operation. However, their maximum operating voltage ratings should exceed the input voltage. Capacitor C3 should be located as close as possible to the ground pin to get good decoupling and ensure stable operation. The value of C3 will depend on zener impedance and noise characteristics. The capacitor types must also be rated over the desired operating temperature range.



Wide Adjustable Range PNP Voltage Regulator



© 1995 National Semiconductor Corporation TL/H/5723

RRD-B30M115/Printed in U. S. A

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

- Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform, when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
- A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

	National Semiconductor	National Semiconductor	National Semiconductor	National Semiconductor
	1111 West Derdin Deed		10th Floor Straight Blook	
· ·	TITT West Baroin Hoad	Fax: (+49) 0-160-530 65 66	Toth Floor, Straight Block,	161: 61-043-299-2309
	Arlington, TX 76017	Email: cnjwge@tevm2.nsc.com	Ocean Centre, 5 Canton Rd.	Fax: 81-043-299-2408
	Tel: 1(800) 272-9959	Deutsch Tel: (+49) 0-180-530 85 85	Tsimshatsui, Kowloon	
	Fax: 1(800) 737-7018	English Tel: (+49) 0-180-532 78 32	Hona Kona	
		Francais Tel: (+49) 0-180-532 93 58	Tel: (852) 2737-1600	
		Italiano Tel: (+49) 0-180-534 16 80	Fax: (852) 2736-9960	

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.