LM3429 Boost Evaluation Board

National Semiconductor Application Note 1986 James Patterson August 3, 2009




Introduction


This evaluation board showcases the LM3429 NFET controller used with a boost current regulator. It is designed to drive 9 to 12 LEDs at a maximum average LED current of 1A from a DC input voltage of 10 to 26V.

The evaluation board showcases most features of the LM3429 including PWM dimming, overvoltage protection and input under-voltage lockout. It also has a right angle connector (J7) which can mate with an external LED load board allowing for the LEDs to be mounted close to the driver. Alternatively, the LED+ and LED- banana jacks can be used to connect the LED load.

The boost circuit can be easily redesigned for different specifications by changing only a few components (see the Alternate Designs section found at the end of this application note). Note that design modifications can change the system efficiency for better or worse. See the LM3429 datasheet for a comprehensive explanation of the device and application information.

Schematic

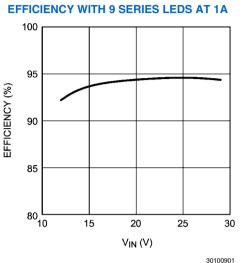

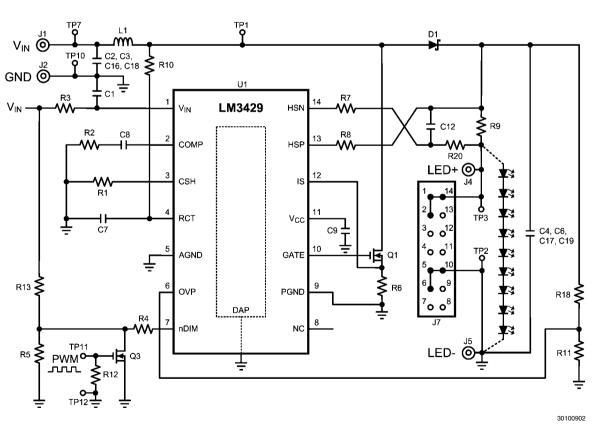

AN-1986


Pin Descriptions

Pin	Pin Name Description		Application Information		
1	V _{IN}	Input Voltage	Bypass with 100 nF capacitor to AGND as close to the device as possible in		
· · · · · · · · · · · · · · · · · · ·			the circuit board layout.		
2	COMP	Compensation	Connect a capacitor to AGND.		
3	CSH	Current Sense High	Connect a resistor to AGND to set the signal current. For analog dimming connect a controlled current source or a potentiometer to AGND as detailed the <i>Analog Dimming</i> section.		
4	RCT	Resistor Capacitor Timing	Connect a resistor from the switch node and a capacitor to AGND to set the switching frequency.		
5	AGND	Analog Ground	Connect to PGND through the DAP copper circuit board pad to provide prop ground return for CSH, COMP, and RCT.		
6	OVP	Over-Voltage Protection	Connect to a resistor divider from V_0 to program output over-voltage lock (OVLO). Turn-off threshold is 1.24V and hysteresis for turn-on is provided 20 μ A current source.		
7	nDIM	Not DIM input	Connect a PWM signal for dimming as detailed in the <i>PWM Dimming</i> section and/or a resistor divider from V_{IN} to program input under-voltage lockout (UVLO). Turn-on threshold is 1.24V and hysteresis for turn-off is provided by 20 μ A current source.		
8	NC	No Connection	Leave open.		
9	PGND	Power Ground	Connect to AGND through the DAP copper circuit board pad to provide proper ground return for GATE.		
10	GATE	Gate Drive Output	Connect to the gate of the external NFET.		
11	V _{CC}	Internal Regulator Output	Bypass with a 2.2 μ F–3.3 μ F, ceramic capacitor to PGND.		
12	IS	Main Switch Current Sense	Connect to the drain of the main N-channel MosFET switch for R _{DS-ON} sensing or to a sense resistor installed in the source of the same device.		
13	HSP	High-Side LED Current Sense Positive	Connect through a series resistor to the positive side of the LED current sense resistor.		
14	HSN	High-Side LED Current Sense Negative	Connect through a series resistor to the negative side of the LED current sense resistor.		
DAP (15)	DAP	Thermal pad on bottom of IC	Star ground, connecting AGND and PGND.		

Bill of Materials


Qty	Part ID	Part Value	Manufacturer	Part Number
2	C1, C4	0.1 µF X7R 10% 100V	ток	C2012X7R2A104K
4	C2, C3, C16, C18	4.7 μF X7R 10% 100V	MURATA	GRM55ER72A475KA01L
3	C6, C17, C19	2.2 µF X7R 10% 100V	TDK	C4532X7R2A225K
1	C7	1000 pF COG/NPO 5% 50V	MURATA	GRM2165C1H102JA01D
1	C8	1 μF X7R 10% 16V	MURATA	GRM21BR71C105KA01L
1	C9	2.2 μF X7R 10% 16V	MURATA	GRM21BR71C225KA12L
1	C12	0.1 µF X7R 10% 25V	MURATA	GRM21BR71E104KA01L
1	D1	Schottky 100V 12A	VISHAY	12CWQ10FNPBF
4	J1, J2, J4, J5	banana jack	KEYSTONE	575-8
1	J7	2 x 7 shrouded header	SAMTEC	TSSH-107-01-SDRA
1	L1	33 µH 20% 6.3A	COILCRAFT	MSS1278-333MLB
1	Q1	NMOS 100V 40A	VISHAY	SUD40N10-25
1	Q3	NMOS 60V 260 mA	ON-SEMI	2N7002ET1G
1	R1	12.4 kΩ 1%	VISHAY	CRCW080512k4FKEA
1	R2	0Ω 1%	VISHAY	CRCW08050000Z0EA
2	R3, R20	10Ω 1%	VISHAY	CRCW080510R0FKEA
1	R4	16.9 kΩ 1%	VISHAY	CRCW080516k9FKEA
1	R5	1.43 kΩ 1%	VISHAY	CRCW08051k43FKEA
1	R6	0.04Ω 1% 1W	VISHAY	WSL2512R0400FEA
2	R7, R8	1.0 kΩ 1%	VISHAY	CRCW08051k00FKEA
1	R9	0.1Ω 1% 1W	VISHAY	WSL2512R1000FEA
1	R10	35.7 kΩ 1%	VISHAY	CRCW080535k7FKEA
1	R11	15.8 kΩ 1%	VISHAY	CRCW080515k8FKEA
2	R12, R13	10.0 kΩ 1%	VISHAY	CRCW080510k0FKEA
1	R18	750 kΩ 1%	VISHAY	CRCW0805750kFKEA
7	TP1, TP2, TP3, TP7, TP10, TP11, TP12	turret	KEYSTONE	1502-2
1	U1	Buck-boost controller	NSC	LM3429MH

PCB Layout

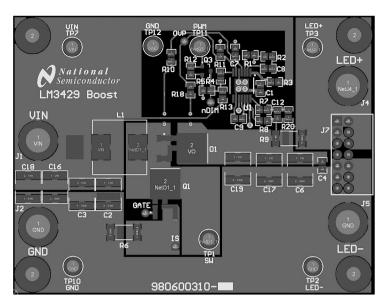

Top Layer

30100903

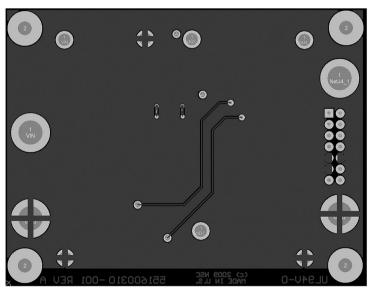

Bottom Layer

30100904

Design Procedure

Refer to LM3429 datasheet for design considerations.

SPECIFICATIONS

$$\begin{split} N &= 9 \\ V_{LED} &= 3.5V \\ r_{LED} &= 325 \ \text{m}\Omega \\ V_{IN} &= 24V \\ V_{IN-MIN} &= 10V; \ V_{IN-MAX} &= 27V \\ f_{SW} &= 700 \ \text{kHz} \\ V_{SNS} &= 100 \ \text{m}V \\ I_{LED} &= 1A \\ \Delta i_{L-PP} &= 250 \ \text{m}A \\ \Delta i_{LED-PP} &= 17 \ \text{m}A \\ \Delta v_{IN-PP} &= 100 \ \text{m}V \\ I_{LIM} &= 6A \\ V_{TURN-ON} &= 10V; \ V_{HYS} &= 3V \\ V_{TURN-OFF} &= 60V; \ V_{HYSO} &= 15V \end{split}$$

1. OPERATING POINT

Solve for V_O and r_D :

$$V_0 = N \times V_{LED} = 9 \times 3.5 V = 31.5 V$$

$$r_{\rm D} = N \times r_{\rm LED} = 9 \times 325 \, {\rm m}\Omega = 2.925 \Omega$$

Solve for D, D', D_{MAX} , and D_{MIN} :

$$D = \frac{V_0 - V_{|N|}}{V_0} = \frac{31.5V - 24V}{31.5V} = 0.238$$

$$D' = 1 - D = 1 - 0.238 = 0.762$$

$$D_{MIN} = \frac{V_{O} - V_{IN-MAX}}{V_{O}} = \frac{31.5V - 26V}{31.5V} = 0.175$$

$$D_{MAX} = \frac{V_{O} - V_{IN-MIN}}{V_{O}} = \frac{31.5V - 10V}{31.5V} = 0.683$$

2. SWITCHING FREQUENCY

Assume C7 = 1 nF and solve for R10:

$$R10 = \frac{25}{f_{SW} \times C7} = \frac{25}{700 \text{ kHz } \times 1 \text{ nF}} = 35.7 \text{ k}\Omega$$

The closest standard resistor is actually 35.7 k Ω therefore the f_{SW} is:

$$f_{SW} = \frac{25}{R10 \text{ x C7}} = \frac{25}{35.7 \text{ k}\Omega \text{ x 1 nF}} = 700 \text{ kHz}$$

The chosen components from step 2 are:

3. AVERAGE LED CURRENT

Solve for R9:

$$R9 = \frac{V_{SNS}}{I_{LED}} = \frac{100 \text{ mV}}{1\text{ A}} = 0.1\Omega$$

Assume R1 = 12.4 k Ω and solve for R8:

$$R8 = \frac{I_{LED} \times R1 \times R9}{1.24V} = \frac{1A \times 12.4 \text{ k}\Omega \times 0.1\Omega}{1.24V} = 1.0 \text{ k}\Omega$$

The closest standard resistor for R9 is 0.1 Ω and the closest for R8 (and R7) is actually 1 k Ω therefore I_{LED} is:

$$I_{LED} = \frac{1.24 \text{V} \text{x} \text{R8}}{\text{R9} \text{x} \text{R1}} = \frac{1.24 \text{V} \text{x} 1.0 \text{ k}\Omega}{0.1\Omega \text{ x} 12.4 \text{ k}\Omega} = 1.0\text{A}$$

The chosen components from step 3 are:

R9 = 0.1Ω		
R1 =12.4 kΩ		
$R8 = R7 = 1 k\Omega$		

4. INDUCTOR RIPPLE CURRENT

Solve for L1:

$$L1 = \frac{V_{\text{IN}} \times D}{\Delta i_{\text{L-PP}} \times f_{\text{SW}}} = \frac{24 \text{V} \times 0.238}{250 \text{ mA} \times 700 \text{ kHz}} = 32.6 \,\mu\text{H}$$

The closest standard inductor is 33 μH therefore the actual $\Delta i_{L\text{-PP}}$ is:

$$\Delta i_{L-PP} = \frac{V_{IN} \times D}{L1 \times f_{SW}} = \frac{24V \times 0.238}{33 \,\mu H \times 700 \,\text{kHz}} = 247 \,\text{mA}$$

Determine minimum allowable RMS current rating:

$$I_{L-RMS} = \frac{I_{LED}}{D'} \times \sqrt{1 + \frac{1}{12} \times \left(\frac{\Delta i_{L-PP} \times D'}{I_{LED}}\right)^2}$$
$$I_{L-RMS} = \frac{1A}{0.762} \times \sqrt{1 + \frac{1}{12} \times \left(\frac{247 \text{ mA} \times 0.762}{1A}\right)^2}$$
$$I_{L-RMS} = 1.31A$$

The chosen component from step 4 is:

L1 = 33 μH

5. OUTPUT CAPACITANCE Solve for C_0 :

$$C_{O} = \frac{I_{LED} \times D}{r_{D} \times \Delta i_{LED-PP} \times f_{SW}}$$

$$C_{\rm O} = \frac{1A \times 0.238}{2.925 \Omega \times 17 \text{ mA} \times 700 \text{ kHz}} = 6.84 \,\mu\text{F}$$

A total value of 6.6 μF (using 3 2.2 μF X7R ceramic capacitors) is chosen therefore the actual Δi_{LED-PP} is:

$$\Delta i_{\text{LED-PP}} = \frac{I_{\text{LED}} \times D}{r_{\text{D}} \times C_{\text{O}} \times f_{\text{SW}}}$$
$$\Delta i_{\text{LED-PP}} = \frac{1A \times 0.238}{2.925\Omega \times 6.6\mu\text{F} \times 700 \text{ kHz}} = 17.6 \text{ mA}$$

Determine minimum allowable RMS current rating:

$$I_{\text{CO-RMS}} = I_{\text{LED}} \times \sqrt{\frac{D_{\text{MAX}}}{1 - D_{\text{MAX}}}} = 1A \times \sqrt{\frac{0.683}{1 - 0.683}} = 1.47A$$

The chosen components from step 5 are:

$$C6 = C17 = C19 = 2.2 \ \mu F$$

6. PEAK CURRENT LIMIT

Solve for R6:

$$R6 = \frac{245 \text{ mV}}{\text{I}_{\text{LIM}}} = \frac{245 \text{ mV}}{6\text{A}} = 0.041 \,\Omega$$

The closest standard resistor is 0.04 Ω therefore I_IIM is:

$$I_{\text{LIM}} = \frac{245 \,\text{mV}}{\text{R6}} = \frac{245 \,\text{mV}}{0.04\Omega} = 6.1\text{A}$$

The chosen component from step 6 is:

7. LOOP COMPENSATION

 ω_{P1} is approximated:

$$ω_{P1} = \frac{2}{r_D \times C_O} = \frac{2}{2.925\Omega \times 6.6\mu F} = 104k \frac{rad}{sec}$$

 ω_{Z1} is approximated:

$$\omega_{z1} = \frac{r_D \times D'^2}{L1} = \frac{2.925\Omega \times 0.762^2}{33\mu H} = 52k \frac{rad}{sec}$$

T_{U0} is approximated:

$$T_{U0} = \frac{D' \times 310V}{I_{LED} \times R_{LIM}} = \frac{0.762 \times 310V}{1A \times 0.04\Omega} = 5900$$

To ensure stability, calculate ω_{P2} :

$$\omega_{P2} = \frac{\min(\omega_{P1}, \omega_{Z1})}{5 \times T_{U0}} = \frac{\omega_{Z1}}{5 \times 5900} = \frac{52k \frac{rao}{sec}}{5 \times 5900} = 1.76 \frac{rad}{sec}$$

Solve for C8:

$$C8 = \frac{1}{\omega_{P2} \times 5e^{6}\Omega} = \frac{1}{1.76 \frac{rad}{sec} \times 5e^{6}\Omega} = 0.11 \,\mu\text{F}$$

Since PWM dimming can be evaluated with this board, a much larger compensation capacitor C8 = 1.0 μ F is chosen. To attenuate switching noise, calculate ω_{P3} :

$$ω_{P3} = max(ω_{P1}, ω_{Z1}) \times 10 = ω_{P1} \times 10$$

$$\omega_{P3} = 104 \text{k} \frac{\text{rad}}{\text{sec}} \times 10 = 1.04 \text{ M} \frac{\text{rad}}{\text{sec}}$$

Assume R20 = 10Ω and solve for C12:

$$C12 = \frac{1}{10\Omega \times \omega_{P3}} = \frac{1}{10\Omega \times 1.04M \frac{rad}{sec}} = 0.097 \mu F$$

The chosen components from step 7 are:

8. INPUT CAPACITANCE

Solve for the minimum C_{IN}:

$$C_{IN} = \frac{\Delta i_{L-PP}}{8 \, x \, \Delta v_{IN-PP} \, x \, f_{SW}} = \frac{250 \text{ mA}}{8 \, x \, 100 \text{ mV} \, x \, 700 \text{ kHz}} = 0.45 \, \mu\text{F}$$

To minimize power supply interaction a much larger capacitance of approximately 20 μ F is used, therefore the actual $\Delta v_{\text{IN-PP}}$ is much lower. Since high voltage ceramic capacitor selection is limited, four 4.7 μ F X7R capacitors are chosen. Determine minimum allowable RMS current rating:

$$I_{\text{IN-RMS}} = \frac{\Delta i_{\text{L-PP}}}{\sqrt{12}} = \frac{250 \text{ mA}}{\sqrt{12}} = 72 \text{ mA}$$

The chosen components from step 8 are:

AN-1986

9. NFET

Determine minimum Q1 voltage rating and current rating:

$$V_{T-MAX} = V_0 = 31.5V$$

$$I_{\text{T-MAX}} = \frac{0.683}{1 - 0.683} \times 1A = 2.2A$$

A 100V NFET is chosen with a current rating of 40A due to the low R_{DS-ON} = 50 m $\Omega.$ Determine I_{T-RMS} and P_T :

$$I_{T-RMS} = \frac{I_{LED}}{D'} \times \sqrt{D} = \frac{1A}{0.762} \times \sqrt{0.238} = 640 \text{ mA}$$

$$P_{T} = I_{T-RMS}^{2} x R_{DSON} = 640 \text{ mA}^{2} x 50 \text{ m}\Omega = 20 \text{ mW}$$

The chosen component from step 9 is:

Q1
$$\rightarrow$$
 40A, 100V, DPAK

10. DIODE

Determine minimum D1 voltage rating and current rating:

$$V_{RD-MAX} = V_0 = 31.5V$$
$$I_{D-MAX} = I_{LED} = 1A$$

A 100V diode is chosen with a current rating of 12A and $V_D = 600 \text{ mV}$. Determine P_D :

$$P_{D} = I_{D} \times V_{FD} = 1A \times 600 \text{ mV} = 600 \text{ mW}$$

The chosen component from step 10 is:

$$D1 \rightarrow 12A$$
, 100V, DPAK

11. INPUT UVLO

Since PWM dimming will be evaluated a three resistor network will be used. Assume R13 = 10 k Ω and solve for R5:

$$R5 = \frac{1.24V \times R13}{V_{\text{TURN-ON}} - 1.24V} = \frac{1.24V \times 10 \text{ k}\Omega}{10V - 1.24V} = 1.43 \text{ k}\Omega$$

The closest standard resistor is 1.43 k Ω therefore $V_{\text{TURN-ON}}$ is:

$$V_{\text{TURN-ON}} = \frac{1.24 \text{Vx} (\text{R5} + \text{R13})}{\text{R5}}$$
$$V_{\text{TURN-ON}} = \frac{1.24 \text{Vx} (1.43 \text{k}\Omega + 10 \text{k}\Omega)}{1.43 \text{k}\Omega} = 9.91 \text{V}$$

Solve for R4:

$$R4 = \frac{R5 x (V_{HYS} - 20 \,\mu A x R13)}{20 \,\mu A x (R5 + R13)}$$
$$R4 = \frac{1.43 \,k\Omega x (2.9V - 20 \,\mu A x 10 \,k\Omega)}{20 \,\mu A x (1.43 \,k\Omega + 10 \,k\Omega)} = 16.9 \,k\Omega$$

The closest standard resistor is 16.9 k Ω making V_{HYS}:

$$V_{HYS} = \frac{20 \ \mu A \ x \ R4 \ x \ (R5 + R13)}{R5} + 20 \ \mu A \ x \ R_{UV2}$$
$$V_{HYS} = \frac{20 \ \mu A \ x \ 16.9 \ k\Omega \ x \ (1.43 \ k\Omega + 10 \ k\Omega)}{1.43 \ k\Omega} + 20 \ \mu A \ x \ 10 \ k\Omega = 2.9V$$

The chosen components from step 11 are:

$R5 = 1.43 k\Omega$	
R13 = $10 k\Omega$	
$R4 = 16.9 k\Omega$	

12. OUTPUT OVLO

Solve for R18:

$$R18 = \frac{V_{HYSO}}{20\,\mu A} = \frac{15V}{20\,\mu A} = 750\,k\Omega$$

The closest standard resistor is 750 k Ω therefore V_{HYSO} is:

$$V_{\rm HYSO} = R18\,x\,20\,\mu A = 750\,k\Omega\,x\,20\,\mu A = 15V$$

Solve for R11:

$$R11 = \frac{1.24V \text{ x } R18}{V_{\text{TURN-OFF}} - 1.24V} = \frac{1.24V \text{ x } 750 \text{ k}\Omega}{60V - 1.24V} = 15.8 \text{ k}\Omega$$

The closest standard resistor is 15.8 k Ω making V_{TURN-OFF}:

$$V_{\text{TURN-OFF}} = \frac{1.24 \text{Vx} (\text{R11} + \text{R18})}{\text{R11}}$$

$$V_{\text{TURN-OFF}} = \frac{1.24 \text{Vx} (15.8 \text{k}\Omega + 750 \text{k}\Omega)}{15.8 \text{k}\Omega} = 40 \text{V}$$


The chosen components from step 12 are:

R11 = 15.8 kΩ
R18 = 750 k Ω

Typical Waveforms

Alternate Designs

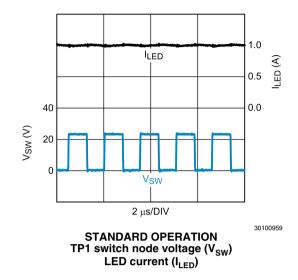 $T_A = +25^{\circ}C$, $V_{IN} = 24V$ and $V_O = 31.5V$.




Alternate designs with the LM3429 evaluation board are pos-

sible with very few changes to the existing hardware. The

evaluation board FETs and diodes are already rated higher

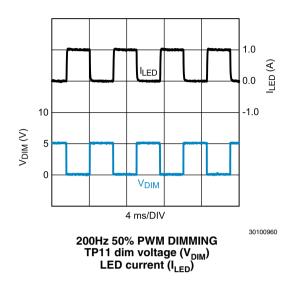than necessary for design flexibility. The input UVLO, output OVP, input and output capacitance can remain the same for



the designs shown below. These alternate designs can be evaluated by changing only R9, R10, and L1.

The table below gives the main specifications for four different designs and the corresponding values for R9, R10, and L1. PWM dimming can be evaluated with any of these designs.

Specification / Component	Design 1	Design 2	Design 3	Design 4
V _{IN}	10V	15V	20V	25V
Vo	14V	21V	28V	35V
f _{SW}	600kHz	700kHz	500kHz	700kHz
I _{LED}	2A	500mA	2.5A	1.25A
R9	0.05Ω	0.2Ω	0.04Ω	0.08Ω
R10	41.2 kΩ	35.7 kΩ	49.9 kΩ	35.7 kΩ
L1	22µH	68µH	15µH	33µH

AN-1986

Notes

Pr	oducts	Design Support	
Amplifiers	www.national.com/amplifiers	WEBENCH® Tools	www.national.com/webench
Audio	www.national.com/audio	App Notes	www.national.com/appnotes
Clock and Timing	www.national.com/timing	Reference Designs	www.national.com/refdesigns
Data Converters	www.national.com/adc	Samples	www.national.com/samples
Interface	www.national.com/interface	Eval Boards	www.national.com/evalboards
LVDS	www.national.com/lvds	Packaging	www.national.com/packaging
Power Management	www.national.com/power	Green Compliance	www.national.com/quality/green
Switching Regulators	www.national.com/switchers	Distributors	www.national.com/contacts
LDOs	www.national.com/ldo	Quality and Reliability	www.national.com/quality
LED Lighting	www.national.com/led	Feedback/Support	www.national.com/feedback
Voltage Reference	www.national.com/vref	Design Made Easy	www.national.com/easy
PowerWise® Solutions	www.national.com/powerwise	Solutions	www.national.com/solutions
Serial Digital Interface (SDI)	www.national.com/sdi	Mil/Aero	www.national.com/milaero
Temperature Sensors	www.national.com/tempsensors	SolarMagic™	www.national.com/solarmagic
Wireless (PLL/VCO)	www.national.com/wireless	PowerWise® Design University	www.national.com/training

For more National Semiconductor product information and proven design tools, visit the following Web sites at:

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

Copyright© 2009 National Semiconductor Corporation

For the most current product information visit us at www.national.com



National Semiconductor Americas Technical Support Center Email: support@nsc.com Tel: 1-800-272-9959

National Semiconductor Europe Technical Support Center Email: europe.support@nsc.com National Semiconductor Asia Pacific Technical Support Center Email: ap.support@nsc.com National Semiconductor Japan Technical Support Center Email: jpn.feedback@nsc.com