Designing Energy-Efficient Handheld Illumination Solutions

Abstract

Portable battery sources are constantly challenged by the handheld applications' increasing functionality and power demands. By better understanding the applications' energy consumption, designers can produce energy-efficient solutions that will conserve battery life and provide a better end-user experience.

Conserving Energy in Portable Displays

Display backlighting presents a significant energy challenge as handheld displays increase in size, resolution, and brightness. A typical small display module can require between three to ten LEDs for proper illumination.

To address the backlit display's energy consumption, one power-efficient method to drive LEDs is the switched capacitor. This technique connects the input voltage to a multiplegain switched capacitor that produces a regulated output. The output voltage equals the gain multiplied by the input voltage during open loop operation. Closed loop operation enables a fixed output that should be slightly higher than the LED forward voltage and any voltage drop. The difference between output voltage and forward voltage is the headroom that needs to be monitored to ensure current flow. The switched capacitor remains in the most efficient gain over the widest input voltage consuming the least amount of energy through gain transitions that maintain regulation based on LED forward voltage and load requirements. Dual gain boost modes (1x and 3/2x for the LM2755 and LM2756; 2x and 3/2x for the LM2757) allow for the highest possible efficiency over a wide input voltage range resulting in longer battery life.

Consumer trends continue to dictate smaller portable devices, making PCB area much more valuable. The switched capacitor topology offers an added benefit as an inductor-less solution that saves on solution size and bill of materials. The LM2755, LM2756, and LM2757 are examples of switched capacitor boost technology that drive up to 10 LEDs (each driving up to 30 mA of diode current). This smaller solution provides the ability to place the driver in a local area, versus a central area, which reduces EMI.

Programmability of white LEDs is important to control display illumination. For example, when an end-user is having a conversation on a mobile phone, they are no longer interacting with the display, and the display has the option to dim. Both the LM2755 and LM2756 include an I²C-compatible interface

National Semiconductor Application Note 1777 Humair Khan February 27, 2008



that controls the display illumination based on handset operation.

Figure 1 shows the 32 exponential dimming step settings with an 800:1 dimming ratio which enables true perceived linear brightness level control and a dimming profile that leads to a smooth on/off display transition. The human eye is a logarithmic detector as it responds to light in terms of equal ratios rather than equal increments. What is recognized to be the linear augmentation of brightness is in reality exponential. By allowing the backlight to be dimmed or turned off, the designer gains flexibility and the ability to save battery life.



FIGURE 1. 32 Exponential Brightness Levels

Figure 2 is a typical application circuit of the LM2756. The LM2756 drives 8 LEDs separated in three independently controlled groups for multiple display purposes. The following equation configures the LED current levels:

 $I_{DxA/B/C (A)} = 189 \text{ x} (V_{ISET} / R_{SET})$

With a properly selected resistor (R_{SET}) placed between I_{SET} and GND, the desired level of current can be passed through the LEDs connected to DxA and DxB, where x is a number referring to the particular LED current sink and A, B, and C refers to the particular group of LEDs.



FIGURE 2. LM2756 Typical Application Circuit

Once the current level is set, analog current scaling internally dims the LEDs using the I²C-compatible interface. The 32 exponential analog brightness levels shown in *Figure 1* can be configured for the LEDs in Group A, while LEDs in Group B and Group C can handle 8 linear analog brightness levels.

With the ability to separately control several groups of LEDs, a single LED driver can control a main display, a secondary subdisplay or keypad LEDs, and an indicator LED. The LM2756 integrates these features by incorporating eight current sinks and dividing them into three groups. Four current sinks are comprised in Group A, while Group B and Group C have one current sink each. By manipulating a register, two extra sinks (D53 and D62) are available for either Group A or Group B. This allows 4, 5, or 6 LEDs to be used for the main display, leaving extra LEDs for additional lighting features.

Peripheral Lighting

Personal mobile devices have greater illumination needs than just the main display. Supplemental LEDs are required for further lighting functions consuming more battery energy. Keypad lighting is an important characteristic of handheld applications that does not require as much LED current matching as current-sourced main display backlighting drivers. The LM2757 provides the smallest switched capacitor, voltage-sourced, boost solution to illuminate keypad LEDs with up to 90% efficiency. Indicator LEDs alert end-users of low battery, battery charging activity, and incoming messages. These LEDs can also be used in fun-lighting applications. With three independent RGB LED outputs, the LM2755 permits programmable blinking patterns, via I²C-compatible interface, for each output enabling multiple zone lighting.

For indicator and cosmetic lighting purposes, LEDs usually require a generated pattern. The LM2755, shown in *Figure 3*, allows the designer to program a trapezoidal dimming waveform to independently control each output. The following equations calculate the durations of the delay, rise, fall, high, and low times shown on the waveform in *Figure 4*:

AN-1777



FIGURE 3. LM2755 Typical Application Circuit

 T_{STEP} = 50µs x 2^(N+1) if using the internal clock or T_{STEP} = (1/f_{PWM}) x 2^(N+1) if using the external clock on the SYNC pin

$$\label{eq:trise/fall_total} \begin{split} t_{rise/fall} &= T_{STEP} \; x \; (n_{high} - n_{low}) \; x \; n_{Trise/fall}, \\ where \; 0 \leq n_{Trise/fall} \leq 255 \end{split}$$

 $t_{rise \text{ or fall Total}} = 50 \mu s \text{ x } (n_{high} - n_{low}),$ where $n_{Trise/fall} = 0$

$$\label{eq:thigh or low} \begin{split} t_{high \mbox{ or low}} &= T_{\mbox{STEP}} \ x \ (n_{high/low} + 1), \\ where \ 0 \leq n_{Thigh/low} \leq 255 \end{split}$$

 $t_{delay} = T_{STEP} \times n_{delay},$ where $0 \le n_{delay} \le 255$ The variables n_{Trise} , n_{Tfall} , n_{Thigh} , and n_{Tlow} are numbers between 0 and 255 while n_{high} and n_{low} are selected numbers between 0 and 31 that become the brightness level boundaries when the dimming waveform enable bits are set to '1'. N is a number from 0 to 7 that is stored in the Time Step register. The PWM modulating signal period, f_{PWM} , is set to a default value of 50 µs. If using an external clock, this signal period becomes: $f_{PWM} = f_{SYNC}/32$. The custom waveforms only need to be programmed once for each output. After the values have been set, the I²C-compatible interface toggles start and stop times for the lighting pattern. Timing control features, like the one found in the LM2755, are an ideal tool for any peripheral lighting needs.



FIGURE 4. LM2755 LED Timing Control

Enabling New Display Technologies

Efficient power conversion for white LEDs provides diminishing returns. Designing towards organic LED (OLED) displays can solve a designer's energy problems. Normal LCD displays rely on white LED backlighting, while OLED displays rely on each pixel to directly produce light, making colors more vibrant. OLED displays conserve more energy by illuminating the display without a backlight. To do this, every pixel is turned on and off as needed by circuitry controlling each column of pixels. A pixel can contain one diode for monochromatic displays, or three diodes (red, green, and blue) for full-color displays. Unlike LCD display modules, the diodes are embedded within the OLED display module. In the case of Passive Matrix OLED (PMOLED) displays, the power supply is used to pre-charge an entire row of pixels, usually with voltages beyond the normal 5V. The amount of voltage applied depends on the number of pixels in each row or the size of the OLED display panel.



FIGURE 5. LM4510 Typical Application Circuit

Figure 5 shows the LM4510 OLED driver which offers currents between 80 mA and 280 mA, and voltages between 5V and 18V from a Li-lon battery input. This switching regulator provides a small energy efficient solution by maximizing power efficiency up to 85% and eliminating an external Schottky diode. Smart solutions like the LM4510 pave the way for next generation technologies in portable media devices.

Consumers continue to demand greater media-centric functionality from their portable handheld devices, including highquality video, audio and other media-rich features, without sacrificing size or battery life. To meet this challenge, designers must develop innovative solutions that conserve energy and deliver the cutting-edge performance and design consumers have grown to expect from their portable handheld devices.

Notes

AN-1777

Notes

Products		Design Support	
Amplifiers	www.national.com/amplifiers	WEBENCH	www.national.com/webench
Audio	www.national.com/audio	Analog University	www.national.com/AU
Clock Conditioners	www.national.com/timing	App Notes	www.national.com/appnotes
Data Converters	www.national.com/adc	Distributors	www.national.com/contacts
Displays	www.national.com/displays	Green Compliance	www.national.com/quality/green
Ethernet	www.national.com/ethernet	Packaging	www.national.com/packaging
Interface	www.national.com/interface	Quality and Reliability	www.national.com/quality
LVDS	www.national.com/lvds	Reference Designs	www.national.com/refdesigns
Power Management	www.national.com/power	Feedback	www.national.com/feedback
Switching Regulators	www.national.com/switchers		
LDOs	www.national.com/ldo		
LED Lighting	www.national.com/led		
PowerWise	www.national.com/powerwise		
Serial Digital Interface (SDI)	www.national.com/sdi		
Temperature Sensors	www.national.com/tempsensors		
Wireless (PLL/VCO)	www.national.com/wireless		

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

Copyright© 2008 National Semiconductor Corporation

For the most current product information visit us at www.national.com



AN-1777

Americas Technical Support Center Email: new.feedback@nsc.com Tel: 1-800-272-9959

National Semiconductor

National Semiconductor Europe Technical Support Center Email: europe.support@nsc.com German Tel: +49 (0) 180 5010 771 English Tel: +44 (0) 870 850 4288 National Semiconductor Asia Pacific Technical Support Center Email: ap.support@nsc.com National Semiconductor Japan Technical Support Center Email: jpn.feedback@nsc.com