

Silently Powering Low Noise Applications

National Semiconductor
Application Note 1950
Frederik Dostal
July 28, 2009



Introduction

Highly sensitive signal path applications such as in the communications infrastructure need to be powered like any other electrical circuit. What makes this task especially difficult is that the power has to be provided without generating unwanted noise and without passing it along into the sensitive signal path circuitry. The power supplies must be as efficient as possible to save energy and to reduce unwanted heat generation. Mostly switch mode power supply circuits are implemented in such systems to fulfill the energy efficiency requirement. Unfortunately they are noisy by definition.


This article will explain how to implement a low noise switch mode power supply solution. It will introduce the sources of noise and explain how to minimize them. A big factor in noise generation and propagation is the printed circuit board layout. Important basics will be discussed. Circuit measurement techniques are also explained to guide a design engineer towards a low noise but efficient solution.

Powering Noise Sensitive Circuitry

An example for noise sensitive loads is an application used in wireless infrastructure systems such as a low IF receiver reference design using the ADC16V130 analog-to-digital converter as well as the LMK04031B clock conditioner which provides digitization and clocking. This reference design RD-170 can be downloaded from the National Semiconductor website (<http://www.national.com/rd/RDhtml/RD-170.html>). For noise purposes very often linear regulators need to be used as power supplies directly powering the load. Since linear regulators become very inefficient when the input to output voltage ratio becomes large, the combination of a switch mode power supply with a linear regulator becomes necessary. In such systems very special care has to be taken to limit the influence of a noisy switch mode power supply onto the signal path of the application.

There are three power management concepts often encountered to power very noise sensitive signal path circuitry. Figure 1 shows three typical concepts. In addition to the shown three concepts there are many more related topologies. In this article we will focus mostly on the bottom concept of Figure

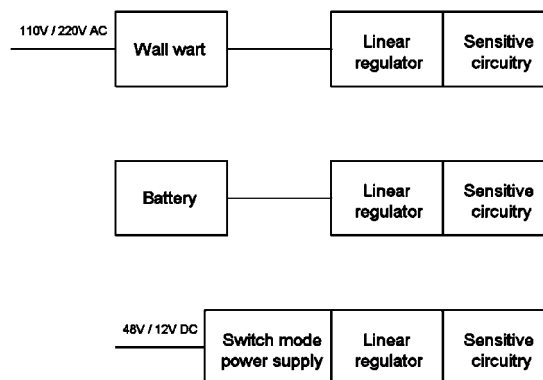1. The reference design RD-170 includes linear regulators as local low noise power supplies and a good solution for a switch mode power supply powering the board RD-170 or other noise sensitive circuitry is discussed in this article.




30092801

FIGURE 1. Typical Concepts of How to Power Very Noise Sensitive Circuitry

Different Point of Load Topologies and Typical Noise

There are different switch mode point of load power management topologies. Figure 2 shows the most common basic topologies. Each one of them uses an inductor and a power switch consisting either of two transistors or one transistor and a diode. When looking at the inputs and outputs of the different topologies, one can see that some are relatively silent and some are relatively noisy. The high noise (high EMI) is caused when there is no inductor close to the connection. In such cases the connection sees large currents which are turning on and off in short amounts of time. In typical switch mode power supplies, the transition from no current to full current at the switch node is 15ns or less. This large di/dt causes high power voltage noise in the system.

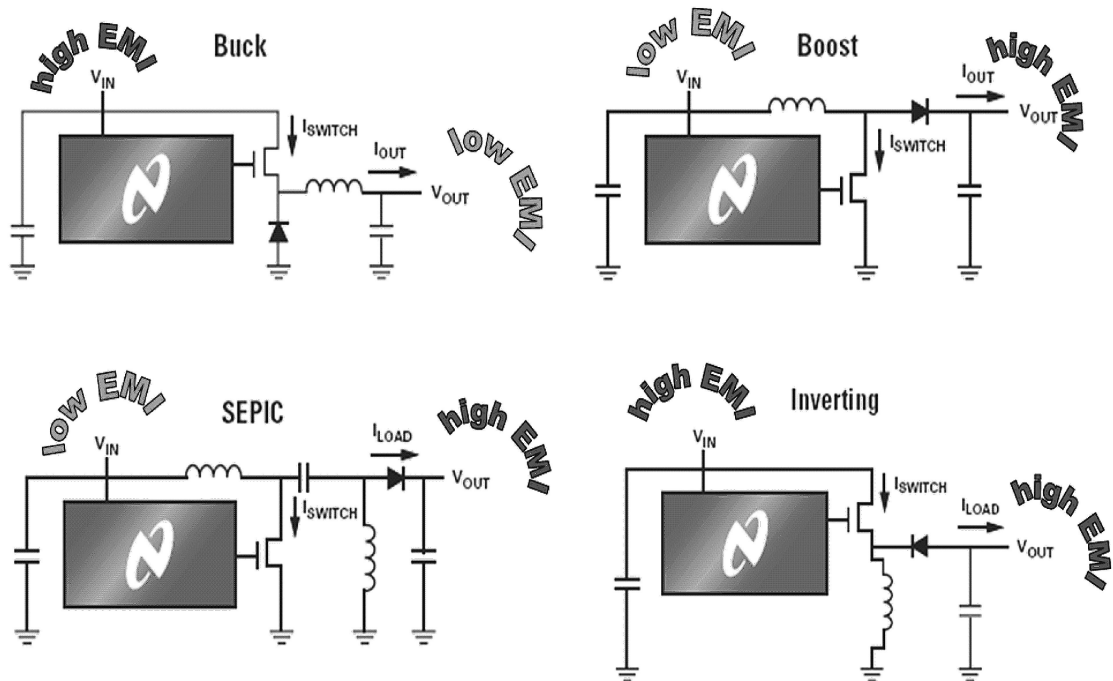

30092802

FIGURE 2. Low EMI and High EMI Terminals on Common DC to DC Topologies

Besides different possible topologies, each one can be realized with different control modes. Figure 3 shows a table of advantaged and disadvantages of the most common control modes. Hysteretic Mode Control has only a hysteretic comparator regulating the output voltage. It is a very fast control method but does not have a fixed switching frequency. This makes it not very suitable for low noise applications because additional filtering can not be optimized easily and it is hard

to predict the frequency of generated noise. Then there is Voltage Mode Control which regulates the output only by looking at the output voltage. It has its unique stability behavior and usually a little bit slower transient response compared to a Current Mode Control system. In Current Mode Control, besides the output voltage sensing, also the switch current is sensed. This makes the loop compensation a bit simpler and also may speed up transient responses.

| | Voltage Mode Control | Current Mode Control | Emulated Current Mode Control | Hysteretic Mode Control | Hysteretic with ripple injection |
|--|----------------------|----------------------|-------------------------------|-------------------------|----------------------------------|
| Loop speed | + | 0 | 0 | ++ | ++ |
| Ease of compensation | - | + | + | No compensation | No compensation |
| Fixed switching frequency | + | + | + | - | - |
| Low dropout voltage at high switching frequency | + | + | - | + | + |
| Large V_{in} to V_{out} difference at high switching frequencies | + | - | + | + | + |
| Low output voltage ripple possible | + | + | + | - | + |

30092809

FIGURE 3. Advantages and Disadvantages of Different Control Modes

Designing a Switch Mode Power Supply for Low Noise

One of the first tasks after having chosen the power conversion topology is the selection of external components while keeping in mind the low noise requirement. For the following considerations we look at the discrete components of a buck (step down) topology. Input capacitors in buck regulators are especially critical. Input filtering is very important due to the fact that the input connection of a buck sees significant AC currents. Possibly even an additional LC filter on the input might be needed to reduce system noise. Low ESR bypass capacitors are needed on the input to handle the fast di/dt currents. Often also some higher ESR input capacitor for input damping is required.

Regarding the power switch there are MOSFETs as well as bipolar transistors to choose from. Bipolar transistors are usually lower noise due to longer transition times and rounder switching edges. MOSFETs are usually preferred however due to their higher efficiency. In non synchronous buck regulators the low side switch is a free wheeling diode. A Schottky diode is a must due to their very small reverse recovery effect. Other diode types are not recommended since Schottkys are much faster than other types such as ultra fast diodes. Shielded inductors are usually better than unshielded ones for low noise applications. In general, the larger the inductance, the lower the inductor current ripple and the lower the output voltage ripple with a given output capacitor. However, if load transients are severe, a large inductance will show a larger load transient response.

The ESR and size of the output capacitors directly define the output ripple voltage with a given inductor size. Large low ESR output capacitors are beneficial for low noise.

Layout is the Biggest Factor for Low Noise

PCB traces have inductance. Thicker traces, effectively bigger wire diameter, will reduce the inductance, but only slightly. The area enclosed by the current loop, and there is always a loop, has the greatest effect on stray inductance. Keep current paths directly adjacent to their return paths, parallel on the same layer or directly above/below on adjacent layer. A typical inch of printed circuit board trace has about 20 nH of inductance. Assuming a transition time of 15 ns from 0A of current to 3A of current will yield a 4V potential offset across that inch long trace. This shows how important a tight layout is to switch mode power supplies especially regarding noise. Signals in a system are not voltages going from one pin to the next over wires.

Signals are currents that must go from a source of energy and they must return to that same source of energy. Currents always take the path of least impedance and not the path of least resistance. For DC currents the path of least impedance is the same as the path of least resistance. For AC currents like we see them in switch mode power supplies, the path of least impedance is often different than the path of least resistance.

Locating the AC Current Paths

In switch mode power supplies the most important board layout rule is to keep AC current traces as low inductance as possible. This means to keep these traces as short as possible and also on one layer with thick traces and preferably no vias. Any inductance in the AC current traces will cause large voltage off-sets which will produce excessive noise. Current flow diagrams show very quickly where these AC traces are. They also show that ground traces are just as much AC traces as other traces. AN-1229 from National Semiconductor explains more details.

Figure 4 shows on the top circuit the current flow as a dotted line in a buck converter in the transistor on-state. The middle circuit shows the current flow as a dotted line during the transistor off-state. The bottom circuit shows all the critical AC traces where current flow is changing from on-state to off-state. Figure 5 shows a layout implementation keeping these critical AC current traces as short as possible to avoid unnecessary trace inductance and to keep noise as low as possible.


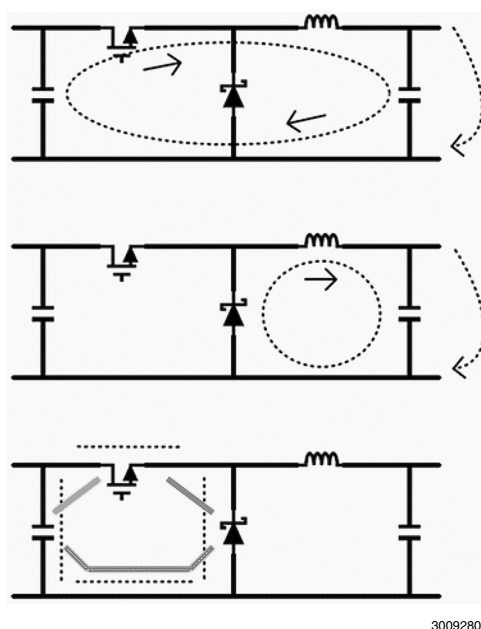


FIGURE 4. Current Flow in a Buck Converter

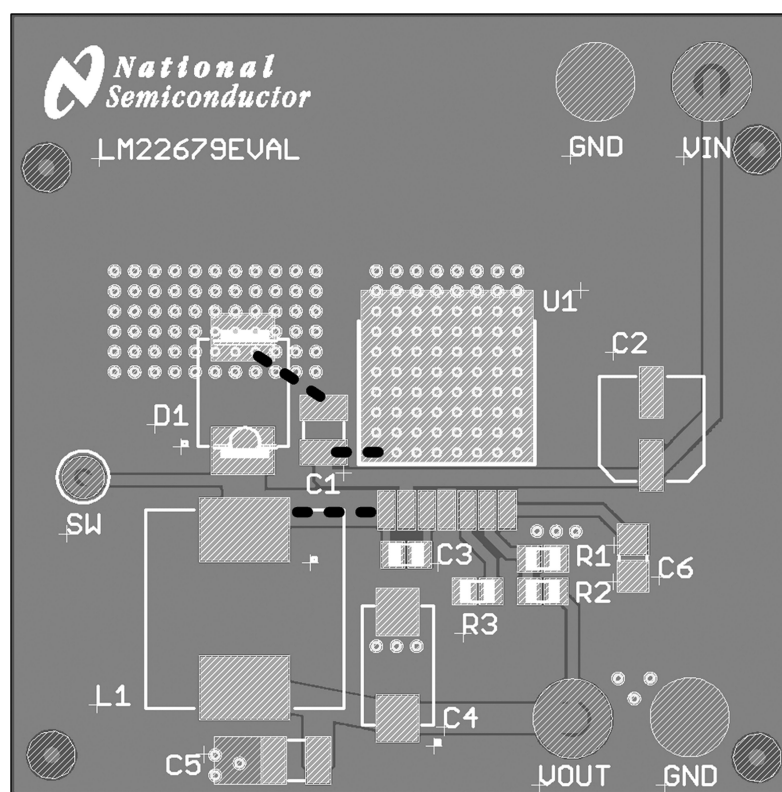

30092804

FIGURE 5. Layout Example with Short AC Traces from Figure 4 Indicated by Dotted Lines

Keeping Things Stable

If a power supply is supposed to be low noise, a very important step is to stabilize the power supply. Since any regulated power supply has a control loop it may be unstable. If the power supply is not stable, some over voltage protection will usually limit the voltage on the output causing higher output voltage ripple as well as unpredictable switching frequencies which are hard to filter. Instability can be observed by looking at the switch node voltage and observing if the falling edge of the signal is randomly jumping back and forth or if it is calm. Some movement of the falling edge is quite common, but it should not move more than about 5% of one switching period. AN-1889 from National Semiconductor is a step by step guide to taking a Bode plot measurement with only a signal generator and a standard oscilloscope. No network analyzer is required to do a thorough control loop measurement of a power supply.

The Beat Frequency Phenomenon

If more than one switch mode power supply is present in a system, the beat frequencies have to be considered. The power supply rejection ratio (PSRR) is usually very poor at high frequencies. The issue is that the switching noise from one switch mode power supply will pass to the output of a second parallel switch mode power supply. A solution in such situations is to use additional LC filtering on the input of the supplies or to synchronize the point of load regulators to share one switching frequency.

Other Helpful Considerations


A snubber can silence the switch node. Typically the switch node ringing is not a big concern regarding noise since it is a very low energy ringing. However, in some applications it is required to snub the high frequency ringing away. The ringing can be dissipated with a RC circuit (snubber) from the switch node to ground.

Additional LC filtering on the output for a high EMI output topology such as a SEPIC topology (see Figure 2) can reduce the output ripple voltage as well as noise dramatically. In some systems linear regulators are used in a cascaded fashion with a switch mode power supply to filter noise. Such a linear regulator post filtering is only useful if there is a longer trace (distance) and decoupled grounds between the switch mode power supply and the linear regulator. If they both are on the same board, an LC filter might be the cheaper and better alternative. A good application for using an LDO is if the switch mode power supply is on a different PCB than the linear regulator. Linear regulators also have the advantage of providing very good DC regulation compared to a LC filter approach.

What is Ripple Voltage and How is it Measured


Common language is misleading when it comes to describing noise in power supplies. What is regarded as switching noise is actually not noise in the common sense of random occurrences in frequency. The noise is deterministic at the switching frequency, transition period frequency and the multiples thereof. Figure 6 shows a typical output voltage measurement

of a step down switch mode power supply. There is some output ripple voltage which is about 5 mV. In addition to the ripple voltage, there is also some high frequency transition amplitude right at the switch transitions of the switch node. This noise shows about 70 mV of spikes and it may be line bound or electro magnetically coupled. The measurement was obtained by using an oscilloscope probe tip with a very short ground connection to the board under test. See Figure 7 for a picture of a good measurement connection.

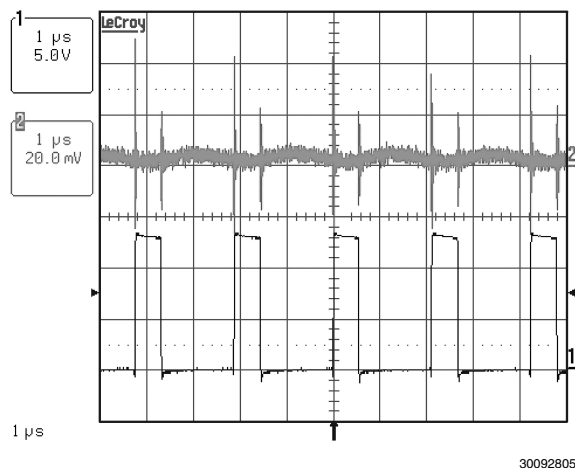

30092805

FIGURE 6. Typical Output Voltage and Switch Node Waveform

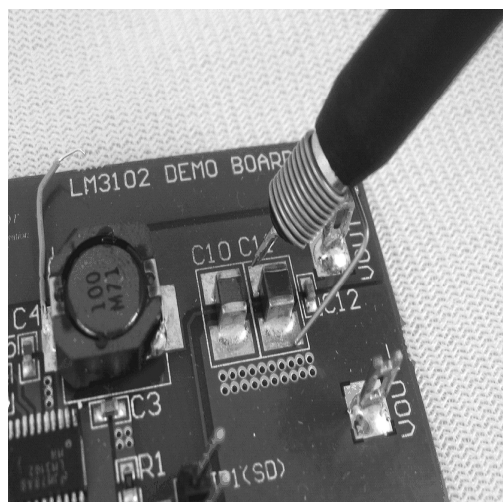


30092806

FIGURE 7. Good Measurement Setup to Measure Output Ripple Voltage


Figure 8 shows a bad measurement technique with a long ground trace connection. This ground cable is a high

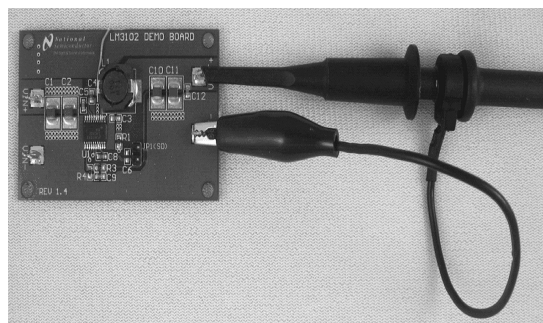impedance node and picks up switching noise like an antenna which is not real in that amplitude. Figure 9 shows the measurement result with the same board and operating conditions as used for Figure 6 but with a careless measurement setup as shown in Figure 8. The measurement shows spikes up to 1V peak to peak and they are only caused by poor measurement.



30092807

FIGURE 8. Poor Measurement Setup

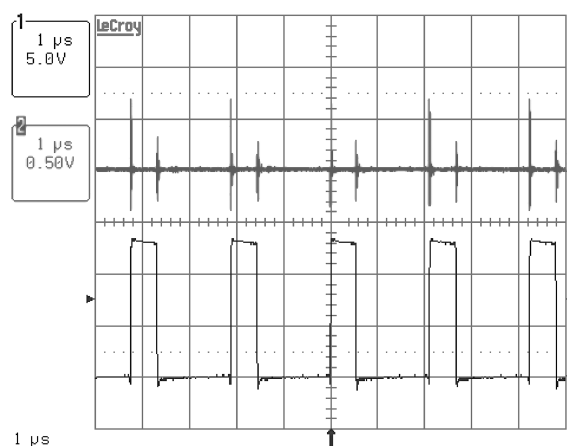

30092808

FIGURE 9. Measurement Results with a Bad Measurement Setup

Silence is Golden

For low noise signal path applications power supply noise is a critical consideration. As described in this text, many factors are important to consider when designing a power supply to power applications such as wireless infrastructure systems. With a good understanding of the issues involved, the right topology, control mode and layout can be selected and implemented. Also noise measurement techniques are very important to consider when optimizing for low noise.

Notes

For more National Semiconductor product information and proven design tools, visit the following Web sites at:

| Products | | Design Support | |
|--------------------------------|--|------------------------------|--|
| Amplifiers | www.national.com/amplifiers | WEBENCH® Tools | www.national.com/webench |
| Audio | www.national.com/audio | App Notes | www.national.com/appnotes |
| Clock and Timing | www.national.com/timing | Reference Designs | www.national.com/refdesigns |
| Data Converters | www.national.com/adac | Samples | www.national.com/samples |
| Interface | www.national.com/interface | Eval Boards | www.national.com/evalboards |
| LVDS | www.national.com/lvds | Packaging | www.national.com/packaging |
| Power Management | www.national.com/power | Green Compliance | www.national.com/quality/green |
| Switching Regulators | www.national.com/switchers | Distributors | www.national.com/contacts |
| LDOs | www.national.com/ldo | Quality and Reliability | www.national.com/quality |
| LED Lighting | www.national.com/led | Feedback/Support | www.national.com/feedback |
| Voltage Reference | www.national.com/vref | Design Made Easy | www.national.com/easy |
| PowerWise® Solutions | www.national.com/powerwise | Solutions | www.national.com/solutions |
| Serial Digital Interface (SDI) | www.national.com/sdi | Mil/Aero | www.national.com/milaero |
| Temperature Sensors | www.national.com/tempsensors | SolarMagic™ | www.national.com/solarmagic |
| Wireless (PLL/VCO) | www.national.com/wireless | PowerWise® Design University | www.national.com/training |

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

Copyright© 2009 National Semiconductor Corporation

For the most current product information visit us at www.national.com



**National Semiconductor
Americas Technical
Support Center**
Email: support@nsc.com
Tel: 1-800-272-9959

**National Semiconductor Europe
Technical Support Center**
Email: europe.support@nsc.com

**National Semiconductor Asia
Pacific Technical Support Center**
Email: ap.support@nsc.com

**National Semiconductor Japan
Technical Support Center**
Email: jpn.feedback@nsc.com