

LMH6554LE–EVAL High Speed Differential Amplifier Evaluation Board

National Semiconductor
Application Note 1945
Vannavong Philavanh
October 23, 2009



General Description

The LMH6554LE–EVAL evaluation board is designed to aid in the characterization of National Semiconductor's LMH6554 fully differential amplifier in an 14 lead LLP package. The LMH6554 is part of the LMH® high speed amplifier family.

Use the evaluation board as a guide for high frequency layout and as a tool to aid in device testing and characterization.

The evaluation board schematic is shown below in [Figure 1](#). Refer to the product datasheets for recommended for component values.

Basic Operation

The LMH6554LE–EVAL evaluation board has been set up to provide maximum flexibility for evaluating National's differential LMH6554 operational amplifier. The board supports fully differential operation as well as single-ended to differential and single-ended to single-ended operation. For fully differential operation, use resistors R_2 and R_3 to set the input impedance of the amplifier. The differential input resistance will be equal to $2 \cdot R_2 \parallel 2 \cdot R_{G_M}$. Where $R_2 = R_3$ and $R_{G_M} = R_{G_P}$. In this mode resistors R_{G_M} , R_{G_F} , R_{F_M} and R_{F_P} set the gain of the amplifier. Amplifier gain = $R_{F_M}/R_{G_M} = R_{F_P}/R_{G_P}$ where $R_{G_M} = R_{G_P}$ and $R_{F_M} = R_{F_P}$. Refer to Table 2 for more details on gain component value selections. For single-ended input mode of operation, the input and termination resistance must be properly configured to give the correct gain and input impedance (R_{IN}). For example, in the case of the LMH6554, if a gain of 2 V/V is desired, $R_2 = R_3 = 76.8\Omega$, $R_{G_M} = R_{G_P} = 90\Omega$, $R_{F_M} = R_{F_P} = 200\Omega$, C_2 and $R_{14} = \text{OPEN}$, $C_3 = 0.1\mu\text{F}$, and $R_{15} = 50\Omega$. Which will make $R_{IN} = 50\Omega$ at the most positive node of R_3 looking into R_{G_M} . Further details of single-ended input mode calculations for the LMH6554 can be found in the datasheet. Components $C_3 = 0.1\mu\text{F}$ and $R_{15} = 50\Omega$ should be used to AC-couple and balance the inputs, otherwise can be left empty. In this example the input signal would be connected to the VIN- input. Refer to Table 1 for more details on gain component value selections.

For differential output applications, load R_6 and R_7 with the desired values to match the output load and leave C_{14} and C_{15} empty. Typically to match a test equipment, $R_6 = R_7 = 50\Omega$.

If single-ended output is desired an output transformer such as the TC4-19 from Mini Circuits can be utilized. The TC4-19 has a 4:1 impedance ratio (2:1 turns/voltage ratio). This is particularly useful for interfacing to a 50Ω test equipment. When referencing the transformer datasheet, the LMH6554LE–EVAL evaluation board has the primary windings on the output side of the evaluation board and the amplifier is driving the secondary windings. This provides a step down transformation from the differential amplifier output to the test equipment. The center-tapped secondary winding also allows a differential to single ended conversion (Balun). The impedance seen by the differential amplifier = $(R_6 + R_7 +$

$R_L \cdot 4)$, where R_L is the impedance from pin 4 of the transformer to the load. For example, if $R_L = 50\Omega$ for the test equipment, to achieve an impedance of 500Ω seen by the LMH6554 differential output $R_6 = R_7 = 150\Omega$ with $C_{14} = C_{15} = R_{12} = R_{13} = 0\Omega$. The LMH6554LE–EVAL board is equipped with pads to add additional filtering schemes using $C_{14} - C_{18}$ and $R_8 - R_{13}$.

Pin 11 on the LMH6554 device is the enable (VEN) pin that can be used to disable the device with an external signal. Pin 11 and 14 have no internal package connections and should be connected to analog ground by using 0Ω resistors for R_4 and R_5 . Refer to the LMH6554 datasheet for more details.

Layout Considerations

Printed circuit board layout and supply bypassing play major roles in determining high frequency performance. When designing your own board use these evaluation boards as a guide and follow these steps to optimize high frequency performance:

1. Symmetry is of the utmost importance.
2. Use precision resistors 0.1% or 0.01%.
3. Use a ground plane.
4. Include large ($\sim 10\mu\text{F}$) ceramic capacitors on both supplies (C_{19} and C_{20}).
5. Near the device use ceramic capacitors $0.1\mu\text{F}$ for C_{22-25} and $0.01\mu\text{F}$ for C_7 , C_8 , C_{12} , and C_{13} from supplies to ground.
6. Remove the ground and power planes from under and around the part, especially the input and output pins.
7. Minimize all trace lengths.
8. Use terminated and matched transmission lines for long traces.

Sample artwork for the LMH6554LE–EVAL evaluation board is shown in [Figure 2](#) and [Figure 3](#).

Measurement Hints

Balance, CMRR and HD2 are highly dependent on resistor matching. Use 0.1 or 0.01% resistors.

The LMH6554LE–EVAL™ evaluation board is designed for differential or single-ended output measurements, but not both at the same time. When not using the transformer make sure to leave C_{14} and C_{15} empty. Likewise, when making single-ended output measurements populate components C_{14} , C_{15} , R_{12} and R_{13} .

Many differential amplifiers are optimized for the higher impedances represented by most ADCs.

On a differential amplifier both inputs are inverting, keep parasitic capacitance to a minimum on both inputs. Also, using probes of any kind on a differential circuit is not recommended.


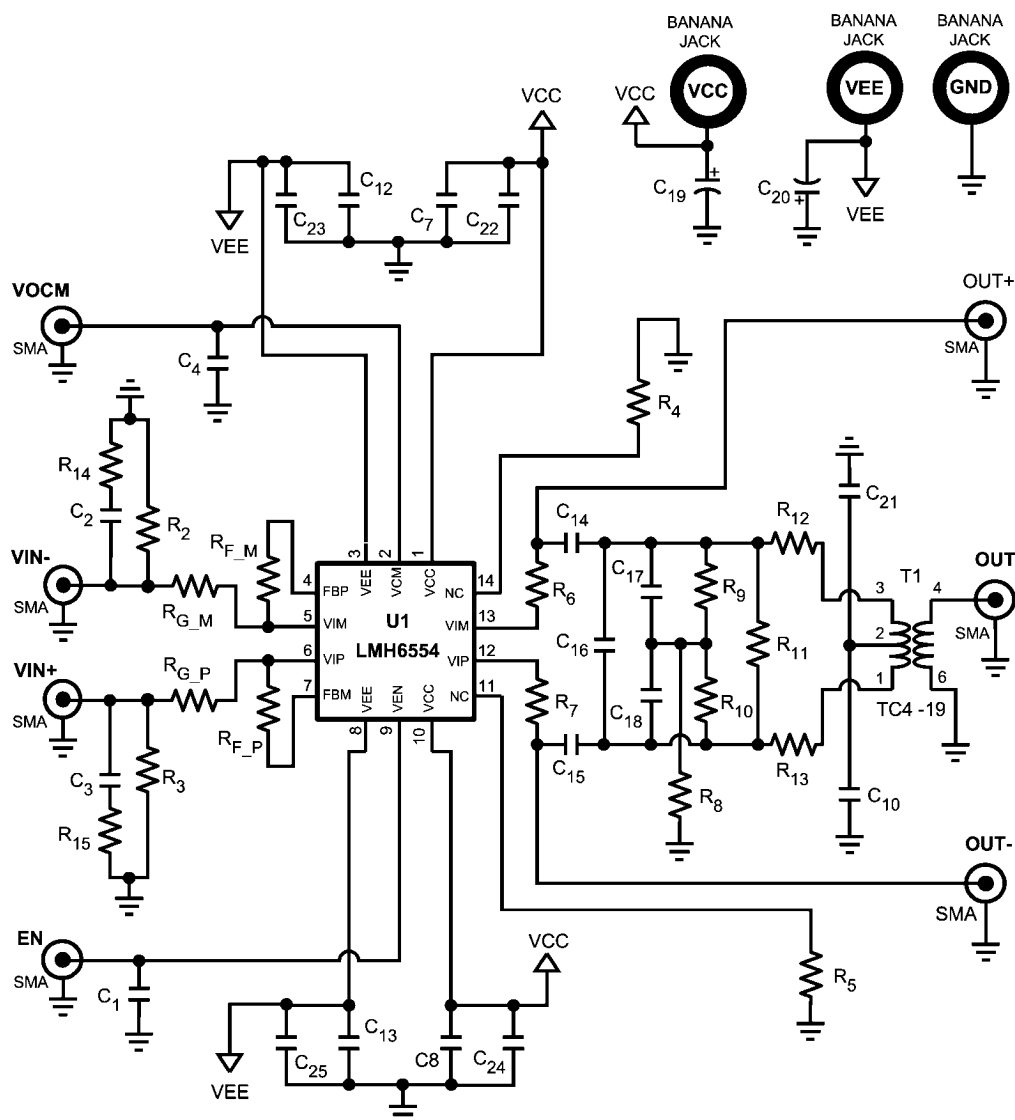


FIGURE 1. Board Schematic

Table 2. Differential Input Gain Resistor Selection for 50Ω System


Gain	$R_{F_M} = R_{F_P}$	$R_{G_M} = R_{G_P}$	R3	R_M	$R_6 = R_7$
0dB	200 Ω	191 Ω	62 Ω	27.7 Ω	50 Ω
6dB	200 Ω	91 Ω	76.8 Ω	30.3 Ω	50 Ω
12dB	200 Ω	35.7 Ω	147 Ω	37.3 Ω	50 Ω

Gain	$R_{F_M} = R_{F_P}$	$R_{G_M} = R_{G_P}$	$R2 = R3$	$R6 = R7$
0dB	200Ω	200Ω	66.67Ω	50Ω
6dB	200Ω	100Ω	100Ω	50Ω
12dB	200Ω	50Ω	—	50Ω

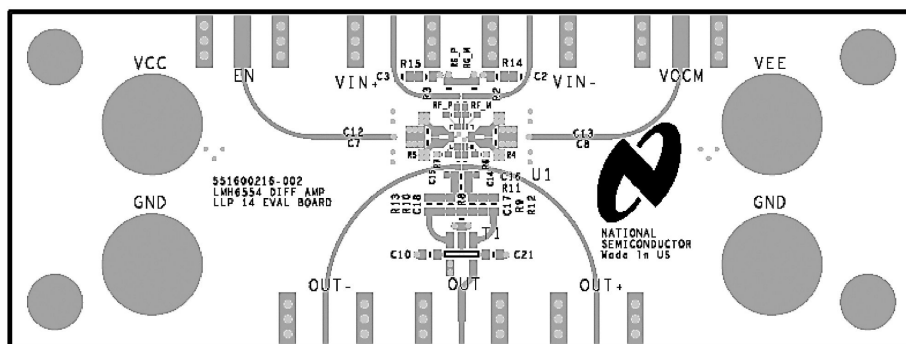

30091201

FIGURE 2. Board Layout Top View

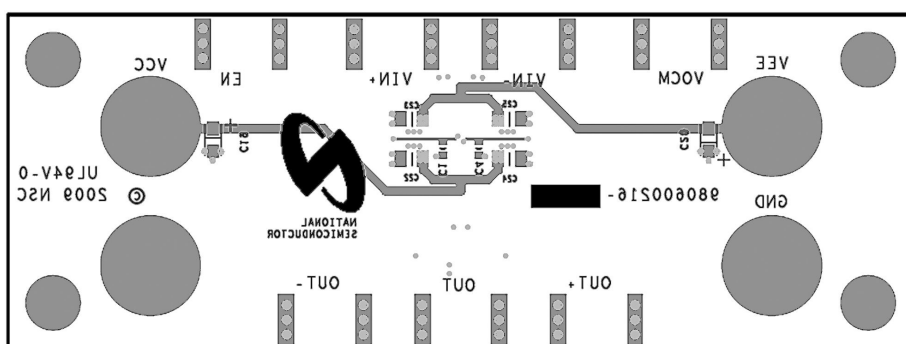

30091202

FIGURE 3. Board Layout Bottom View

Notes

For more National Semiconductor product information and proven design tools, visit the following Web sites at:

Products		Design Support	
Amplifiers	www.national.com/amplifiers	WEBENCH® Tools	www.national.com/webench
Audio	www.national.com/audio	App Notes	www.national.com/appnotes
Clock and Timing	www.national.com/timing	Reference Designs	www.national.com/refdesigns
Data Converters	www.national.com/adac	Samples	www.national.com/samples
Interface	www.national.com/interface	Eval Boards	www.national.com/evalboards
LVDS	www.national.com/lvds	Packaging	www.national.com/packaging
Power Management	www.national.com/power	Green Compliance	www.national.com/quality/green
Switching Regulators	www.national.com/switchers	Distributors	www.national.com/contacts
LDOs	www.national.com/ldo	Quality and Reliability	www.national.com/quality
LED Lighting	www.national.com/led	Feedback/Support	www.national.com/feedback
Voltage Reference	www.national.com/vref	Design Made Easy	www.national.com/easy
PowerWise® Solutions	www.national.com/powerwise	Solutions	www.national.com/solutions
Serial Digital Interface (SDI)	www.national.com/sdi	Mil/Aero	www.national.com/milaero
Temperature Sensors	www.national.com/tempsensors	SolarMagic™	www.national.com/solarmagic
Wireless (PLL/VCO)	www.national.com/wireless	PowerWise® Design University	www.national.com/training

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

Copyright© 2009 National Semiconductor Corporation

For the most current product information visit us at www.national.com



**National Semiconductor
Americas Technical
Support Center**
Email: support@nsc.com
Tel: 1-800-272-9959

**National Semiconductor Europe
Technical Support Center**
Email: europe.support@nsc.com

**National Semiconductor Asia
Pacific Technical Support Center**
Email: ap.support@nsc.com

**National Semiconductor Japan
Technical Support Center**
Email: jpn.feedback@nsc.com