

# LMR24220 Multi-Rail Reference Board

National Semiconductor  
Application Note 2193  
Marc Davis-Marsh  
September 22, 2011



## Introduction

The LMR24220 Multi-Rail reference board implements an extremely compact solution. It is designed to convert from 12V or 24V rails down to typical point-of-load voltages of 3.3V, 1.8V and 1.2V. This design utilizes an LMR24220 Nano Regulator and two LMZ10501 Nano Modules to demonstrate a complete solution for space constrained multi-rail applications.

The LMR24220 Nano Regulator is ideal for intermediate rail conversions and can withstand input voltages up to 42V. It uses a constant on-time (COT) with emulated ripple mode architecture that requires no loop compensation and allows the use of low ESR ceramic capacitors. To further reduce conducted noise on the input supply a pi filter has been implemented on the LMR24220. The LMZ10501 Nano Module is ideal at the point-of-load and uses a current mode architecture combined with an integrated inductor for high efficiency, low noise, and low EMI.

The complete solution size is 20.32 x 13.34 x 2mm with all components placed on a single side. The board can be plugged into a standard 8-pin header with 100 mil spacing and total thickness less than 100mils for ease of prototyping.

## Features

- 5V to 32V Input Voltage Range
- 3.3V / 1.8V / 1.2V Output Voltage Rails
- Up to 1000 mA Output Current Per Rail
- Small Solution Size (20.32 x 13.34 x 2mm)
- No External Compensation Required

## Shutdown Operation

The reference board includes a resistor divider that implements an Under Voltage Lockout (UVLO) that disables the part when  $V_{IN}$  is below 4V. The threshold for the UVLO can be adjusted to suit the needs of the application.

$$R_{et} = (V_{UVLO} * 10K - 12.4K)$$

The midpoint of the resistor divider is clamped to 4.3V by diode D2 so that the EN pin voltage of the LMR24220 does not exceed 7V. The midpoint is also tied to pin 8 of the header (EN). Use the EN pin to disable the device by pulling this node to GND. A logic signal may be applied to the post to test start-up and shutdown of the device.

## Adjusting the Output Voltage

The output voltage on the LMR24220 can be changed from 3.3V to another voltage by adjusting the feedback resistors using the following equation:


$$R1 = [(V_{OUT} / V_{FB}) - 1] * R2$$


Where  $V_{FB}$  is 0.8V.

The output voltage of either LMZ10501 can be changed from 1.8V/1.2V to another voltage by adjusting the feedback resistors using the following equation:

$$RB = [V_{OUT} / (5.875 - V_{OUT})] * RT$$

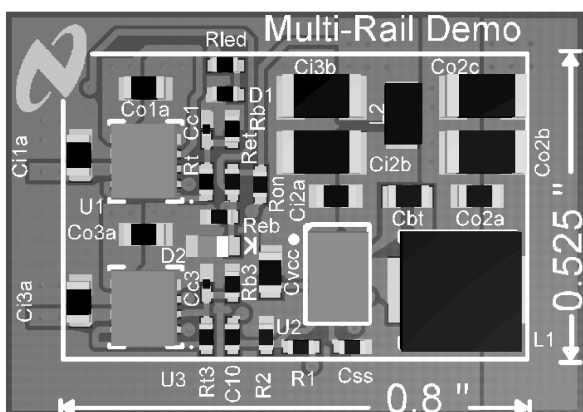For more information on component selection and features see the LMR24220 and LMZ10501 datasheets.



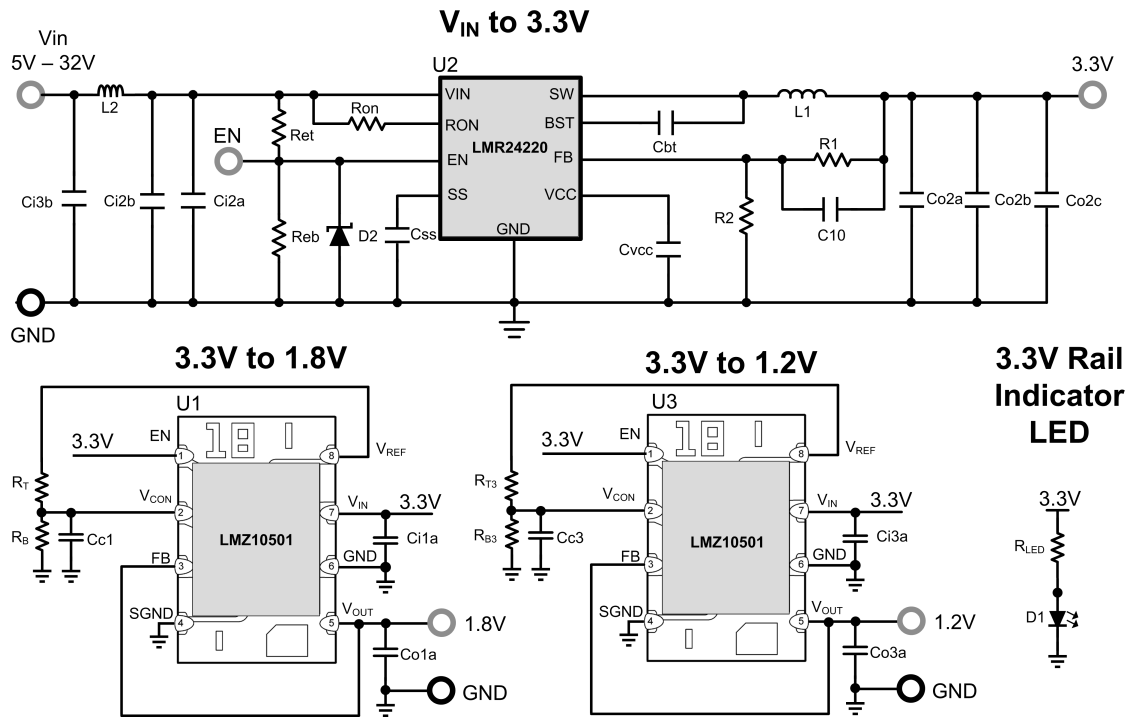

30174201


FIGURE 2. LMR24220 Reference Board Schematic

## Bill of Materials (BOM) LMR24220

Designation	Description	Size	Manufacturer Part #	Vendor
U1	LMZ10501	SE08A	LMZ10501SEX	National
U2	LMR24220	28-ball $\mu$ SMD	LMR24220TLX	National
U3	LMZ10501	SE08A	LMZ10501SEX	National
C10	Cap 10nF 25V X7R	0402	C1005X7R1E103K	TDK
Cbt, Ci2a, Co2a	Cap 0.047 $\mu$ F 50V X7R	0603	GRM188R71H473KA61D	Murata
Cc1, Cc3	Cap 1000pF 25V X7R	0201	GRM033R71E102KA01D	Murata
Ci1a, Ci3a, Co1a, Co3a	Cap 4.7 $\mu$ F 6.3V X5R	0603	C1608X5R0J475M	TDK
Ci2b, Ci3b	Cap 10 $\mu$ F 35V X5R	1206	GRM31CR6YA106KA12L	Murata
Ci2b, Ci3b (alt)	Cap 10 $\mu$ F 50V X5R	1210	UMK325BJ106MMT	Taiyo Yuden
Co2b, Co2c	Cap 47 $\mu$ F 6.3V X5R	1206	C3216X5R0J476M	TDK
Css	Cap 22nF 16V X7R	0402	C1005X7R1C223K	TDK
Cvcc	Cap 1 $\mu$ F 25V X7R	0805	GCM21BR71E105KA56L	Murata
D1	LED, Blue, SMD	0402	LNJ947W8CRA	Panasonic
D2	Zener Diode 4.3V 200mW	SOD-523F	MM5Z4V3	Fairchild
L1	Shielded Inductor 6.8 $\mu$ H 2.4A	(5.49mm x 5.18mm x 2.00mm)	IHLP2020BZER6R8M01	Vishay-Dale
L2	LTCC Inductor 2.2 $\mu$ H 0.9A	(2.50mm x 1.50mm x 1.20mm)	CPL2512T2R2M	Vishay-Dale
R1	RES, 6.81k ohm, 1%, 0.063W	0402	CRCW04026K81FKED	Vishay-Dale

Designation	Description	Size	Manufacturer Part #	Vendor
R2	RES, 2.21k ohm, 1%, 0.063W	0402	CRCW04022K21FKED	Vishay-Dale
Reb	RES, 12.4k ohm, 1%, 0.063W	0402	CRCW040212K4FKED	Vishay-Dale
Ret	RES, 28.0k ohm, 1%, 0.063W	0402	CRCW040228K0FKED	Vishay-Dale
Ron	RES, 76.8k ohm, 1%, 0.063W	0402	CRCW040276K8FKED	Vishay-Dale
Rb, Rb3	RES, 82.5k ohm, 1%, 0.063W	0402	CRCW040282K5FKED	Vishay-Dale
Rt	RES, 187k ohm, 1%, 0.063W	0402	CRCW0402187KFKED	Vishay-Dale
Rt3	RES, 316k ohm, 1%, 0.063W	0402	CRCW0402316KFKED	Vishay-Dale
Rled	RES, 332 ohm, 1%, 0.063W	0402	CRCW0402332RFKED	Vishay-Dale
J1	0.100" (2.54mm), Surface Mount Header, 1x8, Gold plated, Right Angle		961108-5500-AR-PR	3M
J2	0.100" (2.54 mm) Female Header: 1x8-Pin, Straight		960108-6202-AR	3M

Test Setup

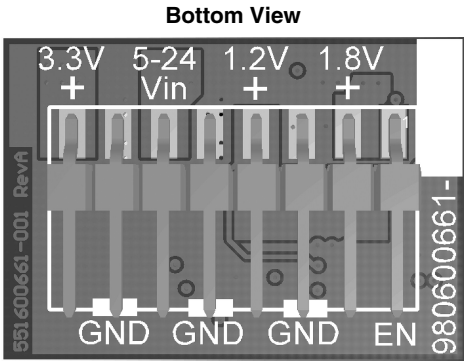

30174203

Pin Descriptions


Pin	Name	Description
1	3.3V	3.3V Output Voltage — Output from the LMR24220 (U2). Supplies current to both the LMZ10501s and any external load. Total Current up to 1.5Amps without airflow. 2Amps with airflow.
2, 4, 6	GND	Ground — Reference point for all stated voltages.
3	VIN	Input supply — Nominal operating range is 5V to 32V. To increase the maximum operating voltage of the design to 42V, use the alternate Ci2b, and Ci3b capacitors called out in the BOM.
5	1.2V	1.2V Output Voltage — Output from the LMZ10501 (U1). Load current up to 1A.
7	1.8V	1.8V Output Voltage — Output from the LMZ10501 (U3). Load current up to 1A.
8	EN	Enable — Input to the LMR24220 precision enable comparator. Rising threshold is 1.274V typical. Leave floating to allow the resistor divider to enable the reference board when $V_{IN}$ exceeds 4V.

Demonstration Board Quick Setup Procedures

Step	Description	Notes
1	Connect a power supply to $V_{IN}$ terminal	$V_{IN}$ range: 5V to 32V
2	Connect a load to 3.3V / 1.8V / 1.2V terminals	$I_{OUT}$ range: 0A to 1.0A
3	EN should be left floating for normal operation. Short this to ground to shutdown the part	
4	Set $V_{IN}$ = 12V, with 0A load applied, check 3.3V / 1.8V / 1.2V rails with a voltmeter	
5	Apply a 1.0A load to any rail and check 3.3V / 1.8V / 1.2V rails with a voltmeter	

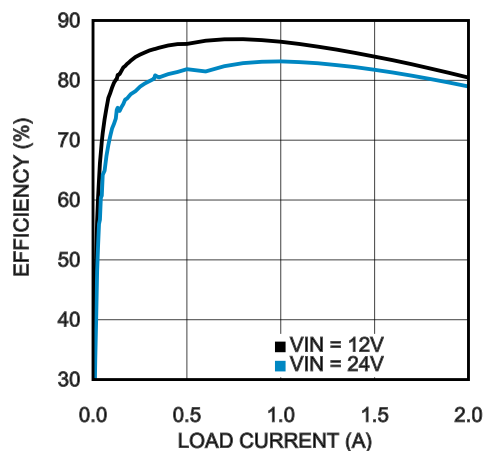
## Typical Performance Characteristics

Efficiency vs. Load Current LMR24220,  $V_{OUT} = 3.3V$




30174204

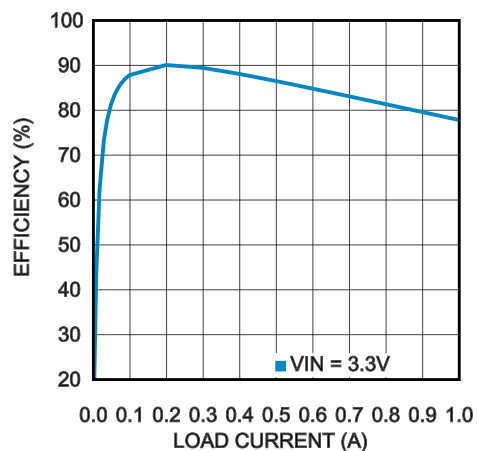Efficiency vs. Load Current LMZ10501,  $V_{OUT} = 1.2V$




30174205

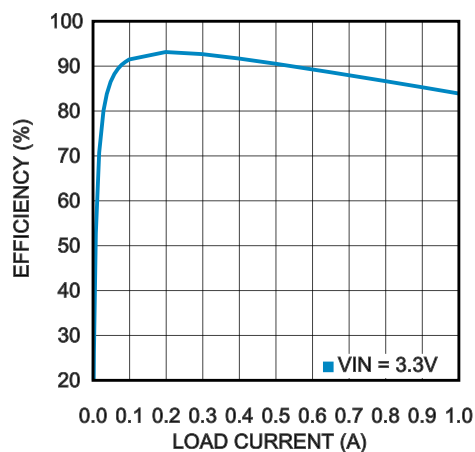Efficiency vs. Load Current LMZ10501,  $V_{OUT} = 1.8V$




30174206

Startup Waveform

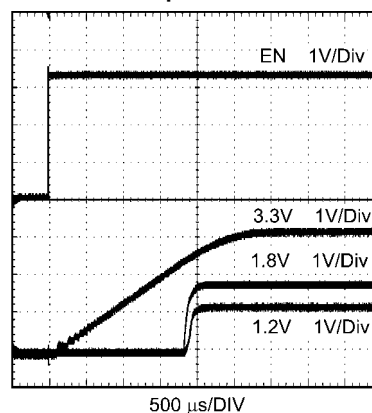


30174207

Output Ripple

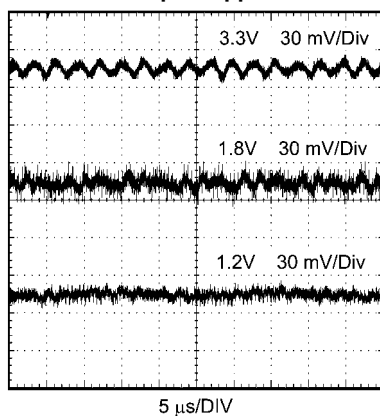


30174214

Output Power Tradeoff

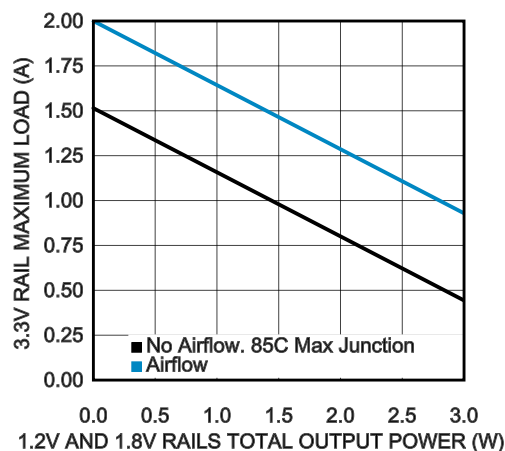


30174215

Layout

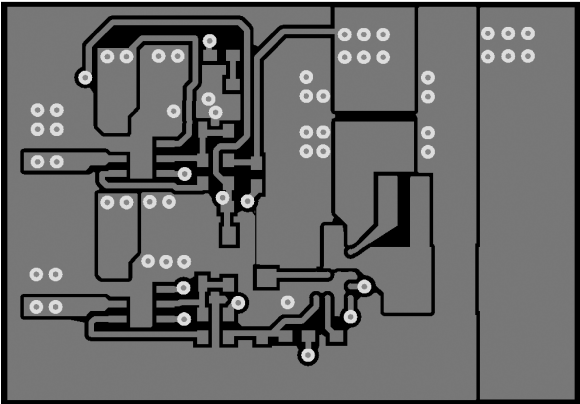


Top Layer

30174208

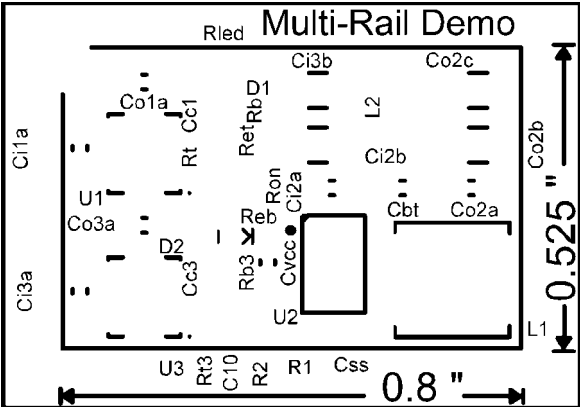


Top Overlay

30174209

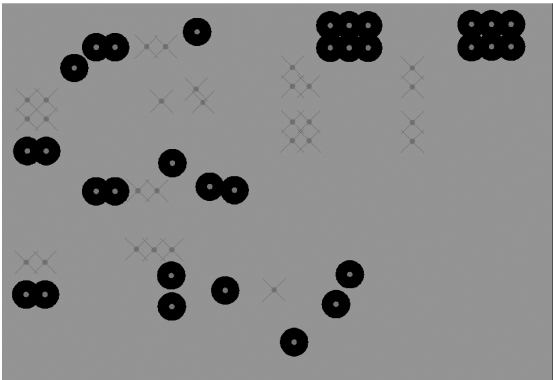


Mid Layer1 (GND)

30174210

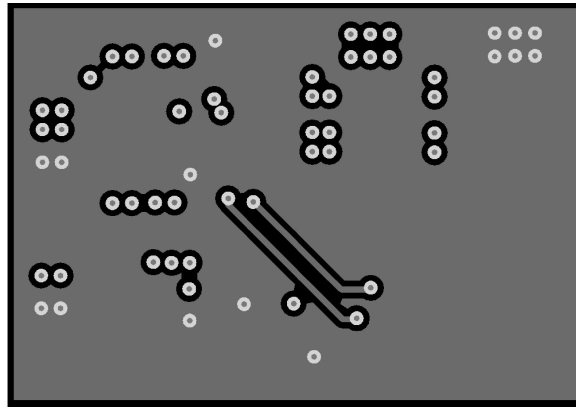


30174211

Mid Layer2 (3.3V)

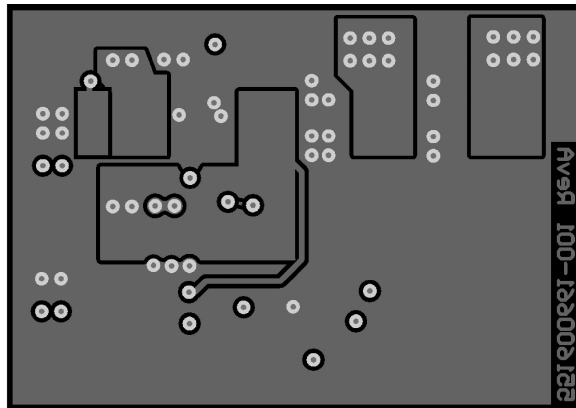

30174212

Bottom Layer

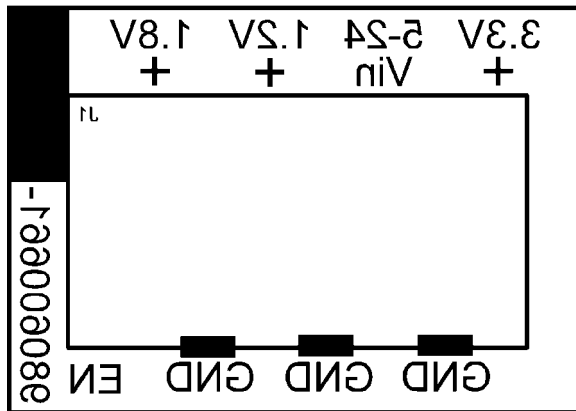

30174213

Bottom Overlay

For more National Semiconductor product information and proven design tools, visit the following Web sites at:  
[www.national.com](http://www.national.com)

Products		Design Support	
Amplifiers	<a href="http://www.national.com/amplifiers">www.national.com/amplifiers</a>	WEBENCH® Tools	<a href="http://www.national.com/webench">www.national.com/webench</a>
Audio	<a href="http://www.national.com/audio">www.national.com/audio</a>	App Notes	<a href="http://www.national.com/appnotes">www.national.com/appnotes</a>
Clock and Timing	<a href="http://www.national.com/timing">www.national.com/timing</a>	Reference Designs	<a href="http://www.national.com/refdesigns">www.national.com/refdesigns</a>
Data Converters	<a href="http://www.national.com/adc">www.national.com/adc</a>	Samples	<a href="http://www.national.com/samples">www.national.com/samples</a>
Interface	<a href="http://www.national.com/interface">www.national.com/interface</a>	Eval Boards	<a href="http://www.national.com/evalboards">www.national.com/evalboards</a>
LVDS	<a href="http://www.national.com/lvds">www.national.com/lvds</a>	Packaging	<a href="http://www.national.com/packaging">www.national.com/packaging</a>
Power Management	<a href="http://www.national.com/power">www.national.com/power</a>	Green Compliance	<a href="http://www.national.com/quality/green">www.national.com/quality/green</a>
Switching Regulators	<a href="http://www.national.com/switchers">www.national.com/switchers</a>	Distributors	<a href="http://www.national.com/contacts">www.national.com/contacts</a>
LDOs	<a href="http://www.national.com/ldo">www.national.com/ldo</a>	Quality and Reliability	<a href="http://www.national.com/quality">www.national.com/quality</a>
LED Lighting	<a href="http://www.national.com/led">www.national.com/led</a>	Feedback/Support	<a href="http://www.national.com/feedback">www.national.com/feedback</a>
Voltage References	<a href="http://www.national.com/vref">www.national.com/vref</a>	Design Made Easy	<a href="http://www.national.com/easy">www.national.com/easy</a>
PowerWise® Solutions	<a href="http://www.national.com/powerwise">www.national.com/powerwise</a>	Applications & Markets	<a href="http://www.national.com/solutions">www.national.com/solutions</a>
Serial Digital Interface (SDI)	<a href="http://www.national.com/sdi">www.national.com/sdi</a>	Mil/Aero	<a href="http://www.national.com/milaero">www.national.com/milaero</a>
Temperature Sensors	<a href="http://www.national.com/tempsensors">www.national.com/tempsensors</a>	SolarMagic™	<a href="http://www.national.com/solarmagic">www.national.com/solarmagic</a>
PLL/VCO	<a href="http://www.national.com/wireless">www.national.com/wireless</a>	PowerWise® Design University	<a href="http://www.national.com/training">www.national.com/training</a>

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

#### LIFE SUPPORT POLICY

**NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION.** As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

Copyright© 2011 National Semiconductor Corporation

For the most current product information visit us at [www.national.com](http://www.national.com)



**National Semiconductor  
Americas Technical  
Support Center**  
Email: [support@nsc.com](mailto:support@nsc.com)  
Tel: 1-800-272-9959

**National Semiconductor Europe  
Technical Support Center**  
Email: [europe.support@nsc.com](mailto:europe.support@nsc.com)

**National Semiconductor Asia  
Pacific Technical Support Center**  
Email: [ap.support@nsc.com](mailto:ap.support@nsc.com)

**National Semiconductor Japan  
Technical Support Center**  
Email: [jpn.feedback@nsc.com](mailto:jpn.feedback@nsc.com)