

LM3103 Demonstration Board Reference Design

National Semiconductor
Application Note 1678
LK Wong
October 2007




Introduction

The LM3103 Step Down Switching Regulator features all required functions to implement a cost effective, efficient buck power converter capable of supplying 0.75A to loads. The Constant On-Time (COT) regulation scheme requires no loop compensation, results in a fast load transient response and simple circuit implementation which allows a low component count, and consequently very small overall board space is required for a typical application. The regulator can function properly even with an all ceramic output capacitor network, and does not rely on the output capacitor's ESR for stability. The operating frequency remains constant with line variations

due to the inverse relationship between the input voltage and the on-time. Protection features include output over-voltage protection, thermal shutdown, V_{CC} under-voltage lock-out, gate drive under-voltage lock-out. The LM3103 is available in the thermally enhanced eTSSOP-16 package.


This application note details the design of a demonstration board which provides a 3.3V output voltage with 0.75A load capability for a wide input voltage range from 8V to 42V. The demonstration board schematic, PCB layout, Bill of Materials, and circuit design descriptions are shown. Typical performance and operating waveforms are also provided for reference.

Demonstration Board Schematic and PCB

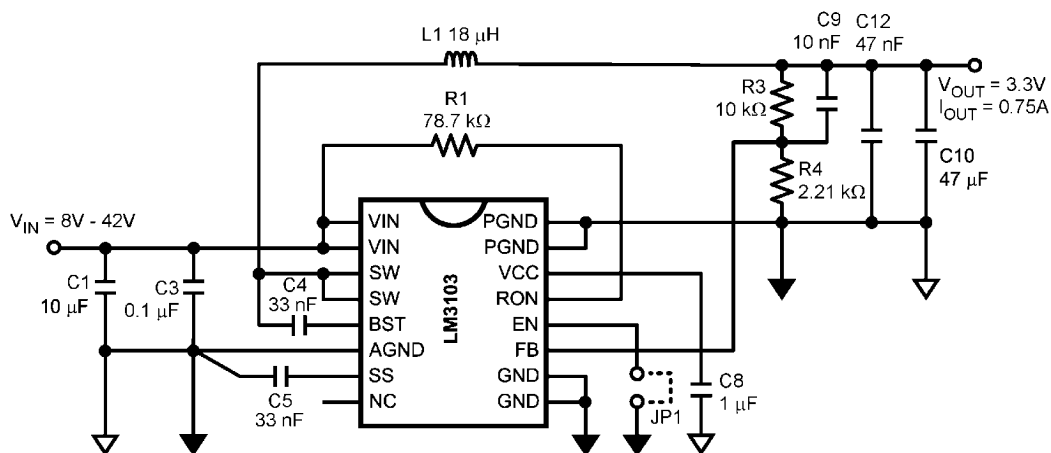

30028801

FIGURE 1. LM3103 Demonstration Board Schematic

 

30028802

FIGURE 2. LM3103 Demonstration Board PCB Top Overlay

 


FIGURE 3. LM3103 Demonstration Board PCB Top View

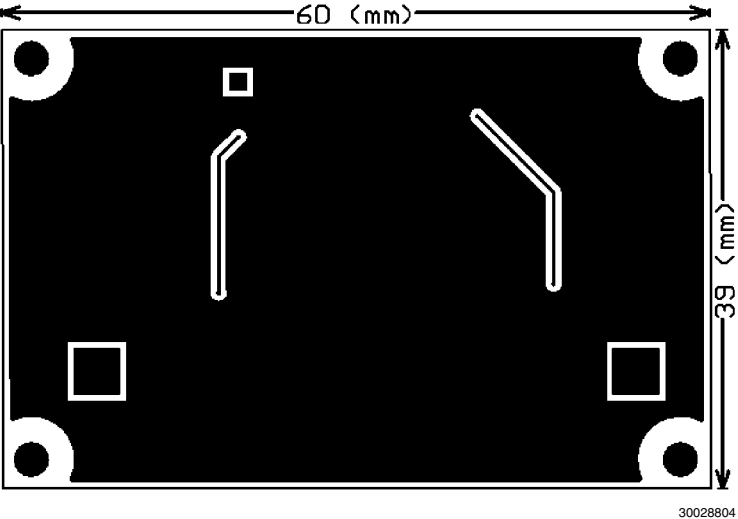


FIGURE 4. LM3103 Demonstration Board PCB Bottom View

Demonstration Board Quick Setup Procedures

Step	Description	Notes
1	Connect a power supply to VIN terminals	V_{IN} range: 8V to 42V
2	Connect a load to VOUT terminals	I_{OUT} range: 0A to 0.75A
3	SD (JP1) should be left open for normal operation. Short this jumper to shutdown	
4	Set $V_{IN} = 18V$, with 0A load applied, check V_{OUT} with a voltmeter	Nominal 3.3V
5	Apply 0.75A load and check V_{OUT}	Nominal 3.3V
6	Short output terminals and check the short circuit current with an ammeter	Nominal 1.05A
7	Short SD (JP1) to check the shutdown function	

Demonstration Board Performance Characteristic

Description	Symbol	Condition	Min	Typ	Max	Unit
Input Voltage	V_{IN}		8	18	42	V
Output Voltage	V_{OUT}		3.2	3.3	3.4	V
Output Current	I_{OUT}		0	-	0.75	A
Output Voltage Ripple	$V_{OUT(Ripple)}$		-	-	50	mVp-p
Output Voltage Regulation	ΔV_{OUT}	ALL V_{IN} and I_{OUT} Conditions	-2		+2	%
Efficiency		$V_{IN} = 8V$	85		91	%
		$V_{IN} = 24V$	71		84	%
		$V_{IN} = 42V$ ($I_{OUT} = 0.1A$ to $0.75A$)	59		78	%
Output Short Current Limit	I_{LIM-SC}			1.05		A

Design Procedure

The LM3103 is easy to use compared with other devices available on the market because it integrates all key components, including both the main and synchronous power MOSFETs, in a single package and requires no loop compensation owing to the use of the Constant On-Time (COT) hysteretic control scheme. The design of the demonstration board in this application note is detailed below.

Design Parameters:

$V_{IN} = 8V$ to $42V$, typical $18V$

$V_{OUT} = 3.3V$

$I_{OUT} = 0.75A$

Step 1: Calculate the feedback resistors

The ratio of the feedback resistor can be calculated from the following equation:

$$\frac{R3}{R4} = \frac{V_{OUT}}{0.6} - 1$$

As a general practice, R3 and R4 should be chosen from standard 1% resistor values in the range of $1.0\text{ k}\Omega$ to $10\text{ k}\Omega$ satisfying the above ratio. Now, select $R3 = 10\text{ k}\Omega$, with $V_{OUT} = 3.3V$,

$$R4 = \frac{10\text{ k}\Omega}{\left(\frac{V_{OUT}}{0.6} - 1\right)} = 2.22\text{ k}\Omega$$

Step 2: Calculate the on-time setting resistor

The switching frequency f_{SW} of the demonstration board is affected by the on-time t_{on} of the LM3103, which is determined by R1. If f_{SW} and V_{OUT} are determined, R1 can be calculated as follows:

$$R1 = \frac{V_{OUT}}{8.3 \times 10^{-11} \times f_{SW}}$$

For this demonstration board design, $V_{OUT} = 3.3V$ and $f_{SW} = 500\text{ kHz}$ are chosen. As a result, $R1 = 78.52\text{ k}\Omega$. To ensure that the on-time is larger than the minimum limit, which is 100 ns , the value of R1 must satisfy the following equation:

$$R1 \geq \frac{V_{IN(MAX)} \times 100\text{ ns}}{8.3 \times 10^{-11}}$$


Now the maximum V_{IN} is $42V$, the calculated R1 satisfies the above equation.

Step 3: Determine the inductance

The main parameter affected by the inductor is the amplitude of the inductor current ripple I_{LR} . Once I_{LR} is selected, L1 can be determined by:

$$L1 = \frac{V_{OUT} \times (V_{IN} - V_{OUT})}{I_{LR} \times f_{SW} \times V_{IN}}$$

 For this demonstration board design, $I_{LR} = 0.3A$ is selected. Now $V_{IN} = 18V$, $V_{OUT} = 3.3V$, and $f_{SW} = 500\text{ kHz}$. As a result, $L = 17.97\text{ }\mu\text{H}$.



Inductor Selection for $V_{OUT} = 3.3V$

30028810

Step 4: Determine the value of other components

C1: The function of C1 is to supply most of the main MOSFET current during the on-time, and limit the voltage ripple at the VIN pin, assuming that the voltage source connecting to the VIN pin has finite output impedance. If the voltage source's dynamic impedance is high (effectively a current source), C1 supplies the average input current, but not the ripple current. At the maximum load current, when the main MOSFET turns on, the current to the VIN pin suddenly increases from zero to the lower peak of the inductor's ripple current and ramps up to the higher peak value. It then drops to zero at turn-off. The average current during the on-time is the load current. For a worst case calculation, C1 must be capable of supplying this average load current during the maximum on-time. C1 is calculated from:

$$C1 = \frac{I_{OUT} \times t_{on}}{\Delta V_{IN}}$$

where I_{OUT} is the load current, t_{on} is the maximum on-time, and ΔV_{IN} is the allowable ripple voltage at V_{IN} . In this demonstration board, a $10\text{ }\mu\text{F}$ capacitor is used.

C3: C3's purpose is to help avoid transients and ringing due to long lead inductance at the VIN pin. A low ESR $0.1\text{ }\mu\text{F}$ ceramic chip capacitor located close to the LM3103 is used in this demonstration board.

C4: A 33 nF high quality ceramic capacitor with low ESR is used for C4 since it supplies a surge current to charge the main MOSFET gate driver at turn-on. Low ESR also helps ensure a complete recharge during each off-time.

C5: The capacitor at the SS pin determines the soft-start time, i.e. the time for the reference voltage at the regulation comparator and the output voltage to reach their final value. The soft-start time is affected by the output capacitor, which can lengthen the time, and the charging of C5. The minimum soft-start time is determined by the following equation:

$$t_{ss} > 180\text{ }\mu\text{s} + \frac{C5 \times 0.6V}{70\text{ }\mu\text{A}}$$

In this demonstration board, a 33 nF capacitor is used for C5, and the corresponding soft-start time is about $600\text{ }\mu\text{s}$.

C8: The capacitor on the V_{CC} output provides not only noise filtering and stability, but also prevents false triggering of the V_{CC} UVLO at the main MOSFET on/off transitions. C8 should be no smaller than 1 μ F for stability, and should be a good quality, low ESR, ceramic capacitor.

C9: If the output voltage is higher than 1.6V, C9 is needed in the Discontinuous Conduction Mode to reduce the output ripple. In this demonstration board, a 10 nF capacitor is used.

C10: The output capacitor should generally be no smaller than 10 μ F. Experiment is usually necessary to determine the minimum value for the output capacitor, as the nature of the load may require a larger value. A load which creates significant transients requires a larger output capacitor than a fixed load. In this demonstration board, a 47 μ F capacitor is used to provide a low output ripple.

C12: C12 is a small value ceramic capacitor located close to the LM3103 to further suppress high frequency noise at V_{OUT} . A 47 nF capacitor is used in this demonstration board.

PC Board Layout

The LM3103 regulation, over-voltage, and current limit comparators are very fast so they will respond to short duration noise pulses. Layout is therefore critical for optimum performance. It must be as neat and compact as possible, and all external components must be as close to their associated pins of the LM3103 as possible. The loop formed by C1, the main and synchronous MOSFET internal to the LM3103, and the PGND pin should be as small as possible. The connection


from the PGND pin to the input capacitors should be as short and direct as possible. Vias should be added to connect the ground of the input capacitors to a ground plane, located as close to the capacitor as possible. The bootstrap capacitor C4 should be connected as close to the SW and BST pins as possible, and the connecting traces should be thick. The feedback resistors and capacitor R3, R4, and C9 should be close to the FB pin. A long trace running from V_{OUT} to R3 is generally acceptable since this is a low impedance node. Ground R4 directly to the AGND pin (pin 7). The output capacitor C10 should be connected close to the load and tied directly to the ground plane. The inductor L1 should be connected close to the SW pin with as short a trace as possible to reduce the potential for EMI (electromagnetic interference) generation. If it is expected that the internal dissipation of the LM3103 will produce excessive junction temperature during normal operation, making good use of the PC board's ground plane can help considerably to dissipate heat. The exposed pad on the bottom of the LM3103 IC package can be soldered to the ground plane, which should extend out from beneath the LM3103 to help dissipate heat. The exposed pad is internally connected to the LM3103 IC substrate. Additionally the use of thick traces, where possible, can help conduct heat away from the LM3103. Using numerous vias to connect the die attached pad to the ground plane is a good practice. Judicious positioning of the PC board within the end product, along with the use of any available air flow (forced or natural convection) can help reduce the junction temperature.

Bill of Materials


Designation	Description	Size	Manufacturer Part #	Vendor
C1	Cap 10 μ F 50V Y5V	1210	GRM32DF51H106ZA01L	Murata
C3	0603/X7R/0.1 μ F/50V	0603	ECJ1VB1H104K	Panasonic
C4, C5	0603/X7R/33000pF/50V	0603	ECJ1VB1H333K	Panasonic
C8	0603/X5R/1 μ F/10V	0603	GRM188R61A105KA61B	Murata
C9	0603/X7R/10000pF/50V	0603	ECJ1VB1H103K	Panasonic
			GRM188R71H103KA01B	Murata
C10	1210/X5R/47 μ F/6.3V	1210	ECJ4YB0J476M	Panasonic
			GRM32ER60J476ME20B	Murata
C12	0603/X7R/47000pF/50V	0603	ECJ1VB1H473K	Panasonic
R1	Resistor Chip 78.7k Ω F	0603	CRCW06037872F	Vishay
R3	Resistor Chip 10k Ω F	0603	CRCW06031002F	Vishay
R4	Resistor Chip 2.21k Ω F	0603	CRCW06032211F	Vishay
L1	Power Inductor 18 μ H 1.45A	6.8x6.8x3	CDR6D28MNNP-180NC	Sumida
	Power Inductor 18 μ H 1.7A	7.3x7.3x3.2	7447789118	Würth
U1	IC LM3103 MH	eTSSOP-16	LM3103 MH	National
PCB	LM3103 demo board			National

Typical Performance and Waveforms

 
All curves and waveforms are taken at $V_{IN} = 18V$ with the demonstration board and $T_A = 25^\circ C$ unless otherwise specified.




30028813

 

30028814

 


30028815

 


30028816

 DCM to CCM Transition
($V_{OUT} = 3.3V$, $0.01A - 0.75A$ Load)




30028817

 Load Transient
($V_{OUT} = 3.3V$, $0.075A - 0.75A$ Load,
Current slew-rate: $2.5A/\mu s$)




30028818

 Power Up
($V_{OUT} = 3.3V$, $0.75A$ Loaded)




30028819

 Enable Transient
($V_{OUT} = 3.3V$, $0.75A$ Loaded)



30028820

 Shutdown Transient
($V_{OUT} = 3.3V$, $0.75A$ Loaded)



30028821

Notes

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

Copyright© 2007 National Semiconductor Corporation

For the most current product information visit us at www.national.com



**National Semiconductor
Americas Customer
Support Center**
Email:
new.feedback@nsc.com
Tel: 1-800-272-9959

**National Semiconductor Europe
Customer Support Center**
Fax: +49 (0) 180-530-85-86
Email: europe.support@nsc.com
Deutsch Tel: +49 (0) 69 9508 6208
English Tel: +49 (0) 870 24 0 2171
Français Tel: +33 (0) 1 41 91 8790

**National Semiconductor Asia
Pacific Customer Support Center**
Email: ap.support@nsc.com

**National Semiconductor Japan
Customer Support Center**
Fax: 81-3-5639-7507
Email: jpn.feedback@nsc.com
Tel: 81-3-5639-7560