LM5006 Evaluation Board

National Semiconductor Application Note 2050 Dennis Morgan February 22, 2011

Introduction

The LM5006EVAL evaluation board provides the design engineer with a fully functional buck regulator, employing the constant on-time (COT) operating principle. This evaluation board provides a 5V output over an input range of 6V to 75V. The circuit delivers load currents to 500 mA, with current limit set at a nominal 1 Amp.

- Input Voltage: 6V to 75V
- Output Voltage: 5V
- Maximum load current: 500 mA
- Minimum load current: 0A
- Current Limit: 1 Amp (nominal)
- Measured Efficiency: 94.75% ($V_{IN} = 6V$, $I_{OUT} = 100$ mA)
- Nominal Switching Frequency: 200 kHz
- Size: 2.6 in. x 1.6 in.



FIGURE 1. Evaluation Board - Top Side

Theory of Operation

Refer to the evaluation board schematic in Figure 6. When the circuit is in regulation, the buck switch is on each cycle for a time determined by R1 and VIN according to the equation:

$$t_{on} = \frac{1.25 \times 10^{-10} \times (R1 + 500\Omega)}{V_{IN} - 0.5V} + 30 \text{ ns}$$

The on-time of this evaluation board ranges from ≈4.38 µs at VIN = 6V, to ≊351 ns at VIN = 75V. The on-time varies inversely with VIN to maintain a nearly constant switching frequency. At the end of each on-time the Minimum Off-Timer ensures the buck switch is off for at least 260 ns. In normal operation, the off-time is much longer. During the off-time, the load current is supplied by the output capacitor (C2). When the output voltage falls sufficiently that the voltage at FB is below 2.5V, the regulation comparator initiates a new on-time period. For stable, fixed frequency operation, a minimum of 25 mV of ripple is required at FB to switch the regulation comparator. Refer to the LM5006 data sheet for a more detailed block diagram, and a complete description of the various functional blocks.

Board Layout and Probing

The pictorial in *Figure 1* shows the placement of the circuit components. The following should be kept in mind when the board is powered:

1) When operating at high input voltage and high load current, forced air flow may be necessary.

2) The LM5006 may be hot to the touch when operating at high input voltage and high load current.

3) Use CAUTION when probing the circuit at high input voltages to prevent injury, as well as possible damage to the circuit.

4) At maximum load current, the wire size and length used to connect the load becomes important. Ensure there is not a significant drop in the wires between this evaluation board and the load.

Board Connection/Start-up

The input connections are made to the J1 connector. The load is connected to the J2 (OUT) and J3 (GND) terminals. Ensure the wires are adequately sized for the intended load current. Before start-up a voltmeter should be connected to the input terminals, and to the output terminals. The load current should be monitored with an ammeter or a current probe. It is rec-

ommended that the input voltage be increased gradually to 6V, at which time the output voltage should be 5V. If the output voltage is correct with 6V at VIN, then increase the input voltage as desired and proceed with evaluating the circuit. DO NOT EXCEED 75V AT VIN.

Output Ripple Control

The LM5006 requires a minimum of 25 mVp-p ripple at the FB pin, in phase with the switching waveform at the SW pin, for proper operation. The required ripple can be supplied from ripple at V_{OUT} , through the feedback resistors as described in Option A below. Options B and C provide lower output ripple with one or two additional components.

Option A) Lowest Cost Configuration: In this configuration R7 is installed in series with the output capacitance (C2). Since $\geq 25 \text{ mVp-p}$ are required at the FB pin, R7 must be chosen to generate $\geq 50 \text{ mVp-p}$ at V_{OUT} , knowing that the minimum ripple current in this circuit is $\approx 51 \text{ mAp-p}$ at minimum V_{IN} . Using 1 Ω for R7, the ripple at V_{OUT} ranges from $\approx 51 \text{ mVp-p}$ to $\approx 280 \text{ mVp-p}$ over the input voltage range. If the application can accept this ripple level, this is the most economical solution. The circuit is shown in *Figure 2*. See *Figure 9*. R8, C6, C7, and C8 are not used in this configuration.



FIGURE 2. Lowest Cost Configuration

Option B) Reduced Ripple Configuration: This configuration generates less ripple at V_{OUT} than option A above by the addition of one capacitor (C8) across R5, as shown in *Figure* 3.





Since the output ripple is passed by C8 to the FB pin with little or no attenuation, R7 can be reduced so the minimum ripple at V_{OUT} is \approx 25 mVp-p. The minimum value for Cff is calculated from:

$$C8 \geq \frac{3 \times t_{ON (max)}}{(R5//R6)}$$

where $t_{ON(max)}$ is the maximum on-time (at minimum V_{IN}), and R5//R6 is the parallel equivalent of the feedback resistors. The ripple at V_{OUT} ranges from 28 mVp-p to 159 mVp-p over the input voltage range. See *Figure 9*.

Option C) Minimum Ripple Configuration: To obtain minimum ripple at V_{OUT} , R7 is set to 0Ω , and R8, C6, and C7 are added to generate the required ripple for the FB pin. In this configuration, the output ripple is determined primarily by the characteristics of the output capacitance and the inductor's ripple current. See *Figure 9*.

The ripple voltage required by the FB pin is generated by R8, and C6 since the SW pin switches from -0.1V to V_{IN} , and the right end of C6 is a virtual ground. The values for R8 and C6 are chosen to generate a 30-100 mVp-p triangle waveform at their junction. That triangle wave is then coupled to the FB pin through C7. The following procedure is used to calculate values for R8, C6 and C7:

1) Calculate the voltage V_A :

v

$$V_{A} = V_{OUT} - (V_{SW} \times (1 - (V_{OUT}/V_{IN})))$$

where V_{SW} is the absolute value of the voltage at the SW pin during the off-time (typically 0.1V with Q1), and V_{IN} is the minimum input voltage. For this circuit, V_A calculates to 4.98V. This is the approximate DC voltage at the R8/C6 junction, and is used in the next equation.

2) Calculate the R8 x C6 product:

$$R8 \times C6 = \frac{(V_{IN} - V_A) \times t_{ON}}{\Delta V}$$

where t_{ON} is the maximum on-time, V_{IN} is the minimum input voltage, and ΔV is the desired ripple amplitude at the R8/C6 junction, 40 mVp-p for this example.

R8 x C6 =
$$\frac{(6V - 4.98V) \times 4.38 \ \mu s}{0.04}$$
 = 1.12 x 10⁻⁴

R8 and C6 are then chosen from standard value components to satisfy the above product. Typically C6 is 3000 to 10000 pF, and R8 is 10 k Ω to 300 k Ω . C7 is chosen large compared to C6, typically 0.1 µF. The ripple at V_{OUT} is typically less than 10 mVp-p. See *Figure 4* and *Figure 9*.





LG (Low Side Gate) Output

As supplied, this evaluation board employs synchronous rectification by using an N-Channel MOSFET (Q1) in place of a more traditional flyback diode. This board accepts any device in a SOT-23 package, such as a Vishay Si2328. The LG output pin switches between approximately 7.5V (the VCC voltage) and ground. The LG output is capable of sourcing 250 mA, and sinking 300 mA. An external gate driver is not needed if the selected MOSFET has a total gate charge of less than 10 nC.

Use of a synchronous rectifier generally results in higher circuit efficiency due to the lower voltage drop across the MOS-

FET as compared to a diode. See Figure 5. Another advantage of using a synchronous rectifier is that the circuit remains in continuous conduction mode, providing a relatively constant switching frequency, for all values of load current, including zero. If a flyback diode is used, the switching frequency decreases significantly at low values of load current when the circuit changes to discontinuous conduction mode.

If a flyback diode is preferred over a synchronous rectifier, remove Q1 and install a diode at the pads labeled D1. This board accepts devices such as the DFLS1100 from Diodes Inc.



30121109

FIGURE 5. Efficiency Comparison at 200 kHz

Under-Voltage Detector

The Under Voltage Detector can be used to monitor the input voltage, or any other system voltage as long as the voltage at the UV pin does not exceed its maximum rating. On this evaluation board the input voltage is monitored via resistors R2 and R3.

An appropriate pull-up voltage less than 10 volts must be connected to test point TP2-UVO on this evaluation board. R4 is the pull-up resistor for the UVO output. The under-voltage status can then be monitored at the TP3-Status test point.

On this evaluation board the UVO output switches low when the input voltage exceeds 12V, and it switches high when the input voltage is less than 11V. If it is desired to change the thresholds, the equations for determining the resistor values are:

$$R2 = \frac{V_{UVH} - V_{UVL}}{5 \,\mu A} = \frac{V_{UV(HYS)}}{5 \,\mu A}$$

$$R3 = \frac{R2 \times 2.5V}{V_{UVL} - 2.5V}$$

Where $V_{\rm UVH}$ is the upper threshold at VIN, and $V_{\rm UVL}$ is the lower threshold. The threshold at the UV pin is 2.5V.

The UVO output is high when the VCC voltage is below its UVLO threshold, or when the LM5006 is shutdown by grounding the TP1-SD test point, regardless of the voltage at the UV pin.



FIGURE 6. Complete Evaluation Board Schematic (As Supplied)

Monitor The Inductor Current

The inductor's current can be monitored or viewed on a scope with a current probe. Remove R9, and install an appropriate current loop across the two large pads where R9 was located. In this way the inductor's ripple current and peak current can be accurately determined.

Multiple Outputs

Multiple outputs can be produced by replacing the inductor (L1) with a transformer, and using a MOSFET (Q1) for synchronous rectification. The synchronous rectification is required to ensure the circuit is in continuous conduction mode at all values of the main output's load current. This ensures the secondary output voltages are correct at all times.

In Figure 15, a second isolated output is provided at $V_{\text{OUT2}}.$ Its regulation depends on the relative output voltages, current

levels at the both outputs, and the design of the transformer L1. The two outputs can be isolated, or share a common ground.

Figure 16 shows a circuit which provides a regulated 12V output, and two secondary 5V outputs. V_{OUT2} and V_{OUT3} can be isolated from V_{OUT1} and from each other, or share ground connections, depending on the application.

Scope Probe Adapters

Scope probe adapters are provided on this evaluation board for monitoring the waveform at the SW pin, and at the circuit's output (V_{OUT}), without using the probe's ground lead which can pick up noise from the switching waveforms.

www.national.com

Bill of Materials

	1		1	
Item	Description	Mfg., Part Number	Package	Value
C1	Ceramic Capacitor	TDK C3225X7R2A225M	1210	2.2 μF, 100V
C2	Ceramic Capacitor	TDK C3225X7R1C156M	1210	15 µF, 16V
C3	Ceramic Capacitor	TDK C1608X7R1C105K	0603	1 µF, 16V
C4	Ceramic Capacitor	TDK C1608X7R2A103K	TDK C1608X7R2A103K 0603	
C5	Ceramic Capacitor	TDK C2012X7R2A104M 0805		0.1 μF, 100V
C6	Ceramic Capacitor	TDK C1608X7R2A332K 0603		3300 pF, 100V
C7	Ceramic Capacitor	TDK C2012X7R2A104M 0805		0.1 μF, 100V
C8	Unpopulated			
C9	Ceramic Capacitor	TDK C1608X7R2A102K	0805	1000 pF, 100V
L1	Inductor	Coiltronics DR74-820-R or Wurth Electronics 744771182		82 uH,1A
Q1	N-Channel	Vishay Si2328DS	SOT-23	100V, 1.5A
	MOSFET			
R1	Resistor	Vishay CRCW0603191KF	0603	191kΩ
R2	Resistor	Vishay CRCW0603200KF	Vishay CRCW0603200KF 0603	
R3	Resistor	Vishay CRCW060359KOF	Vishay CRCW060359KOF 0603	
R4	Resistor	Vishay CRCW0603100KF 0603		100 kΩ
R5	Resistor	Vishay CRCW06033KO1F 0603		3.01 kΩ
R6	Resistor	Vishay CRCW06033KO1F 0603		3.01 kΩ
R7	Resistor	Vishay CRCW06030000Z	Vishay CRCW06030000Z 0603	
R8	Resistor	Vishay CRCW060336K5F 0603		36.5 kΩ
R9	Resistor	Vishay CRCW06030000Z 0603		0Ω jumper
U1	Switching Regulator	National Semiconductor LM5006MM	MSOP-10	

Circuit Performance



FIGURE 7. Efficiency vs Load Current



FIGURE 8. Efficiency vs Input Voltage







FIGURE 10. Switching Frequency vs. Input Voltage



FIGURE 11. Current Limit vs Input Voltage











Typical Waveforms







FIGURE 16. Generate Three Outputs

PC Board Layout



Board Silkscreen





Board Top Layer

30121118

AN-2050



Board Bottom Layer (Viewed from Top)

30121119

For more National Semiconductor product information and proven design tools, visit the following Web sites at: www.national.com

Pr	oducts	Design Support		
Amplifiers	www.national.com/amplifiers	WEBENCH® Tools	www.national.com/webench	
Audio	www.national.com/audio	App Notes	www.national.com/appnotes	
Clock and Timing	www.national.com/timing	Reference Designs	www.national.com/refdesigns	
Data Converters	www.national.com/adc	Samples	www.national.com/samples	
Interface	www.national.com/interface	Eval Boards	www.national.com/evalboards	
LVDS	www.national.com/lvds	Packaging	www.national.com/packaging	
Power Management	www.national.com/power	Green Compliance	www.national.com/quality/green	
Switching Regulators	www.national.com/switchers	Distributors	www.national.com/contacts	
LDOs	www.national.com/ldo	Quality and Reliability	www.national.com/quality	
LED Lighting	www.national.com/led	Feedback/Support	www.national.com/feedback	
Voltage References	www.national.com/vref	Design Made Easy	www.national.com/easy	
PowerWise® Solutions	www.national.com/powerwise	Applications & Markets	www.national.com/solutions	
Serial Digital Interface (SDI)	www.national.com/sdi	Mil/Aero	www.national.com/milaero	
Temperature Sensors	www.national.com/tempsensors	SolarMagic™	www.national.com/solarmagic	
PLL/VCO	www.national.com/wireless	PowerWise® Design University	www.national.com/training	

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

Copyright© 2010 National Semiconductor Corporation

For the most current product information visit us at www.national.com



National Semiconductor Americas Technical Support Center Email: support@nsc.com Tel: 1-800-272-9959

National Semiconductor Europe Technical Support Center Email: europe.support@nsc.com National Semiconductor Asia Pacific Technical Support Center Email: ap.support@nsc.com National Semiconductor Japan Technical Support Center Email: jpn.feedback@nsc.com