

Powering FPGAs Using LM201xx PowerWise® Synchronous Buck Regulators

National Semiconductor
Application Note 1745
P. Ranucci
October 2007




The LM201xx PowerWise® synchronous buck regulators are full-featured products, capable of delivering up to 5A of continuous output current. The devices in the family operate from input voltages between 2.95V and 5.5V and convert down to outputs as low as 0.8V. The integrated low RDSon FETs enable a very efficient power supply solution for the multiple rails required to power a FPGA. All of the devices are current-mode controlled providing excellent line regulation and load transient response, and require only two external components for compensation. They feature precision enable, soft-start, tracking, UVLO, OVP, over-temp protection, and PGOOD. The soft-start pin can be used with a capacitor to control start-up inrush current or with an external voltage source to track or sequence multiple supplies. All devices can start into a pre-biased output without discharging it, and they have a diode emulation mode for higher efficiency at light loads. The devices are differentiated by output current capability (3A, 4A, and 5A), frequency (500 kHz, 1 MHz, and 1.5 MHz), and synchronization mode (free-running, sync-in, sync-out, and external resistor adjust). Based on the supply requirements of the FPGA design, an appropriate combination of devices can combine to create a small, efficient, and complete solution.

FPGA Power Supply Requirements

There are several high performance FPGAs currently on the market such as the Xilinx Virtex and Spartan series, and the Altera Cyclone and Stratix series. All of these require multiple power rails including the FPGA core, the I/O, as well as additional rails for powering clocks, PLLs, transceivers, and other circuitry. The core voltage in FPGAs can currently be as low as 0.9V with the current demand for this rail being highly dependent on the utilization of the FPGA. FPGA manufacturers offer power estimation software which assists users in identifying their power needs based on the performance requirements of the design. The I/O rail can also have demanding power needs depending on the number of I/O registers employed in the FPGA design. Most of the latest generation FPGAs have internal POR circuitry which can eliminate the need for power rail sequencing. Select FPGAs specify input inrush currents for particular power-up sequences and others require sequencing rails to avoid start-up or latch-up problems. Start-up time requirements for FPGA rails are varied ranging from 100-200 us at the fastest and 50-100 ms at the slowest.

Example FPGA Power Supply Design

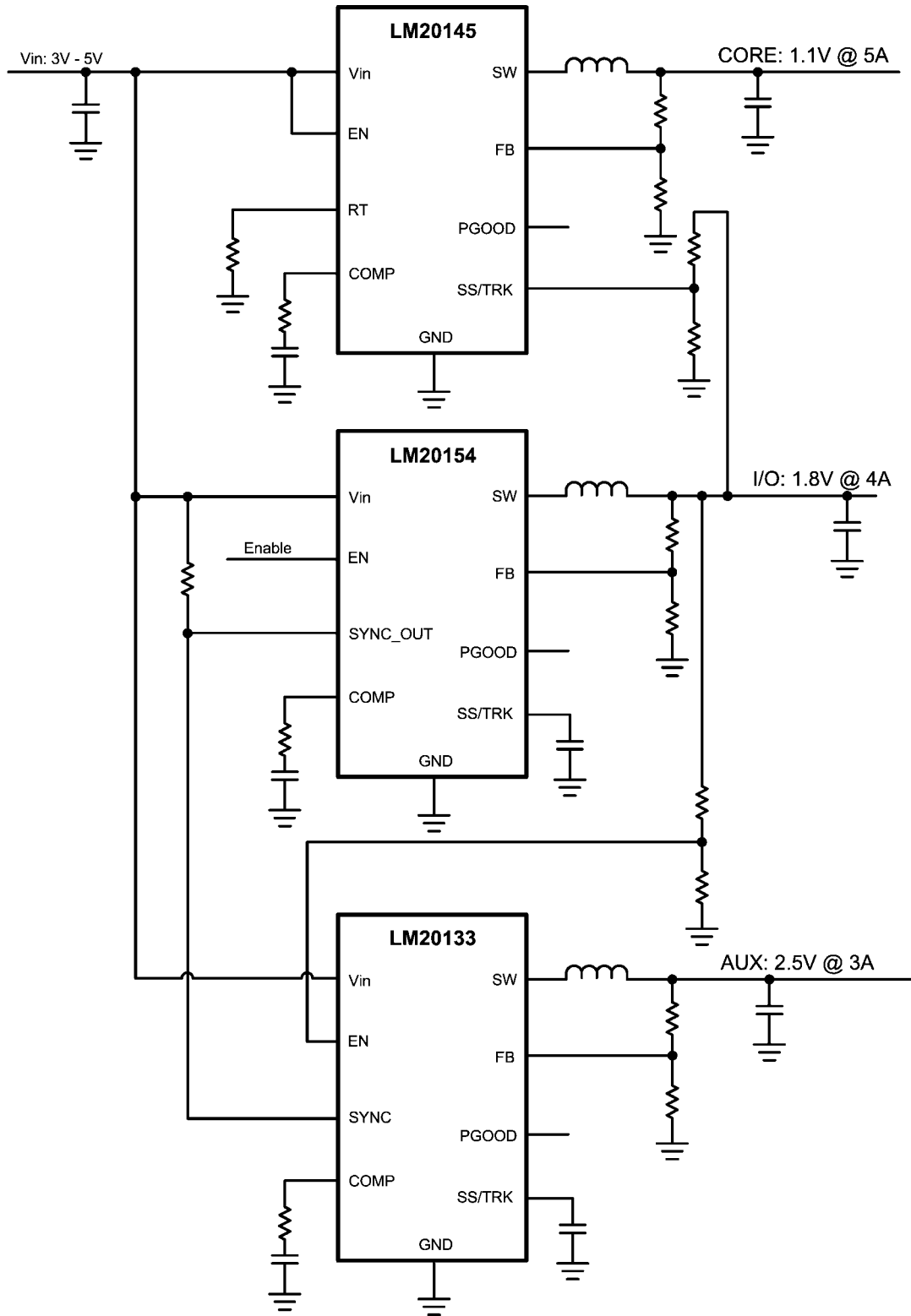


30043301

FIGURE 1. Example FPGA Power Design

For the purposes of illustration, an example FPGA power supply design is shown in block diagram form in *Figure 1*. This design features a LM20145 supplying a core voltage of 1.1V capable of delivering up to 5A, a LM20154 supplying an I/O voltage arbitrarily chosen as 1.8V capable of delivering up to 4A, and a LM20133 supplying an auxiliary rail of 2.5V at 3A. Output voltage rails can regulate within 1.5% over temp and

Design Features

One of the features highlighted in this design is the many useful frequency synchronization options available. The LM20145 has a resistor adjustable frequency which can be tuned to keep switching noise within a particular spectrum. The LM20133 is a sync-in part which can be synchronized to an external clock signal to achieve the same effect. In this case the LM20133 is synchronized to the sync-out signal coming from the LM20154 which has the added benefit of synchronizing the two parts 180° out of phase. This reduces input ripple current on the input power supply and can thus reduce the input capacitor requirements. *Figure 2* shows an example of input ripple current reduction using out of phase converters.

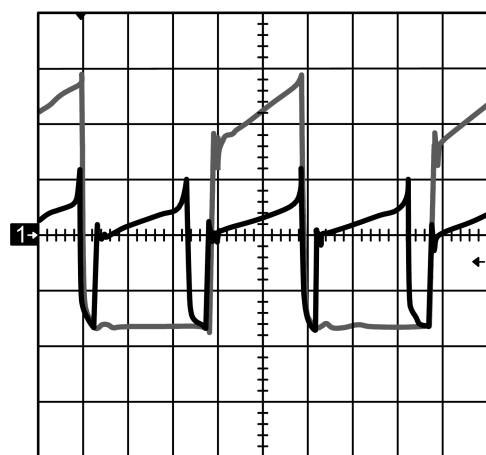

200 ns/DIV


Ch1: i_{Cin} (2A/Div), Ref2: i_{Cin} (2A/Div)

30043302

FIGURE 2. Input Capacitor Current Comparison of LM20134/LM20154 (out of phase) and LM20154/LM20154 (in phase) based Buck Regulators

are also easily scaled by a resistor divider between the output and the FB pin. All of the devices are packaged in a slim exposed pad TSSOP-16 package enabling a compact power supply design. Additionally, they are pin-to-pin compatible so output current capability can be easily scaled to the FPGA design's power requirements simply by choosing different devices in the family.

All of the devices have flexible sequencing options as shown in *Figure 3*. In the example design, the LM20145 is "tracked" off of the I/O rail by using the SS pin with a resistive voltage divider. This type of sequencing, known as simultaneous sequencing, allows the voltage difference between the two rails to be minimized which can eliminate parasitic conduction paths between the two rails. The precision EN pin on the LM20133 allows it to be sequentially sequenced by the LM20154 using a voltage divider from the I/O rail. Another method for sequencing involves attaching the PGOOD pin of one part to the EN pin of another. In that case the second part will enable when the output of the first has reached 94% (typ) of its final value.

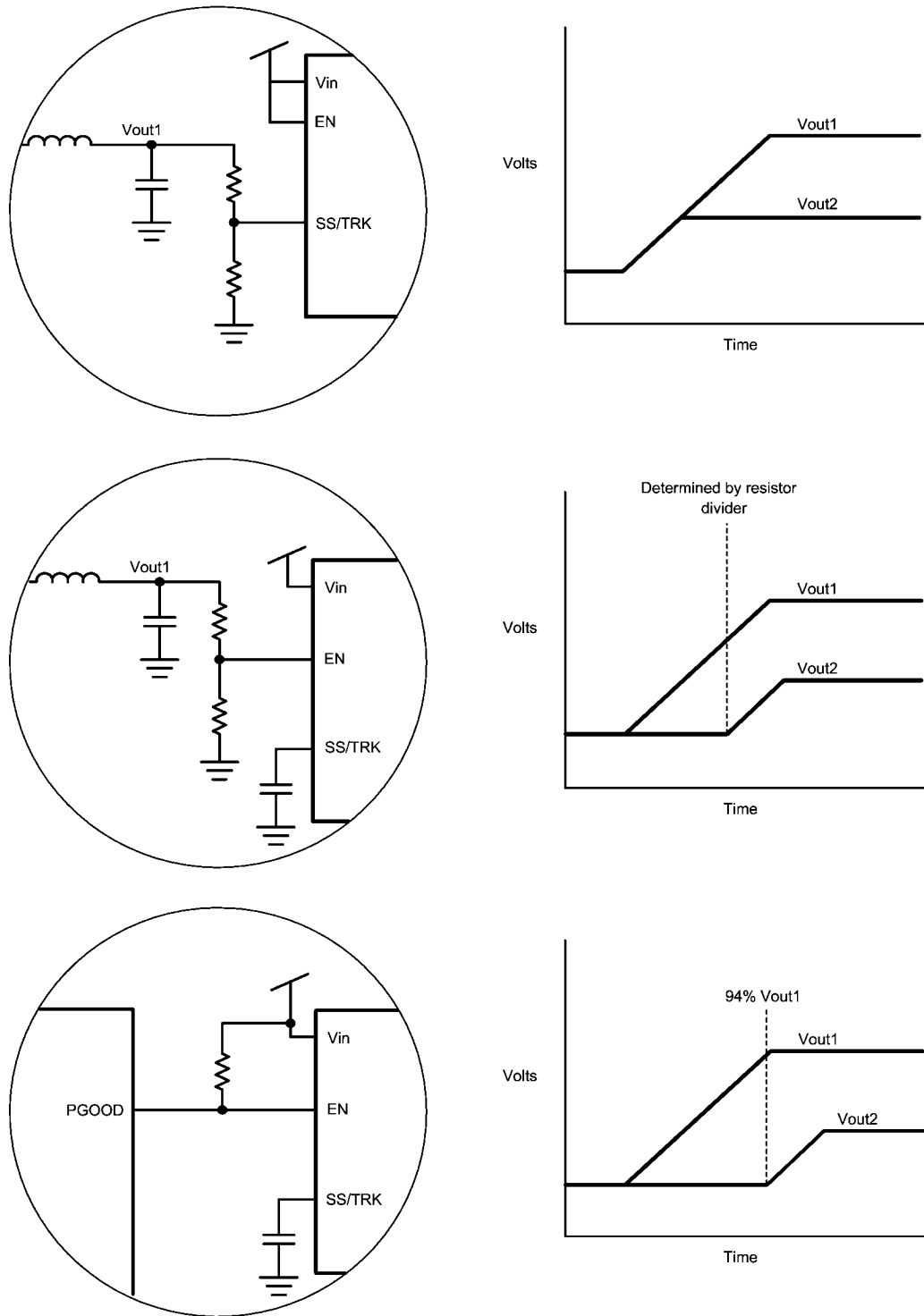

30043303

FIGURE 3. Multiple Sequencing Options

Conclusion

The LM201xx family offers a full range of features and options enabling a FPGA designer to fully customize their power so-

lution to meet the system application needs. Full details of the many options and useful features of the entire LM201xx family can be found in the product datasheets at www.national.com/switcher.

Notes

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

Copyright© 2007 National Semiconductor Corporation

For the most current product information visit us at www.national.com



**National Semiconductor
Americas Customer
Support Center**
Email:
new.feedback@nsc.com
Tel: 1-800-272-9959

**National Semiconductor Europe
Customer Support Center**
Fax: +49 (0) 180-530-85-86
Email: europe.support@nsc.com
Deutsch Tel: +49 (0) 69 9508 6208
English Tel: +49 (0) 870 24 0 2171
Français Tel: +33 (0) 1 41 91 8790

**National Semiconductor Asia
Pacific Customer Support Center**
Email: ap.support@nsc.com

**National Semiconductor Japan
Customer Support Center**
Fax: 81-3-5639-7507
Email: jpn.feedback@nsc.com
Tel: 81-3-5639-7560