

# Replacing the CLC012 Adaptive Cable Equalizer with the LMH0074

National Semiconductor  
Application Note 2003  
Gary Melchior  
October 5, 2009



## Introduction

The LMH0074 SD-SDI adaptive cable equalizer can replace the CLC012 adaptive cable equalizer in many applications. The LMH0074 and CLC012 are both adaptive cable equalizers designed to recover data sent over long cables. The supported data rates and cable lengths are similar between the two devices. The LMH0074 and CLC012 are both rated for industrial temperature range operation ( $-40^{\circ}\text{C}$  to  $+85^{\circ}\text{C}$ ). The LMH0074, the newer generation SDI equalizer, has more advanced features and is pin compatible with the LMH0044

HD-SDI equalizer and the LMH0344 or LMH0384 3G-SDI equalizer. This allows a forward migration path from SD to HD to 3G. The LMH0074 also offers a lower supply voltage (3.3V), enabling system designers to migrate to lower-power designs. The LMH0074 provides a 38% power savings over the CLC012, with typical power of 209 mW in comparison with 340 mW for the CLC012.

*Table 1* shows the key differences between the CLC012 and LMH0074.

TABLE 1. CLC012 and LMH0074 Key Differences



	CLC012	LMH0074
Power Supply ( $V_{CC}$ )	5.0V	3.3V
Package	14-pin SOIC	16-pin LLP
Data Rates	50 to 650 Mbps	125 to 540 Mbps
ESD Rating	$\geq \pm 500\text{V}$ HBM	$\geq \pm 8\text{ kV}$ HBM
Input Interface	Requires $100\Omega$ series resistor on each input	Requires return loss network of 6.8 nH in parallel with $75\Omega$ on active input
Output Structure	Open collector, requires external $75\Omega$ pullups to 5V	CML with internal $50\Omega$ pullups (to 3.3V)
AEC Capacitor Value	100 pF	1.0 $\mu\text{F}$
LOS/CD and Mute	LOS, $\overline{\text{MUTE}}$	$\overline{\text{CD}}$ , MUTE
Other Features	OEM	$\text{MUTE}_{\text{REF}}$ , BYPASS

## How To Replace the CLC012 with the LMH0074

Replacing the CLC012 with the LMH0074 requires a few simple steps. The device packages and pinouts are quite different so this change requires a new PCB layout; however, the equalizer core and features are similar. To replace the CLC012 with the LMH0074, follow these steps:

1. Change the power supply from 5V to 3.3V.
2. Remove the  $100\Omega$  series resistors at the input to the equalizer.
3. Add an input return loss network consisting of a 6.8 nH inductor in parallel with a  $75\Omega$  resistor on the active input between the BNC and the  $75\Omega$  termination.
4. Removed the  $75\Omega$  pullups on the output and replace with a  $100\Omega$  differential termination located at the input of the next stage. The outputs may also be AC coupled, but no pullups are required.
5. Replace the 100 pF AEC capacitor with a 1.0  $\mu\text{F}$  AEC capacitor.

*Figure 1* shows the typical application for the CLC012, and *Figure 2* shows the typical application for the LMH0074.

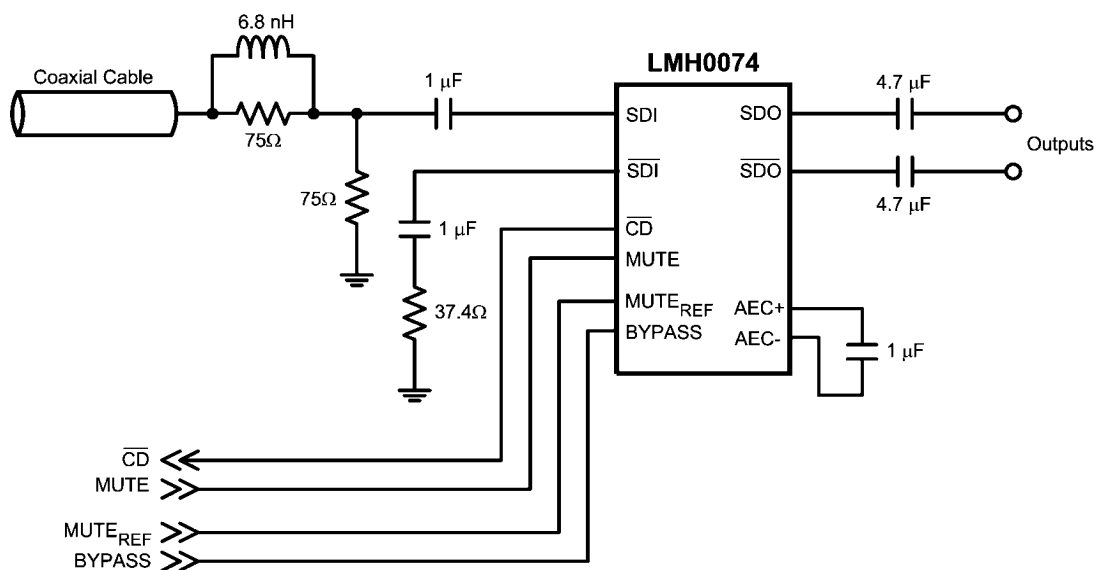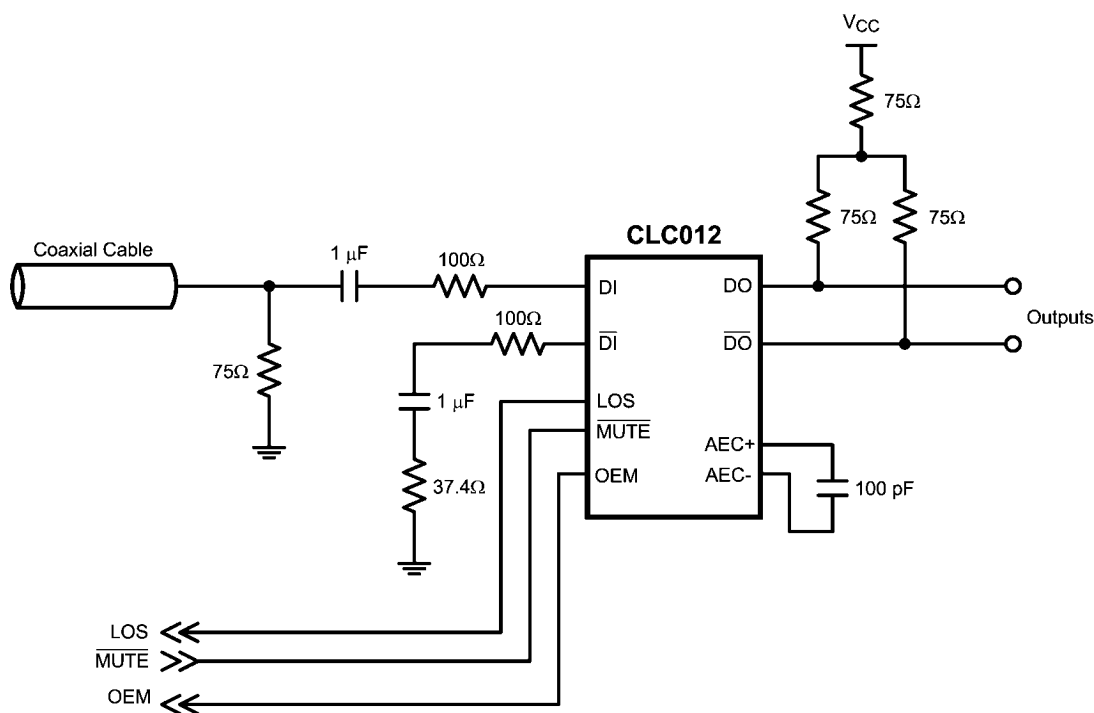

## INPUT INTERFACE

For the typical input interface, the equalizer receives a single-ended signal over 75Ω coaxial cable. The CLC012 requires a 75Ω termination to ground, a 1.0 μF input coupling capacitor, and a 100Ω series resistor on each input. On the unused input, the 75Ω termination to ground is replaced by 37.4Ω to match the impedance on the active side (which has the 75Ω cable in parallel with the 75Ω termination).

The 100 $\Omega$  series resistors are not required for the LMH0074; however, a 6.8 nH inductor in parallel with a 75 $\Omega$  resistor should be added in series on the active input between the input BNC and the 75 $\Omega$  pulldown resistor (see [Figure 2](#)). This network provides excellent input return loss. All of these components should be placed close to the LMH0074 input pins. To comply with the 1 V<sub>P-P</sub> levels required for ITU-T G.703, CLC012 applications sometimes include a 2 dB 75 $\Omega$  attenu-

ator at the equalizer input. This 2 dB attenuator decreases the voltage swing to the range required by the CLC012 for proper cable equalization ( $800\text{ mV} \pm 10\%$ ). The LMH0074 expects the same cable input voltage swing as the CLC012 ( $800\text{ mV} \pm 10\%$ ), so this same 2 dB attenuator may be used for LMH0074 applications as well.

## OUTPUT INTERFACE

The CLC012 outputs are open collector and require  $75\Omega$  pullups to 5V to generate an output voltage. This structure has some limitations when interfacing to non-5V systems. The CLC012 outputs are essentially cut off if the DO output voltage drops below  $V_{CC} - 1.6\text{V}$  (typically  $3.4\text{V}$ ), so this prevents DC-coupling to other  $3.3\text{V}$  devices.

The LMH0074 provides much more flexibility. The LMH0074 outputs are CML with internal  $50\Omega$  pullups to  $3.3\text{V}$ . They may be DC coupled to many more types of inputs, including the LMH0026 or LMH0036 reclocker and the LMH0001 cable driver. Typically only a far-end differential termination (a simple resistor) is required. If the LMH0074 output common mode voltage is not compatible with the input common mode voltage of the receiving device, the outputs may be AC coupled as shown in [Figure 2](#). The outputs do not require pullups to  $V_{CC}$ .

## AEC CAPACITOR VALUE

The CLC012 AEC capacitor is typically  $100\text{ pF}$  and may be changed to change the adaptive loop time constant. For the LMH0074, the AEC capacitor should be  $1.0\text{ }\mu\text{F}$  only. The LMH0074 was designed and optimized for a  $1.0\text{ }\mu\text{F}$  AEC capacitor and it should not be changed.

## LOSS OF SIGNAL / CARRIER DETECT AND MUTE

The CLC012 has a loss of signal (LOS) indicator that complies with the ITU-T standards. The LMH0074 has a standard car-

rier detect (CD) indicator for input signal detection. The LMH0074 carrier detect indicator is very robust and the input signal detection is similar to that of the CLC012, but it does not strictly comply to the ITU-T standards.

In CLC012 applications, the LOS pin is typically tied to the  $\overline{\text{MUTE}}$  pin to inhibit the output when there is no input signal. For the LMH0074 this can be done as well. The only difference is that the polarity of the input signal detect and mute is reversed for the LMH0074; the carrier detect pin,  $\overline{\text{CD}}$ , is active low, and the mute pin, MUTE, is active high.

## OTHER FEATURES

The CLC012 has an Output Eye Monitor which shows the equalized eye pattern prior to the output comparator. This feature is not included in the LMH0074; however, the LMH0074 includes features in addition to those in CLC012, such as the  $\text{MUTE}_{\text{REF}}$  and BYPASS functions.  $\text{MUTE}_{\text{REF}}$  sets the threshold for CD and (with  $\overline{\text{CD}}$  tied to MUTE) determines the amount of cable to equalize before muting the outputs. This may be useful to limit the maximum cable length that can be equalized, or for very noisy environments where CD would need to be less sensitive. BYPASS passes the input signal through to the output with no equalization. This may be useful for very low data rate applications.

## 100 $\Omega$ DIFFERENTIAL TWISTED PAIR CABLE APPLICATIONS

The equalizers can both be used for differential twisted pair cable applications. [Figure 3](#) shows the differential twisted pair input interface for the CLC012 and [Figure 4](#) shows the differential twisted pair input interface for the LMH0074.

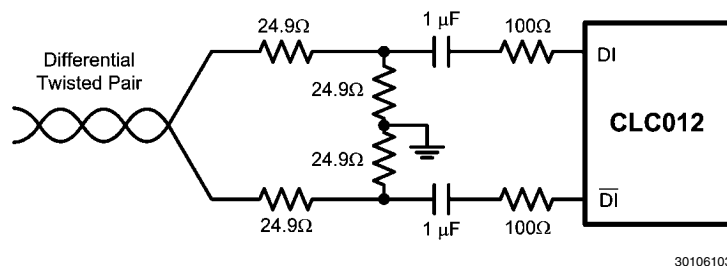


FIGURE 3. CLC012 Differential Twisted Pair Input Interface

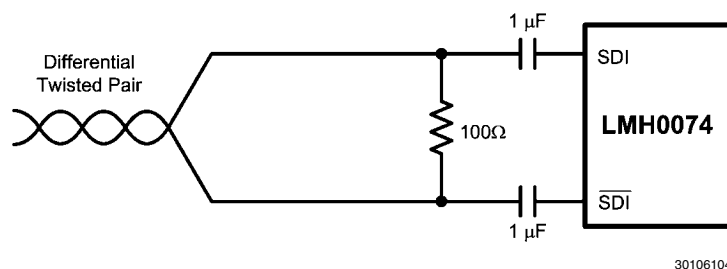


FIGURE 4. LMH0074 Differential Twisted Pair Input Interface

## LMH0074 Enhancements over the CLC012

The LMH0074 is a solid upgrade and good replacement for the CLC012. It is designed in a newer, more advanced process. The LMH0074 offers lower power, better ESD protection, a more flexible output interface, and new features such

as the ability to bypass equalization. The LMH0074's smaller, space-saving package allows for more compact designs. The PCB layout is simpler as the LMH0074 requires less PCB components overall than the CLC012. In addition, the LMH0074's pin compatibility with HD-SDI and 3G-SDI equalizers offers an easy upgrade path and allows future-proof designs.

## Notes

## Notes

For more National Semiconductor product information and proven design tools, visit the following Web sites at:

Products		Design Support	
Amplifiers	<a href="http://www.national.com/amplifiers">www.national.com/amplifiers</a>	WEBENCH® Tools	<a href="http://www.national.com/webench">www.national.com/webench</a>
Audio	<a href="http://www.national.com/audio">www.national.com/audio</a>	App Notes	<a href="http://www.national.com/appnotes">www.national.com/appnotes</a>
Clock and Timing	<a href="http://www.national.com/timing">www.national.com/timing</a>	Reference Designs	<a href="http://www.national.com/refdesigns">www.national.com/refdesigns</a>
Data Converters	<a href="http://www.national.com/adc">www.national.com/adc</a>	Samples	<a href="http://www.national.com/samples">www.national.com/samples</a>
Interface	<a href="http://www.national.com/interface">www.national.com/interface</a>	Eval Boards	<a href="http://www.national.com/evalboards">www.national.com/evalboards</a>
LVDS	<a href="http://www.national.com/lvds">www.national.com/lvds</a>	Packaging	<a href="http://www.national.com/packaging">www.national.com/packaging</a>
Power Management	<a href="http://www.national.com/power">www.national.com/power</a>	Green Compliance	<a href="http://www.national.com/quality/green">www.national.com/quality/green</a>
Switching Regulators	<a href="http://www.national.com/switchers">www.national.com/switchers</a>	Distributors	<a href="http://www.national.com/contacts">www.national.com/contacts</a>
LDOs	<a href="http://www.national.com/ldo">www.national.com/ldo</a>	Quality and Reliability	<a href="http://www.national.com/quality">www.national.com/quality</a>
LED Lighting	<a href="http://www.national.com/led">www.national.com/led</a>	Feedback/Support	<a href="http://www.national.com/feedback">www.national.com/feedback</a>
Voltage Reference	<a href="http://www.national.com/vref">www.national.com/vref</a>	Design Made Easy	<a href="http://www.national.com/easy">www.national.com/easy</a>
PowerWise® Solutions	<a href="http://www.national.com/powerwise">www.national.com/powerwise</a>	Solutions	<a href="http://www.national.com/solutions">www.national.com/solutions</a>
Serial Digital Interface (SDI)	<a href="http://www.national.com/sdi">www.national.com/sdi</a>	Mil/Aero	<a href="http://www.national.com/milaero">www.national.com/milaero</a>
Temperature Sensors	<a href="http://www.national.com/tempsensors">www.national.com/tempsensors</a>	SolarMagic™	<a href="http://www.national.com/solarmagic">www.national.com/solarmagic</a>
Wireless (PLL/VCO)	<a href="http://www.national.com/wireless">www.national.com/wireless</a>	PowerWise® Design University	<a href="http://www.national.com/training">www.national.com/training</a>

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

### LIFE SUPPORT POLICY

**NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION.** As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

Copyright© 2009 National Semiconductor Corporation

For the most current product information visit us at [www.national.com](http://www.national.com)



**National Semiconductor  
Americas Technical  
Support Center**  
Email: [support@nsc.com](mailto:support@nsc.com)  
Tel: 1-800-272-9959

**National Semiconductor Europe  
Technical Support Center**  
Email: [europe.support@nsc.com](mailto:europe.support@nsc.com)

**National Semiconductor Asia  
Pacific Technical Support Center**  
Email: [ap.support@nsc.com](mailto:ap.support@nsc.com)

**National Semiconductor Japan  
Technical Support Center**  
Email: [jpn.feedback@nsc.com](mailto:jpn.feedback@nsc.com)