Switched Capacitor Circuits Provide Efficient and Functional White LED Drive

National Semiconductor Application Note 1251 Clinton Jensen September 2002



Introduction

Since the conception of cellular phones, PDAs, and handheld computers, there has been a continuing push for more useful and dynamic displays. One of the more drastic changes in miniature display technology has emerged due to the availability of Internet content, pictures, and videos on ever-shrinking personal devices. The promise of more content and functionality has caused a migration toward higher resolution color displays. This presents some added design issues, however, as a color LCD display requires white backlighting as opposed to the more standard green. The current options are using a cold cathode fluorescent lamp (CCFL), an electroluminescent backlight, or newer white LEDs. White LEDs are quickly becoming the light of choice because of their falling costs, longer life, and smaller size. The problem this presents is that the white LED has a high

Switched Capacitor Voltage Regulator

voltage drop (3.1V to 4.0V depending on manufacturer) as compared to the green LED with a voltage drop of 1.8V to 2.7V. Whereas the green LED can be powered directly from the commonly used Li-Ion battery, with a linear regulator, and a ballast resistor, the white LED used for backlight or frontlight purposes will requires the battery voltage be boosted.

National has many solutions for driving LEDs including switched capacitor converters and inductive based switching regulators. This application note will describe some different switched capacitor methods of driving white LEDs and the benefits of each. The main areas of concern for most designers of portable equipment are efficiency, size, cost, functionality, and LED current matching. Balancing these competing demands will help designers make the right choice for his or her application.



FIGURE 1. Switched Capacitor Voltage Regulator

This circuit is capable of supplying 90mA at 4.1V output (see the LM3355 for up to 50mA output current). The number of LEDs that may be driven depends on the LED current desired in each. The current is set using the equation:

$I_{D} = (4.1V - V_{F})/R_{SET}$

where VF is the forward voltage drop of the LED chosen. As the LEDs are in parallel, the current matching is not perfect. The current matching will depend on the forward voltage drop of each LED and how well they match. This circuit is smaller than a switching regulator solution yet still maintains an average efficiency of about 70% (actual efficiency to LEDs, some power is dissipated by the ballast resistors) over the Li-lon input voltage range. The brightness of the LEDs in this circuit may be controlled using a 60Hz to 200Hz PWM signal on the shutdown (SD) pin.

The switched capacitor voltage regulator approach is desirable for applications requiring 1 to 10 LEDs, high efficiency, brightness control functionality, lower cost and small solution size. However, this solution suffers from poor brightness matching due to varying LED currents.

AN-1251

Switched Capacitor Current Regulator

The second method presented here is a switched capacitor current regulator. Current regulation is achieved by using a switched capacitor boost circuit to drive a set of current sources. Figure 2 shows the LM2792 switched capacitor LED driver.



FIGURE 2. Switched Capacitor Current Regulator

This circuit uses a switched capacitor doubler (2X) circuit to power the current sources. It is capable of driving 1 to 2 LEDs at up to 32mA total (16mA each LED when using two). The current is set using the resistor RSET and the BRGT pin (refer to the datasheet for a description on setting current using RSET and the BRGT pin). Because current sources are used, the LED current matching is exceptional, within one percent. This circuit yields a smaller solution size than the voltage regulator and it provides more functionality, although at the cost of a significantly lower efficiency. The brightness can be controlled one of two ways. A PWM signal between 100Hz and 1kHz may be used at the shutdown (SD) pin as in the previous two examples. An analog voltage can be applied to the BRGT pin as well. This provides the ability to control the brightness with much better linearity. The BRGT pin also allows a variety of lighting patterns and effects since a continuous analog waveform of any desired shape can be used for controlling LED brightness.

For driving up to 4 LEDs the LM2794 or LM2795 may be used. These circuits are similar to the LM2792 in that they

have all the same functionality. The difference is that a three halves (3/2X) charge pump is used to power the current sources. This provides higher efficiency (see Graph 1) since the current sources will have a reduced voltage drop across the transistors. They are capable of supplying a total of 60mA for up to 4 LEDs. The LM2794 and LM2795 also do not require the diode D shown in the LM2792 schematic. The only other difference is that where the LM2792 requires some signal at the BRGT pin to set the LED current, the LM2794 and LM2795 LED currents can be set using only RSET if desired. LM2794 and LM2795 are identical except for the polarity of the shutdown pin, to make it easier for designers to incorporate these solutions into existing systems.

The switched capacitor current regulator approach is desirable for circuits requiring 1 to 4 LEDs, precise current matching, small solution size, lowest cost and the highest functionality and control.

Switched Capacitor Current Regulator (Continued)



Comparison of LM2792 and LM2794/5 Efficiency

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

- Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
- 2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

 National Semiconductor Corporation Americas Email: support@nsc.com
 National Semiconductor Europe

 www.national.com
 Fax: +49 (0) 180-530 85 86 Email: europe.support@nsc.com

 bettsch
 Email: europe.support@nsc.com

 bettsch
 Tel: +49 (0) 69 9508 6208 English

 Tel: +44 (0) 870 24 0 2171
 Français Tel: +33 (0) 1 41 91 8790

National Semiconductor Asia Pacific Customer Response Group Tel: 65-2544466 Fax: 65-2504466 Email: ap.support@nsc.com National Semiconductor Japan Ltd. Tel: 81-3-5639-7560 Fax: 81-3-5639-7507

AN-125

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.